



RadioShack®

Science and Communication Circuits and Projects

Build projects
to detect:

- Rain drops
- Temperature
- Earthquakes
- Haze
- Pressure
- Solar radiation
- Motion
- Light
- And more



Forrest M. Mims III


CIRCUIT SYMBOLS



FIXED
RESISTOR



VARIABLE
RESISTOR

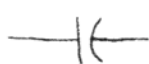

FIXED
CAPACITOR



POLARIZED
CAPACITOR



RECTIFIER/
DIODE




ZENER
DIODE



PNP
TRANSISTOR



NPN
TRANSISTOR

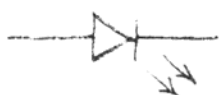

LED



SOLAR
CELL



PHOTO-
RESISTOR



PHOTO-
TRANSISTOR



CONNECTED
WIRES



UNCONNECTED
WIRES



POSITIVE
SUPPLY




GROUND



SPST
SWITCH




SPDT
SWITCH

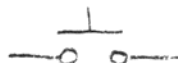

NORMALLY
OPEN
PUSHBUTTON



NORMALLY
CLOSED
PUSHBUTTON

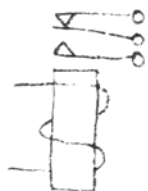

RELAY



TRANSFORMER



SPEAKER



PIEZO-
SPEAKER



METER



LAMP



BATTERY



OP-AMP

ENGINEER'S MINI-NOTEBOOK COLLECTION

ELECTRONIC SENSOR CIRCUITS & PROJECTS

BY
FORREST M. MIMS III

FIRST PRINTING-2000

COPYRIGHT ©1996, 1998-2000 BY FORREST M. MIMS III
ALL RIGHTS RESERVED

PRINTED IN THE UNITED STATES OF AMERICA

ABOUT THE ENGINEER'S MINI-NOTEBOOK COLLECTION

EACH BOOK IN THIS COLLECTION INCLUDES THREE OR FOUR ENGINEER'S MINI-NOTEBOOKS. EACH BOOK INCLUDES BOTH STANDARD CIRCUITS AND CIRCUITS DESIGNED BY FORREST M. MIMST III. EACH CIRCUIT WAS BUILT AND TESTED AT LEAST TWICE. THE CIRCUITS WERE ALSO BUILT FROM THE FINAL BOOK TO FIND ERRORS.

VARIATIONS IN COMPONENTS AND CONSTRUCTION METHODS MAY CAUSE YOUR RESULTS TO DIFFER FROM THOSE DESCRIBED HERE. THEREFORE THE AUTHOR AND RADIOSHACK ARE NOT RESPONSIBLE FOR THE SUITABILITY OF THE CIRCUITS FOR ANY APPLICATION. FOR EXAMPLE, THE CIRCUITS IN THIS BOOK SHOULD NOT BE USED FOR MEDICAL APPLICATIONS, SAFETY DEVICES, TRAFFIC CONTROLLERS OR ANY OTHER USE THAT MIGHT SOMEHOW RESULT IN DAMAGE TO PROPERTY OR INJURY TO YOU OR OTHERS. IT IS YOUR RESPONSIBILITY TO DETERMINE IF COMMERCIAL USE, SALE OR MANUFACTURE OF ANY DEVICE BASED ON INFORMATION IN THIS BOOK INFRINGES ANY PATENT, COPYRIGHT OR OTHER RIGHT.

FOR MORE INFORMATION

DUE TO THE MANY INQUIRIES RECEIVED BY THE AUTHOR AND RADIOSHACK, IT IS NOT POSSIBLE TO PROVIDE CUSTOM CIRCUIT DESIGNS AND TECHNICAL ADVICE. YOU CAN LEARN MORE ABOUT ELECTRONICS FROM OTHER BOOKS AVAILABLE FROM RADIOSHACK AND FROM RADIOSHACK LAB KITS. ELECTRONICS MAGAZINES ARE ALSO A GOOD SOURCE OF INFORMATION. VARIOUS ELECTRONICS SITES ON THE INTERNET AND WORLD WIDE WEB ARE ALSO VERY HELPFUL.

I. SENSOR PROJECTS	9
OVERVIEW	9
DESIGN TIPS	9
ELECTRONIC SENSORS	10
GO-NO GO SENSORS	10
ANALOG SENSORS	11
BASIC SENSOR CIRCUITS	12
SENSORS AND COMPUTERS	13
TOUCH SWITCHES	14
MULTI-LAYER SWITCH	14
TACTILE FEEDBACK SWITCH	14
WHISKER-STYLE LEVER SWITCH	15
PUFF SWITCH	16
PAPER CLIP SWITCH	17
PHONE PLUG SWITCH	17
TILT SWITCH	17
MUSIC WIRE VIBRATION SENSOR	18
PIEZOELECTRIC VIBRATION SENSOR	19
PENDULUM SWITCH	20
PENDULUM QUADRANT SWITCH	21
SWITCH-TYPE ALARM SYSTEMS	22
OPEN-CIRCUIT ALARMS	22-23
CLOSED-CIRCUIT ALARM	23
INTELLIGENT SECURITY ALARM	24-25
FIRE OR WATER SENSOR	26
PULL SWITCH	27
	3

VOLTAGE SENSORS	28-29
ANALOG PRESSURE SENSOR	30-31
PRESSURE-TO-VOLTAGE SENSOR	31
STRAIN SENSORS	32
STRAIN SENSOR APPLICATIONS	33
STRAIN SENSOR DESIGNS	33
STRAIN SENSOR RELAY	34
STRAIN SENSOR TONE GENERATOR	34
STRAIN SENSOR AMPLIFIER	35
MAGNETIC FIELD SENSOR	36
MAGNETIC FIELD SWITCH	37
MAGNETIC FIELD AMPLIFIER	37
VIDEO MONITOR SENSORS	38
VIDEO MONITOR TONE GENERATOR	39
VIDEO MONITOR RELAY CIRCUITS	40-41
VIDEO MONITOR SENSOR PROGRAMS	42-43
LIGHTNING SENSOR	44-45
INFRARED SENSOR	46
INFRARED SWITCH	46
INFRARED AMPLIFIER	47
POLARIZED LIGHT	48
POLARIZED LIGHT SENSOR	49
INTEGRATED LIGHT SENSORS	50
LIGHT-TO-TONE SENSOR	50
IR REMOTE CONTROL SENSOR	51
LIGHT ACTIVATED RELAY	51
OPTICAL LEVEL SENSORS	52
VARIABLE TONE LEVEL SENSOR	52
SWITCHED TONE LEVEL SENSOR	52

II. MAGNET SENSOR PROJECTS

OVERVIEW	53
MAGNETITE	53
MAGNETIC FIELDS	54
MAGNETIC POLES	54
MAGNETIC FIELD INTENSITY	55
EARTH'S MAGNETIC FIELD	55
EARTH'S GEOGRAPHIC POLES	56
EARTH'S MAGNETIC POLES	56
LIVING MAGNETS	57
MAGNETIC BACTERIA	57
APPLICATIONS FOR MAGNETS	58
MAGNET CONFIGURATIONS	59
TEMPORARY MAGNETS	60
PERMANENT MAGNETS	60
USING AND CARING FOR MAGNETS	61
THE COMPASS	62
MAPPING A MAGNETIC FIELD	63
ELECTROMAGNET	64
SOLENOID	64
ELECTROMAGNETIC RELAY	65
RELAY DRIVER	65
MAGNET SWITCHES	66
MAGNETIC SWITCH INTERFACE	67
MAGNETIC-ACTUATED TONE	67
THE HALL EFFECT	68
APPLICATIONS FOR HALL SENSORS	69
HALL SENSOR BASICS	70
BASIC HALL SENSOR	70
BASIC HALL SENSOR CIRCUIT	70
HALL SENSOR OUTPUT VOLTAGE	71
HALL SENSOR + LOGIC CIRCUIT	72

INTEGRATED DIGITAL HALL SENSOR	72
HALL SENSOR + AMPLIFIER	73
INTEGRATED LINEAR HALL SENSOR	73
HALL SENSOR SPECIFICATIONS	74
BASIC GAUSS METER	74
POWER HALL SENSOR	75
HALL LAMP DRIVER	75
 HALL SENSOR OPERATING TIPS	 76
HALL SENSOR MAGNET SEPARATION	77
FLUX CONCENTRATORS	77
BEST MAGNET ARRANGEMENTS	78
HEAD-ON OPERATION	78
SLIDE-BY OPERATION	78
PUSH-PUSH OPERATION	79
PUSH-PULL OPERATION	79
 INTERFACING DIGITAL SENSORS	 80
LED INTERFACE	80
TRANSISTOR INTERFACE	80
TTL LOGIC INTERFACE	81
CMOS LOGIC INTERFACE	81
 APPLICATION CIRCUITS	 82
FERROUS METAL INDICATOR	82
HALL SENSOR RELAY	83
LEVEL INDICATOR	84
MAGNET POSITION DETECTOR	85
DUAL-OUTPUT HALL SENSORS	86
FIELD STRENGTH BARGRAPH	87
HALL SENSOR DIRECTION INDICATOR	88
ULTRA-SENSITIVE MAGNET SWITCH	89
MAGNET MUSIC	90
MUSICAL PENDULUM	91
DAMPED OSCILLATING TONE	91
PRESSURE-SENSITIVE TONE	91
SUPER-SENSITIVE FIELD SENSOR	92
SUPER-SENSITIVE FIELD SWITCH	93
GIANT COMPASS MAGNETOMETER	94
HALL SENSOR NORTH COMPASS	95
SPECIALIZED HALL SENSORS	96
A3421 DIRECTION SENSOR	96
ATSG10 GEAR TOOTH SENSOR	96

III. SOLAR CELL PROJECTS

OVERVIEW	97
SOLAR ENERGY MILESTONES	98-99
ENERGY FROM THE SUN	100
THE SOLAR CONSTANT	100
SOLAR CONSTANT TABLE	101
SUNLIGHT AND ATMOSPHERE	102
SOLAR CELLS	104
HOW SOLAR CELLS WORK	104
SOLAR CELL EFFICIENCY	105
SILICON SOLAR CELL RATINGS	106
SILICON SOLAR CELL VOLTAGE	106
INCREASING SOLAR CELL VOLTAGE	106
SILICON SOLAR CELL CURRENT	107
INCREASING SOLAR CELL CURRENT	107
SOLDERING LEADS TO SOLAR CELLS	108
MOUNTING SOLAR CELLS	110
ADVANTAGES OF MOUNTED CELLS	110
INSTALLING CELLS IN AN ENCLOSURE	110
MOUNTING SOLAR CELLS ON A PANEL	111
SOLAR CELL CONCENTRATORS	112
PARABOLIC REFLECTOR	112
FRESNEL LENS	113
TROUGH CONCENTRATOR	113
BOX CONCENTRATOR	113
SOLAR CELL BATTERY CHARGERS	114
STORAGE BATTERY PRECAUTIONS	114
SOLAR CELL BATTERY CHARGER	116
MONITORING A SOLAR CHARGER	117
TAKE A SOLAR CELL INTO SPACE	118

SOLAR POWERED MOTORS	122
BASIC SOLAR POWERED MOTOR	122
HIGHER POWER SOLAR MOTOR	122
REVERSIBLE SOLAR MOTOR	123
SOLAR MOTOR WITH BATTERY BACKUP	123
SOLAR ACTUATED MOTORS	124
POWER FET ACTUATOR (1)	124
TRANSISTOR ACTUATOR	124
POWER FET ACTUATOR (2)	125
OP AMP-POWER FET ACTUATOR	125
SOLAR CELL LIGHT METERS	126
LIGHT METER (VOLTAGE TYPE)	126
LIGHT METER (CURRENT TYPE)	126
SOLAR CELL RADIOMETER	127
SUNLIGHT ACTUATED RELAY	128
LIGHT ACTUATED RELAY	129
BREAK-BEAM DETECTION	130
STEADY-STATE BREAK-BEAM SYSTEM	131
PULSED BREAK-BEAM SYSTEM	132
PULSED BREAK-BEAM TRANSMITTER	132
PULSED BREAK-BEAM RECEIVER	133
SUN POWERED TONE GENERATORS	134
SOLAR POWERED PIEZO BUZZER	134
SOLAR POWERED DUAL GATE OSCILLATOR	134
SOLAR POWERED 555 OSCILLATOR	135
SOLAR POWERED CLICKERS	135
LIGHT CONTROLLED TONE	136
LIGHT CONTROLLED 555 OSCILLATOR	136
HIGH-GAIN LIGHT CONTROLLED TONE	137
IR REMOTE CONTROL TESTERS	138
PIEZO AND MAGNETIC TESTERS	138
TRANSISTOR REMOTE CONTROL TESTER	139
OP AMP REMOTE CONTROL TESTER	139
SOLAR POWERED NIGHT LIGHT	140

I. SENSOR PROJECTS

OVERVIEW

ELECTRONIC SENSORS DETECT PRESSURE, HEAT, LIGHT, MAGNETIC FIELDS AND SO FORTH. THESE ARE AMONG THE SENSOR APPLICATIONS IN THIS MINI-NOTEBOOK. YOU CAN MAKE SOME SENSORS, AND MANY SENSORS AND SENSING SYSTEMS ARE AVAILABLE FROM RADIO SHACK STORES AND RADIO SHACK UNLIMITED.

DESIGN TIPS

1. THE UBIQUITOUS 741 OPERATIONAL AMPLIFIER IS USED IN THIS SECTION. OF COURSE YOU CAN SUBSTITUTE NEWER OP AMPS IF YOU DO NOT EXCEED THEIR MAXIMUM POWER SUPPLY VOLTAGE. BE SURE TO CHECK THE PIN OUTLINE.
2. UNLESS OTHERWISE SPECIFIED, USE $1/4$ OR $1/2$ WATT RESISTORS AND CAPACITORS RATED FOR AT LEAST THE POWER SUPPLY VOLTAGE. IF EXACT VALUES ARE UNAVAILABLE, YOU CAN USUALLY SUBSTITUTE VALUES WITHIN 10 TO 20 % OF THE SPECIFIED VALUE.
3. ALWAYS BUILD A TEST VERSION OF A CIRCUIT ON A SOLDERLESS BREADBOARD BEFORE MAKING A PERMANENT VERSION. THIS WILL ALLOW YOU TO MAKE MODIFICATIONS TO THE CIRCUIT.

SAFETY FIRST


1. POWER SENSOR CIRCUITS WITH BATTERIES.
2. DO-IT-YOURSELF SENSOR CIRCUITS ARE NOT APPROPRIATE FOR MEDICAL APPLICATIONS OR WHEN HUMAN LIFE OR SAFETY IS AT RISK.

ELECTRONIC SENSORS


AN ELECTRONIC SENSOR RESPONDS TO AN EXTERNAL STIMULUS SUCH AS LIGHT, SOUND, PRESSURE, VIBRATION OR TEMPERATURE. MOST SENSORS CAN BE PLACED IN ONE OF TWO CATEGORIES: SIMPLE GO-NO GO SENSORS THAT ACT MUCH LIKE AN ON-OFF SWITCH AND ANALOG SENSORS WHOSE OUTPUT IS PROPORTIONAL TO THE STIMULUS.

GO-NO GO SENSORS

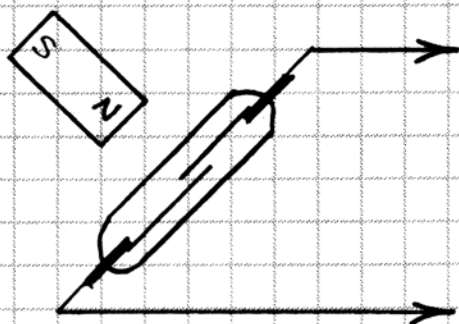GO-NO GO SENSORS ARE ALSO KNOWN AS ON-OFF, YES-NO OR BINARY SENSORS. SOME ARE SIMPLE MECHANICAL DEVICES SUCH AS MAGNETIC PROXIMITY SWITCHES AND VIBRATION SENSORS LIKE THOSE USED IN VARIOUS SECURITY SYSTEMS.



MAGNETIC REED SWITCH
(MAGNET SENSOR)

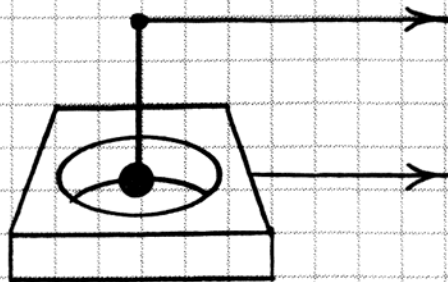

PENDULUM SWITCH
(VIBRATION SENSOR)

SOME GO-NO GO SENSORS INCLUDE AN ANALOG SENSOR AND A CIRCUIT THAT SWITCHES ON (OR OFF) WHEN THE AMPLITUDE OF WHAT IS BEING SENSED EXCEEDS (OR FALLS BELOW) A CERTAIN LEVEL. OFTEN THE POINT AT WHICH THE CIRCUIT SWITCHES CAN BE ADJUSTED BY ADDING OR CHANGING THE VALUE OF AN EXTERNAL RESISTOR OR BY A DIGITAL SWITCH ARRAY.

ANALOG SENSORS

MANY KINDS OF ANALOG SENSORS ARE READILY AVAILABLE. SOME OF THE MOST COMMON ARE DESCRIBED HERE.


PHOTORESISTOR

LIGHT-SENSITIVE RESISTOR WHOSE RESISTANCE CHANGES WITH LIGHT.



PHOTODIODE

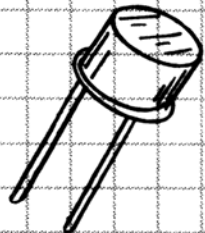LIGHT-SENSITIVE DIODE WHICH PRODUCES A CURRENT IN RESPONSE TO LIGHT.




THERMISTOR

TEMPERATURE-SENSITIVE RESISTOR WHOSE RESISTANCE CHANGES WITH TEMPERATURE.



MICROPHONE

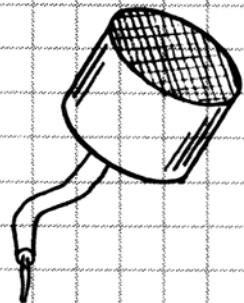SOUND-SENSITIVE SENSOR WHICH PRODUCES A VOLTAGE OR CHANGES A CAPACITANCE AS THE SOUND LEVEL CHANGES.




PIEZOELECTRIC

VARIOUS CRYSTALS OR CERAMICS WHICH PRODUCE A VOLTAGE WHEN BENT, VIBRATED OR SUBJECTED TO MECHANICAL SHOCK.




BASIC SENSOR CIRCUITS

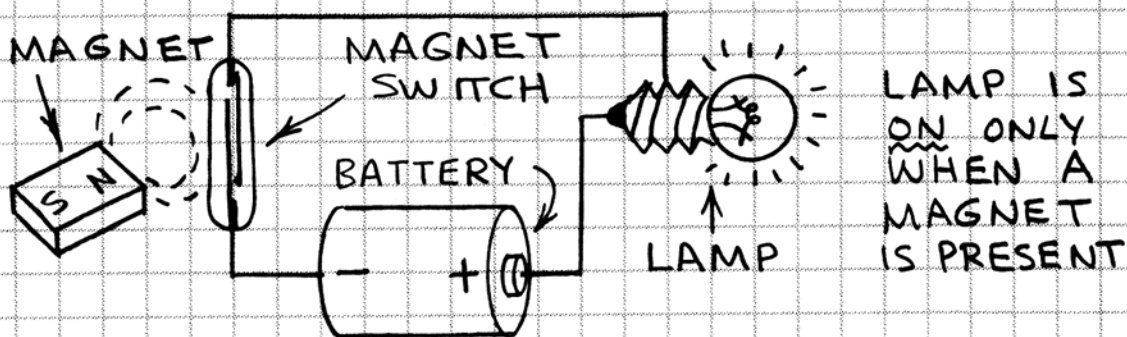
ELECTRONIC SENSORS REQUIRE A DEVICE THAT INDICATES WHEN SOMETHING HAS BEEN SENSED. THE INDICATOR FOR A SIMPLE GO-NO GO SENSOR SUCH AS A MAGNET SWITCH CAN BE A LAMP, LED OR BUZZER.



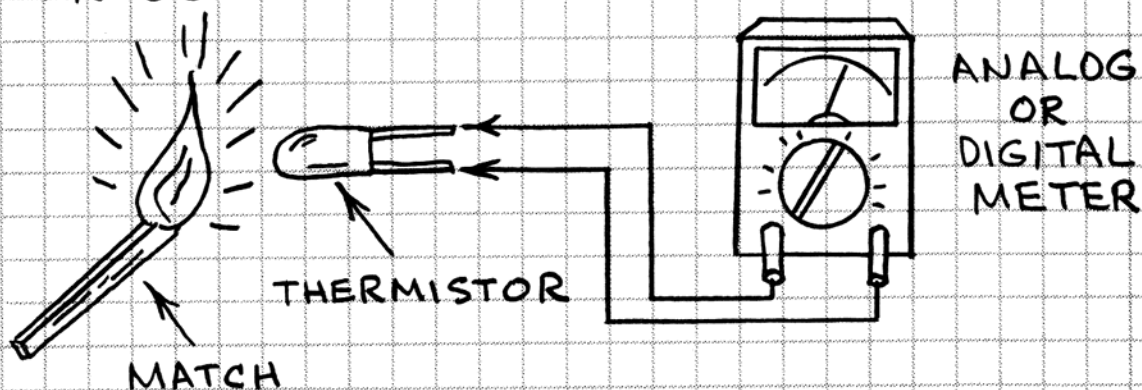THE OUTPUT DEVICE FOR AN ANALOG SENSOR CAN BE AN ANALOG OR DIGITAL METER, AN OSCILLOSCOPE OR A COMPUTER.




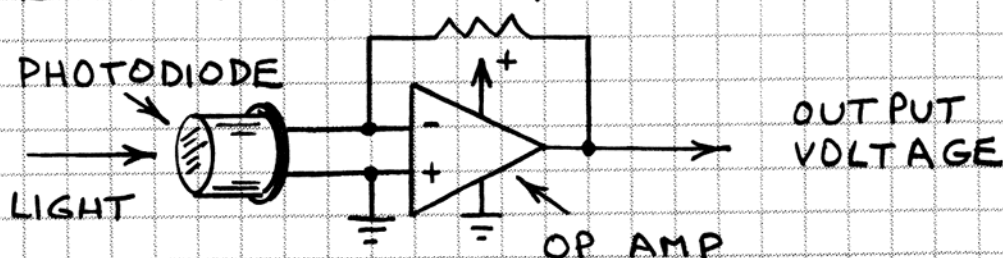MANY ANALOG SENSORS REQUIRE A CIRCUIT TO PREPARE THE SIGNAL FOR AN OUTPUT INDICATOR. AN ESPECIALLY USEFUL CIRCUIT IS THE OPERATIONAL AMPLIFIER (OP AMP). THE OP AMP CAN TRANSFORM THE TINY CURRENT FROM A PHOTODIODE INTO A VOLTAGE THAT IS EASILY INDICATED BY A METER.




SENSORS AND COMPUTERS

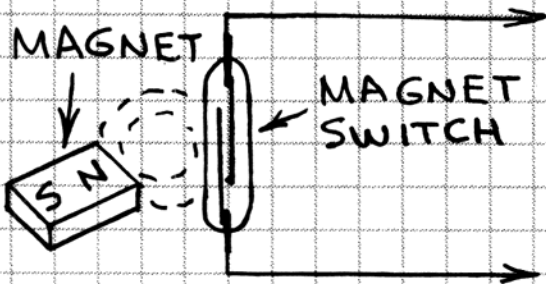GO-NO GO SENSORS CAN BE EASILY CONNECTED TO COMPUTERS AND DIGITAL CIRCUITS.




TO COMPUTER
MOUSE SWITCH,
JOYSTICK SWITCH
OR PARALLEL PORT.

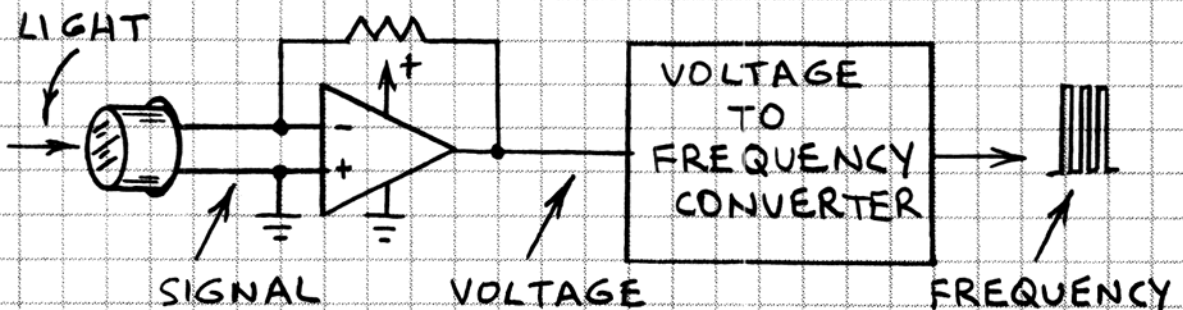ANALOG SENSORS REQUIRE A CIRCUIT THAT TRANSFORMS THE SIGNAL FROM THE SENSOR INTO DIGITAL FORM THAT A COMPUTER CAN UNDERSTAND. ONE APPROACH IS TO CHANGE THE SIGNAL INTO A STRING OF PULSES WHOSE FREQUENCY IS PROPORTIONAL TO THE AMPLITUDE OF THE SIGNAL. THE COMPUTER IS THEN PROGRAMMED TO COUNT THE PULSES DURING A GIVEN TIME.



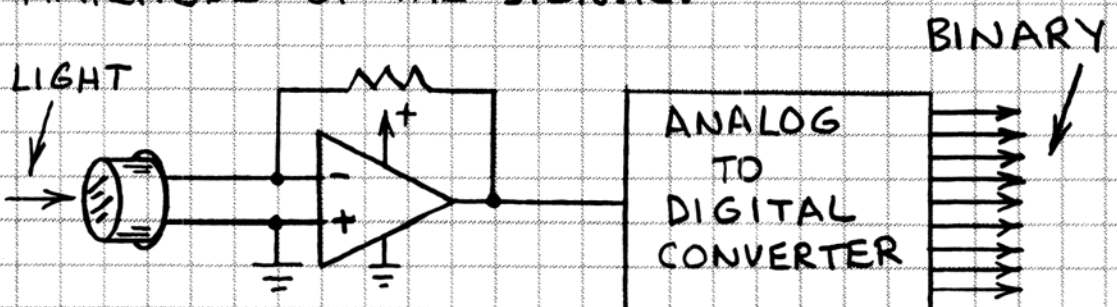
AN ANALOG-TO-DIGITAL CONVERTER (A/D CONVERTER) CHANGES A SIGNAL FROM A SENSOR INTO A BINARY NUMBER PROPORTIONAL TO THE AMPLITUDE OF THE SIGNAL.



TOUCH SWITCHES

USE A STANDARD SWITCH WHEN POSSIBLE.
FOR SPECIAL APPLICATIONS OR FOR ULTRA-THIN SWITCHES TRY THESE SWITCHES.

MULTI-LAYER SWITCH

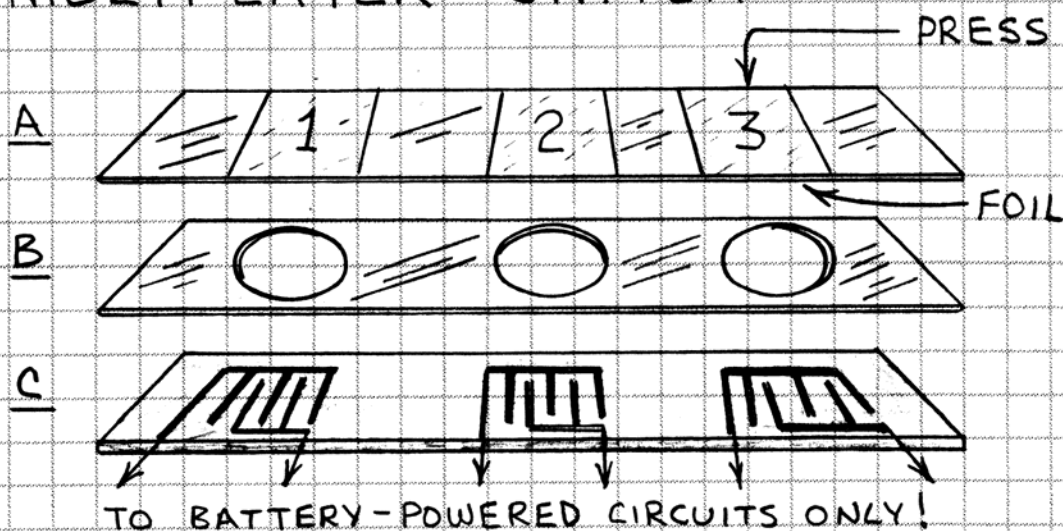


A - OVERHEAD TRANSPARENCY FILM WITH ALUMINUM FOIL SQUARES ATTACHED TO LOWER SIDE WITH CEMENT OR DOUBLE-SIDED TAPE.

B - SAME MATERIAL AS A WITH A HOLE PUNCHED AT EACH SWITCH POSITION.


C - MAKE ETCHED CIRCUIT BOARD AS SHOWN OR POSITION SWITCH ELEMENTS OVER FOIL PATTERN IN A PRE-ETCHED BOARD.

TACTILE FEEDBACK SWITCH

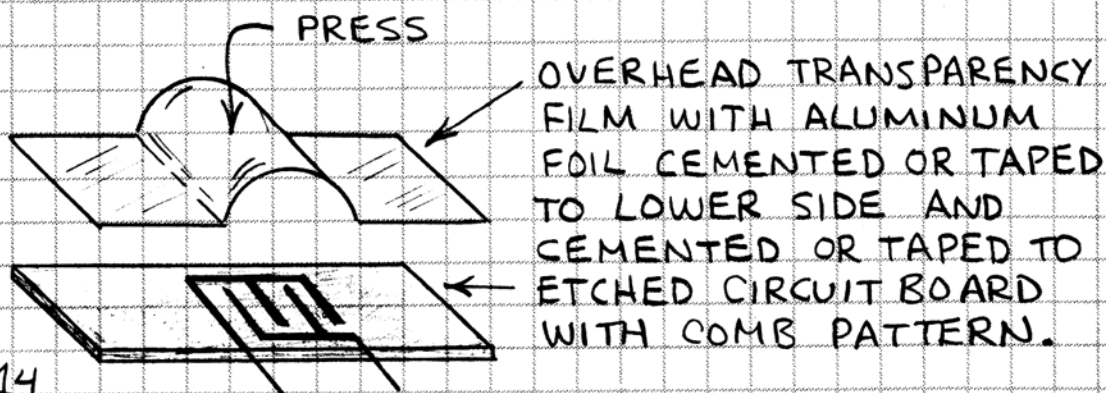

WHISKER-STYLE LEVER SWITCH

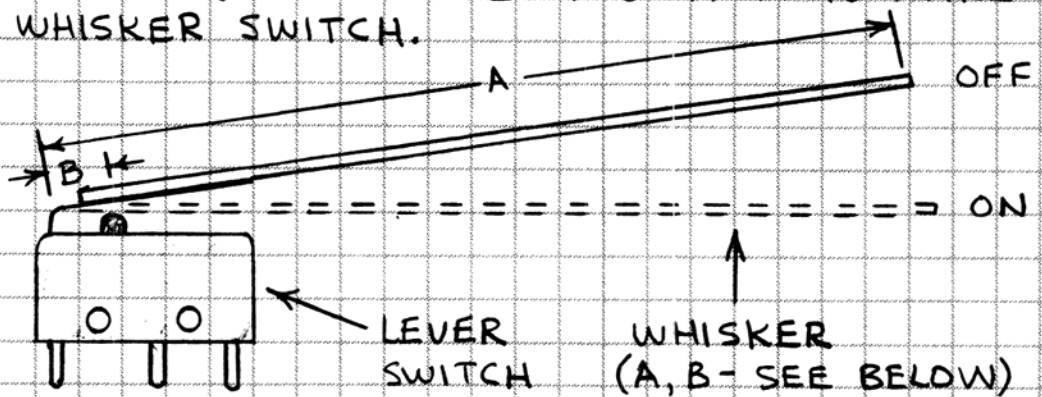ATTACH STIFF PLASTIC ROD OR MUSIC WIRE TO MOVABLE LEVER ON A LEVER SWITCH TO MAKE A WHISKER SWITCH.



WHISKER SWITCH APPLICATIONS:


ROBOTICS - SENSE PRESENCE OF OBJECTS.

INDUSTRY - HANG WHISKER OVER CONVEYOR BELT TO DETECT CARTONS AND OBJECTS PASSING BY.

RESEARCH - DRAG WHISKER OVER SOIL OR GRASS TO DETECT AND COUNT ROCKS AND PLANTS.

PHYSICS OF LEVER SWITCHES

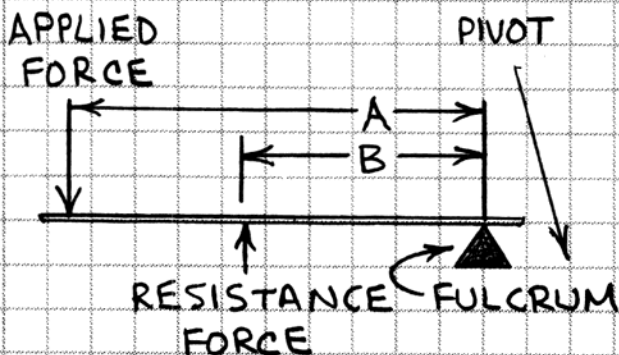THE WHISKER SWITCH IS A SECOND CLASS LEVER.



FOR AN IDEAL LEVER
 $\text{APPLIED FORCE} \times A =$
 $\text{RESISTANCE FORCE} \times B$

RESULTS BELOW
FROM POSTAGE SCALE
AND RULER TAPED TO
SWITCH LEVER. RULER
WAS PRESSED AGAINST
SCALE PLATFORM.


A (cm)	FORCE (grams)
2	49.6
5	22.7
10	11.3
15	7.1

1 OUNCE = 28.35 GRAMS


PUFF SWITCH

A PUFF SWITCH IS CLOSED BY AIR PRESSURE OR SIMPLY BY BLOWING INTO A TUBE. PUFF SWITCHES ARE EXPENSIVE AND HARD TO FIND, BUT YOU CAN EASILY MAKE THEM. OF THE VARIOUS KINDS I HAVE MADE THE TYPE SHOWN HERE IS THE MOST RELIABLE.

PRINCIPLE OF OPERATION:

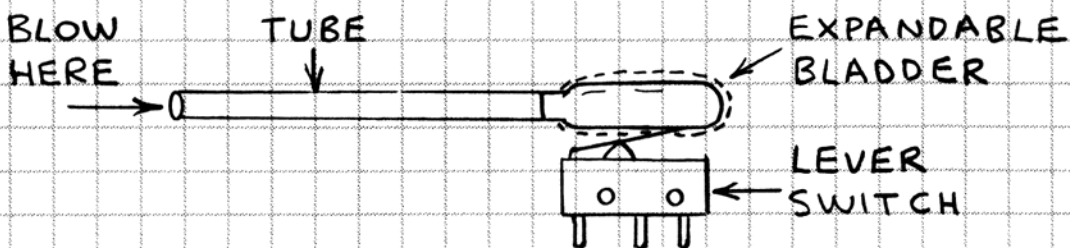


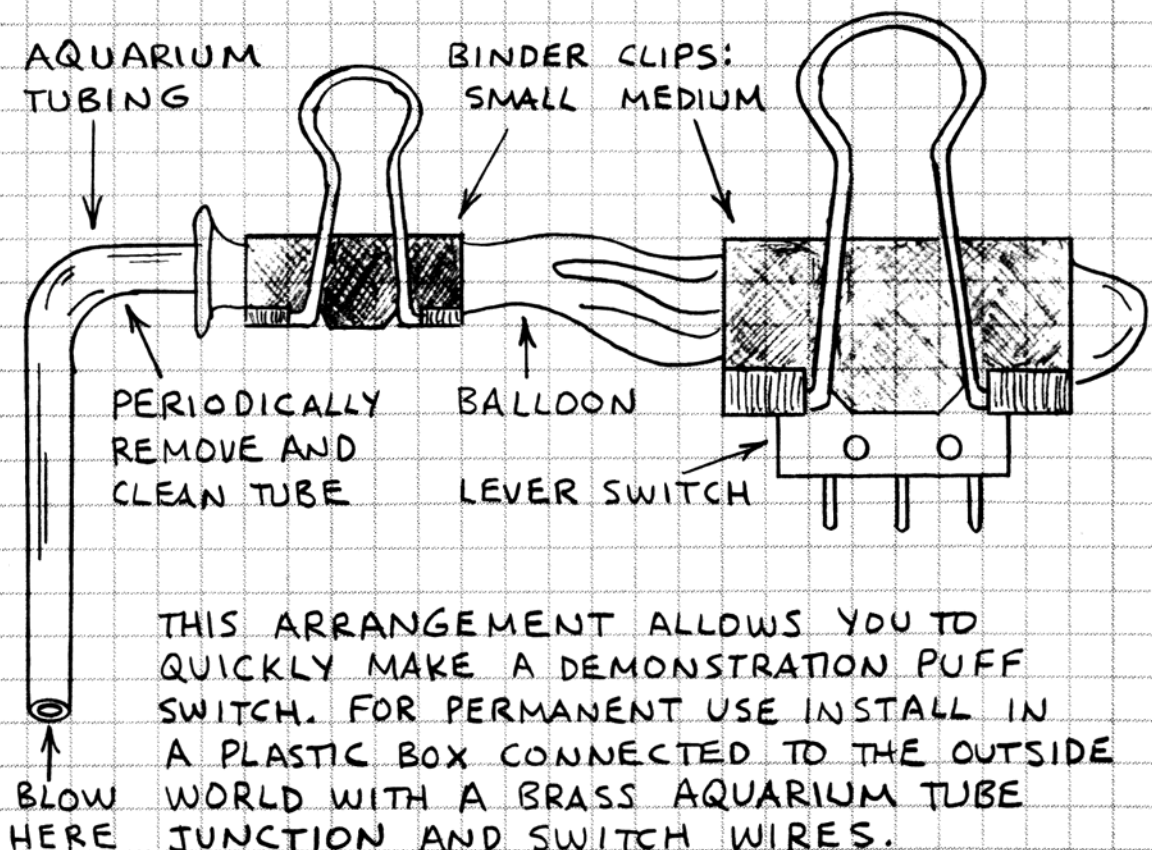MOISTURE IN YOUR BREATH WILL CONDENSE INSIDE THE TUBE AND CAUSE A SWITCH MECHANISM TO CORRODE OR STICK. THIS METHOD KEEPS MOISTURE AWAY FROM THE SWITCH. BELOW IS A DEMONSTRATION SWITCH WHICH CAN FORM THE BASIS OF A WORKING PUFF SWITCH.




THIS ARRANGEMENT ALLOWS YOU TO QUICKLY MAKE A DEMONSTRATION PUFF SWITCH. FOR PERMANENT USE INSTALL IN A PLASTIC BOX CONNECTED TO THE OUTSIDE WORLD WITH A BRASS AQUARIUM TUBE JUNCTION AND SWITCH WIRES.


PAPER CLIP SWITCH

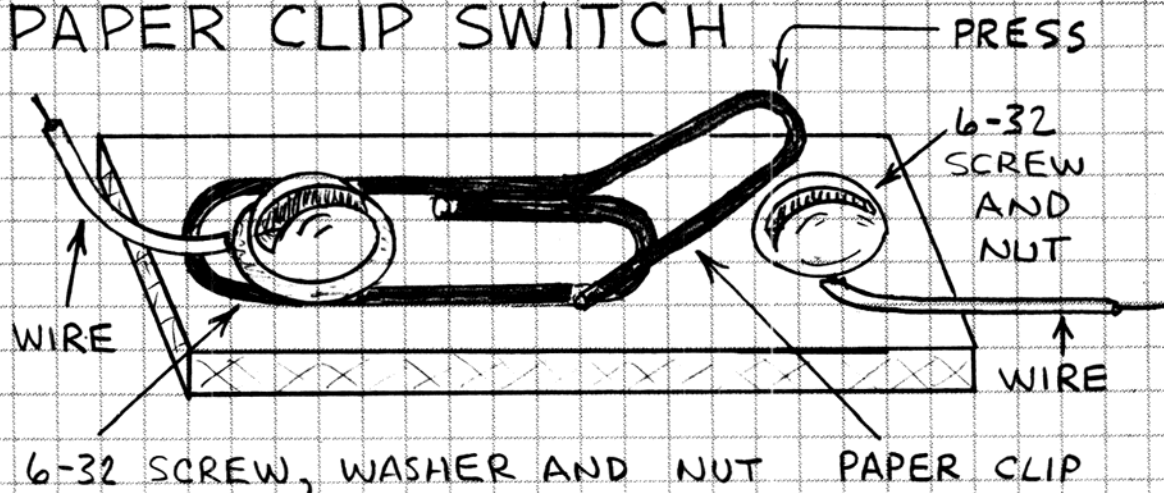


PHONE PLUG SWITCH

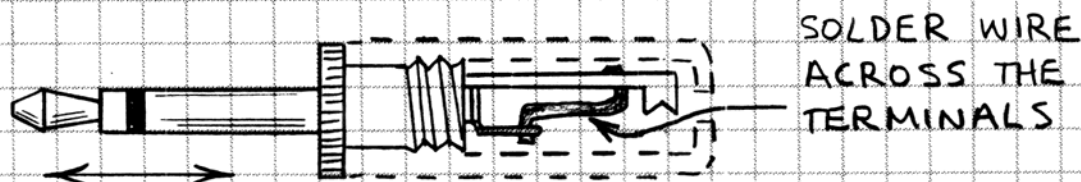

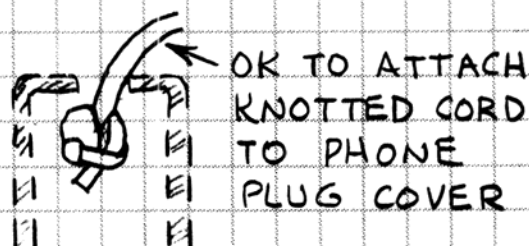INSERT PLUG IN JACK
TO CLOSE SWITCH.
PULL PLUG FROM JACK
TO OPEN SWITCH.



TILT SWITCH

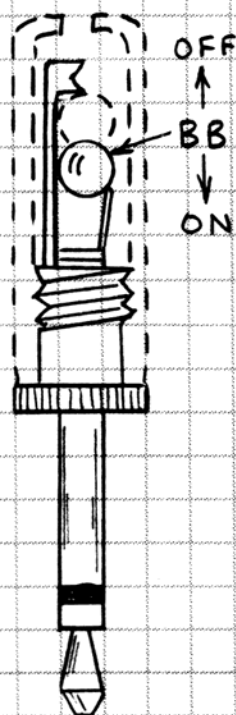


THIS SWITCH CLOSSES WHEN A STEEL AIR GUN SHOT (BB) ROLLS AGAINST THE TERMINALS IN A 1/8-INCH PHONE PLUG. INVERT PHONE PLUG TO OPEN SWITCH.

PROTOTYPE USED ZINC-PLATED, 4.5 mm BB COATED WITH A LAYER OF PROTECTIVE LACQUER WHICH DOES NOT CONDUCT ELECTRICITY. THEREFORE I PLACED BB IN SMALL HOLE BORED IN WOOD, MELTED SOLDER OVER IT AND PUSHED BB FROM HOLE WITH SOLDERING IRON. (BB WAS HOT!)

MUSIC WIRE VIBRATION SENSOR

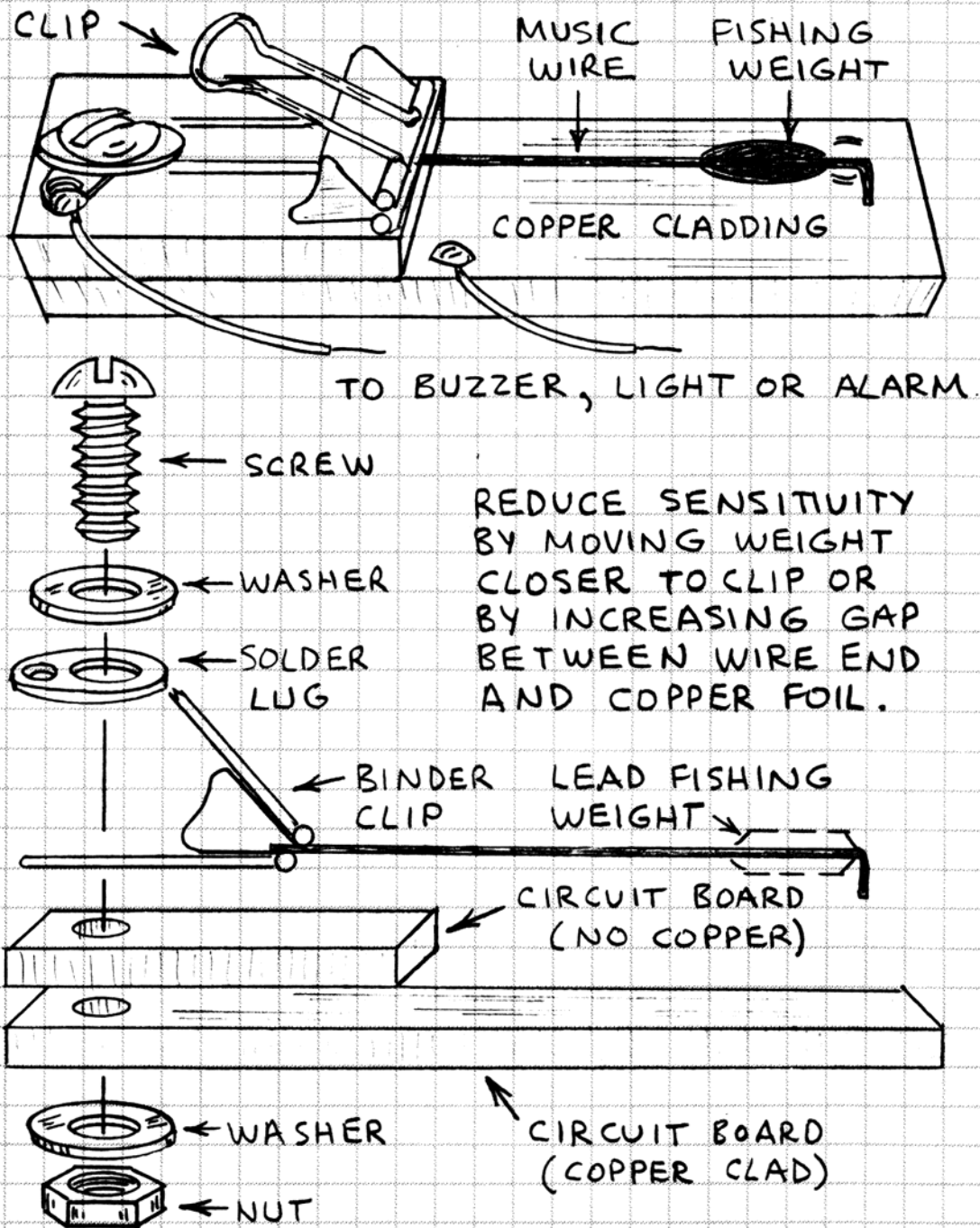
MUSIC WIRE (AVAILABLE FROM HOBBY AND CRAFT STORES) IS STIFF STEEL WIRE THAT SPRINGS BACK TO ITS ORIGINAL POSITION AFTER BEING BENT GENTLY. MUSIC WIRE CAN BE USED TO MAKE MANY KINDS OF TILT AND VIBRATION SWITCHES THAT WORK IN VARIOUS POSITIONS. CAUTION: USE DO-IT-YOURSELF SENSOR LIKE THIS ONLY FOR BATTERY-POWERED APPLICATIONS!



HARDWARE: 6-32 OR 8-24


PIEZOELECTRIC VIBRATION SENSOR

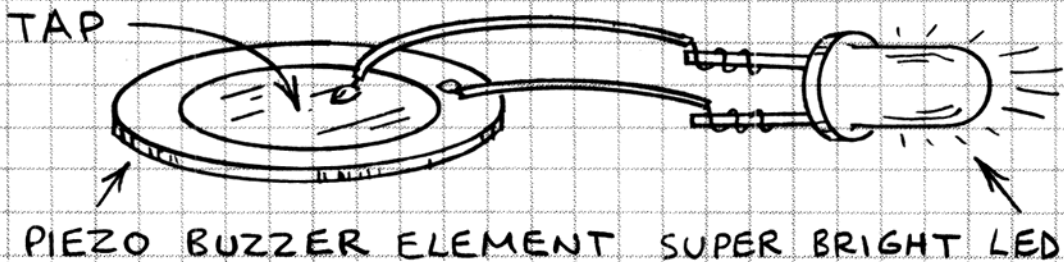CERTAIN CRYSTALS AND CERAMICS BEND IN RESPONSE TO A VOLTAGE AND GENERATE A VOLTAGE WHEN BENT. THIS PROPERTY IS THE PIEZOELECTRIC EFFECT. A PIEZOELECTRIC BUZZER ELEMENT IS A SENSITIVE VIBRATION SENSOR. TRY THIS:




TAP THE PIEZO ELEMENT WITH A PENCIL WHILE LOOKING INTO THE END OF THE LED. EACH TAP WILL CAUSE THE LED TO FLASH.

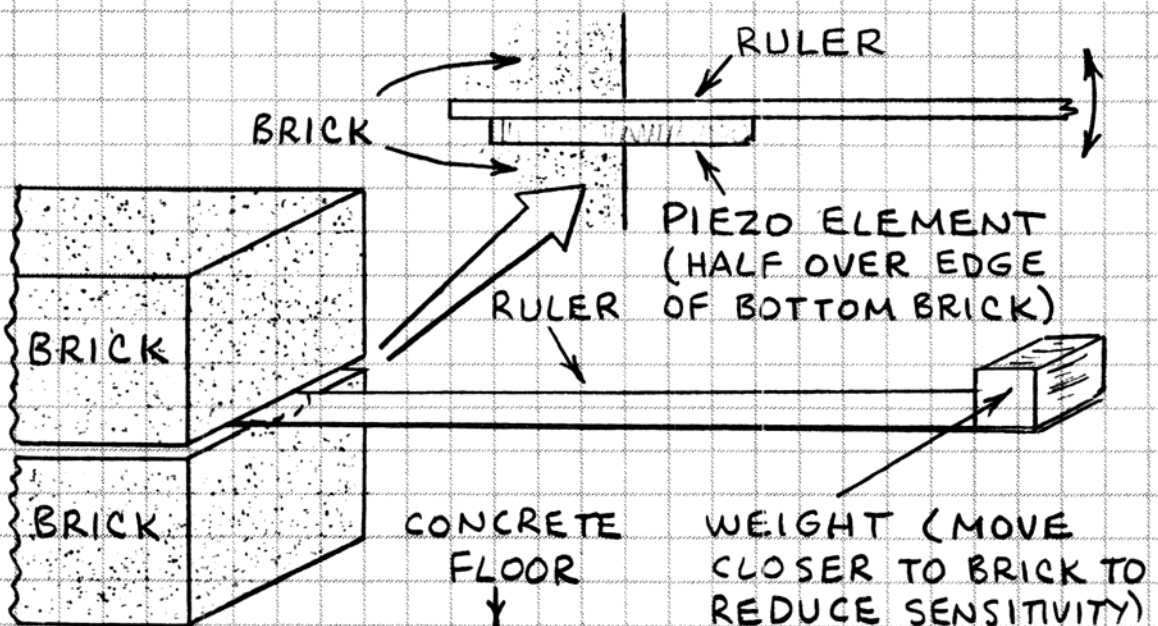THE SETUP BELOW IS A SEISMIC SENSOR. THE VERSION I MADE DETECTED TRAINS 1 MILE (1.6 KM) AWAY. CONNECT THE LEADS FROM THE PIEZO ELEMENT TO AN ANALOG VOLT METER. SEISMIC VIBRATIONS WILL CAUSE THE NEEDLE TO JUMP UP TO A VOLT OR SO. THE WEIGHT CAN BE A LEAD FISHING WEIGHT OR A 9-VOLT BATTERY.



PENDULUM SWITCH

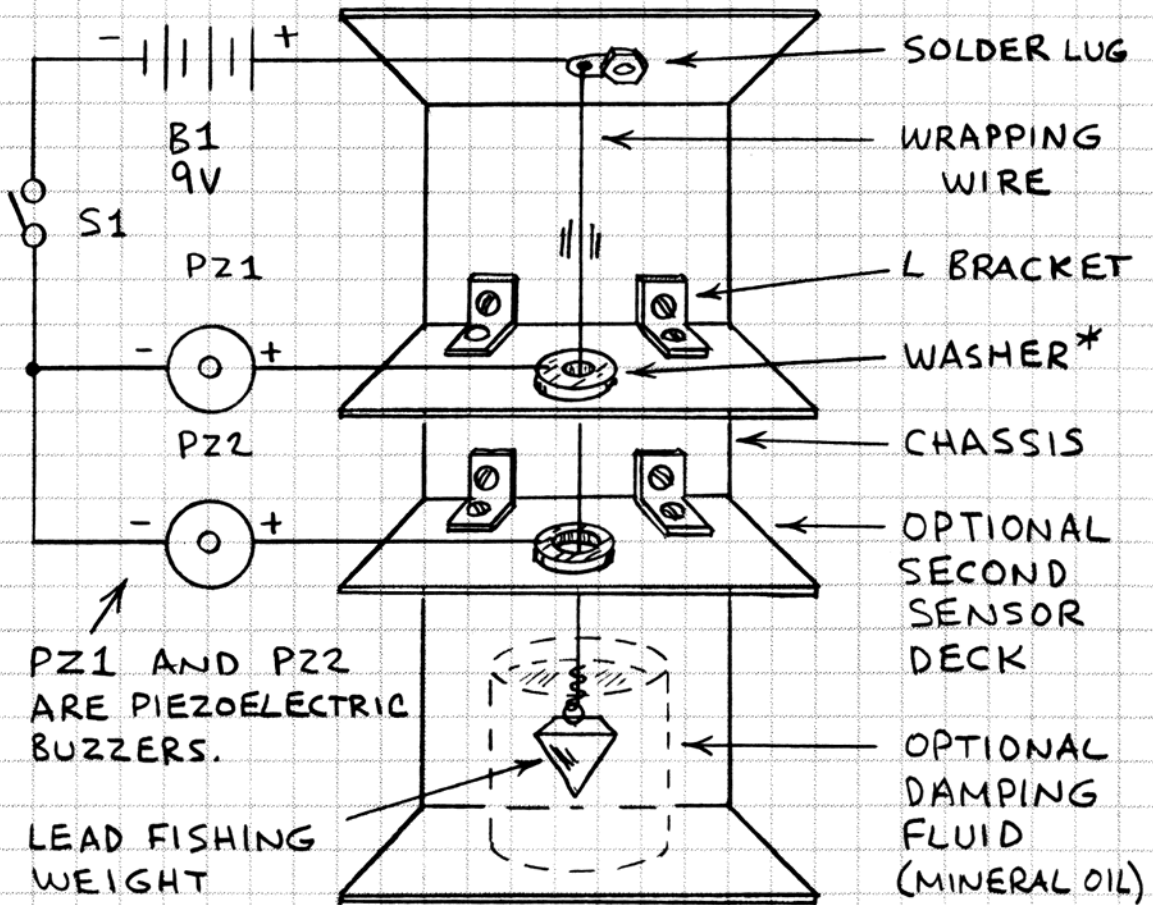PENDULUM SWITCHES ARE IDEAL FOR DETECTING TILT AND VIBRATION. THEY ARE USED IN SECURITY SYSTEMS AND SEISMIC SENSORS. PENDULUM SWITCHES ARE EASILY MADE FROM READILY AVAILABLE MATERIALS. HERE'S ONE YOU CAN MAKE.




*WASHER—USE TINNED WASHER. SOLDER A WIRE TO WASHER. CEMENT WASHER OVER HOLE DRILLED IN THE SENSOR DECK.

CHASSIS IS PLASTIC OR METAL ENCLOSURE. SENSOR DECK IS CIRCUIT BOARD MATERIAL (WITHOUT COPPER FOIL). SECOND SENSOR DECK HAS WASHER WITH LARGER HOLE THAN WASHER IN UPPER DECK. THIS PROVIDES A SECOND SIGNAL AS TILT OR VIBRATION IS INCREASED.

PENDULUM QUADRANT SWITCH

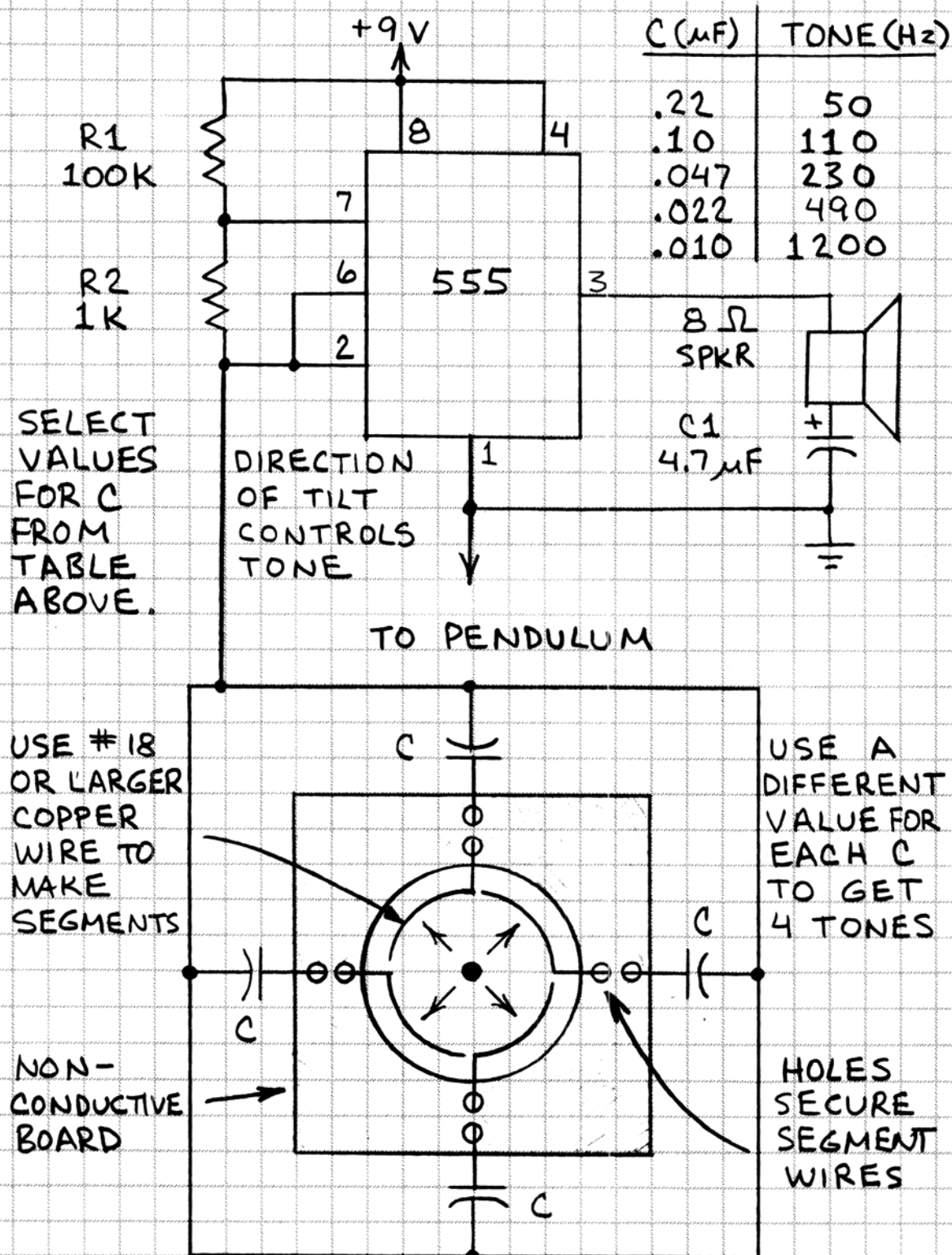
REPLACE THE SIMPLE GO-NO GO WASHER SWITCH ON THE FACING PAGE WITH A CIRCULAR ARRAY OF FOUR OR MORE SEGMENTS AND YOU CAN MAKE A SWITCH WHICH INDICATES THE DIRECTION OF TILT OR VIBRATION.




SWITCH-TYPE ALARM SYSTEMS

MANY SECURITY ALARM SYSTEMS USE ON-OFF (SPST) SWITCHES TO DETECT OPEN DOORS AND WINDOWS OR VIBRATION. MAGNET SWITCHES, METAL FOIL (WHICH BREAKS WHEN A WINDOW IS BROKEN) AND VIBRATION SENSORS ARE OFTEN USED.

TYPICAL MAGNET SWITCH

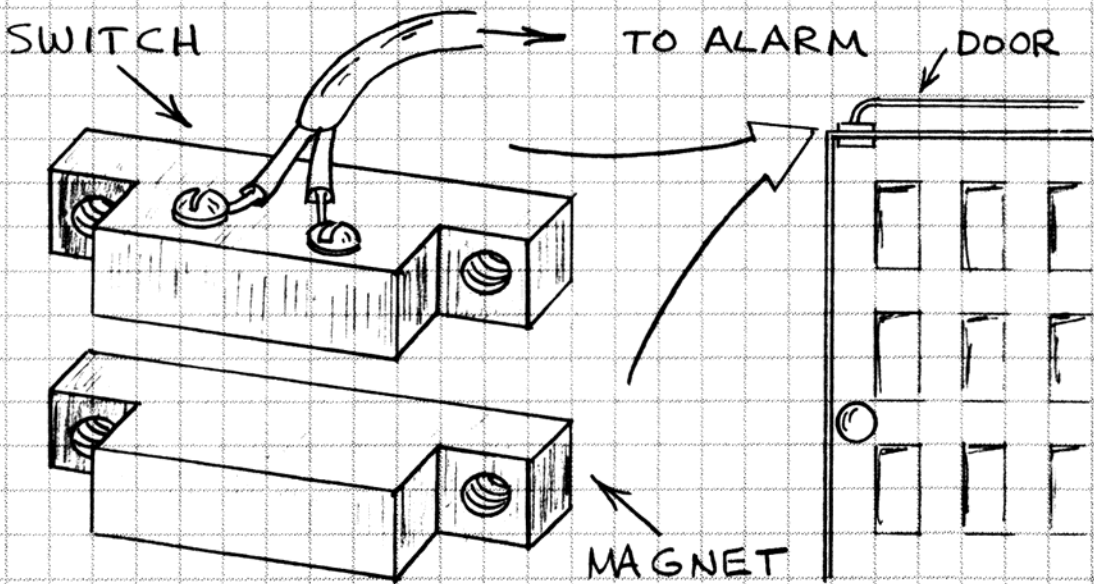


BASIC OPEN-CIRCUIT ALARM

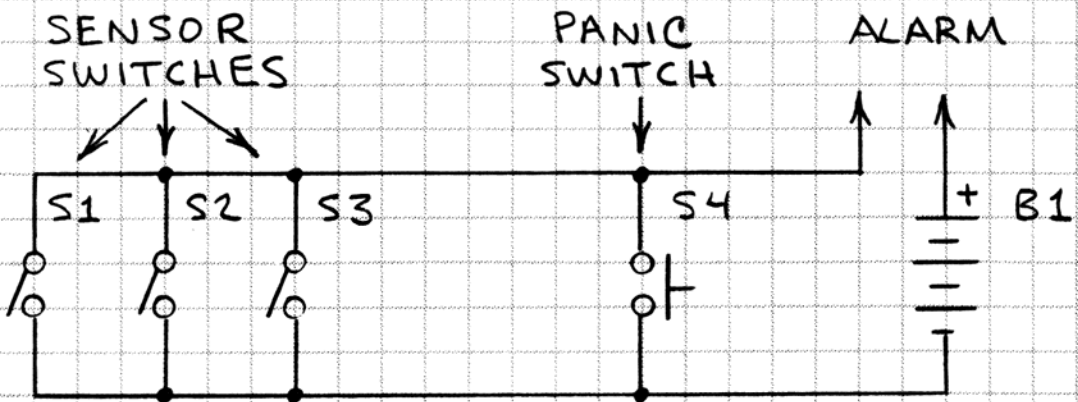

ALARM (BELL, SIREN, BUZZER OR LAMP) IS ACTIVATED WHEN A SWITCH CLOSSES. BUT THIS CIRCUIT IS EASILY DEFEATED SIMPLY BY CUTTING A WIRE.


IMPROVED OPEN-CIRCUIT ALARM

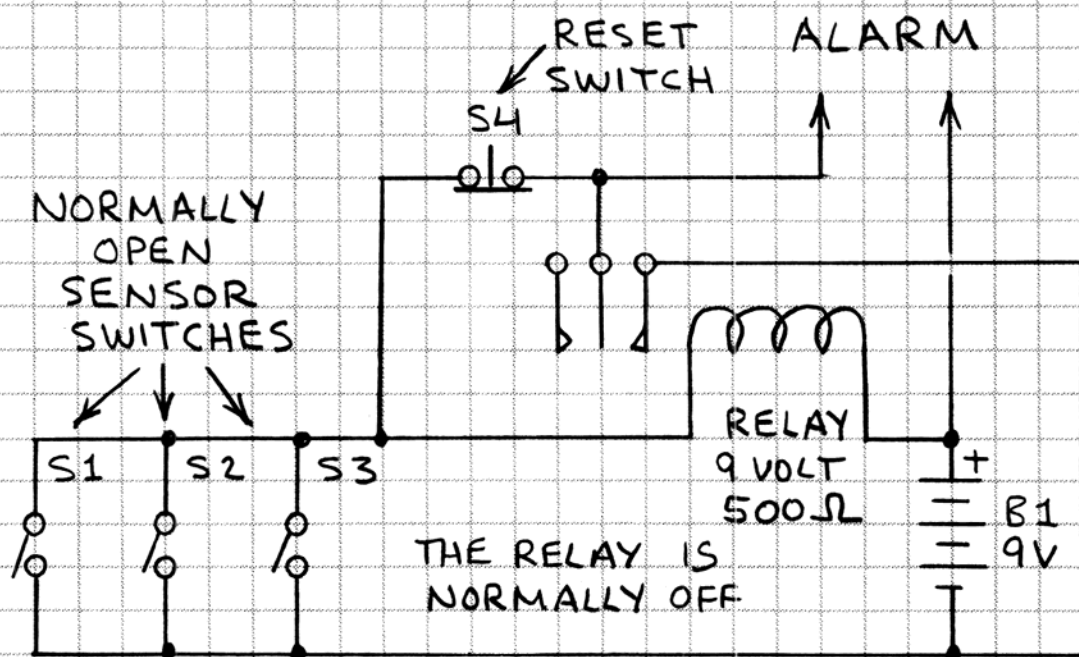

WHEN A SENSOR SWITCH IS CLOSED THE RELAY PULLS IN AND THE ALARM STAYS ON UNTIL THE RESET SWITCH IS OPENED. THE CIRCUIT CAN BE DEFEATED BY CUTTING A SWITCH WIRE BEFORE CLOSING A SENSOR.


CLOSED-CIRCUIT ALARM

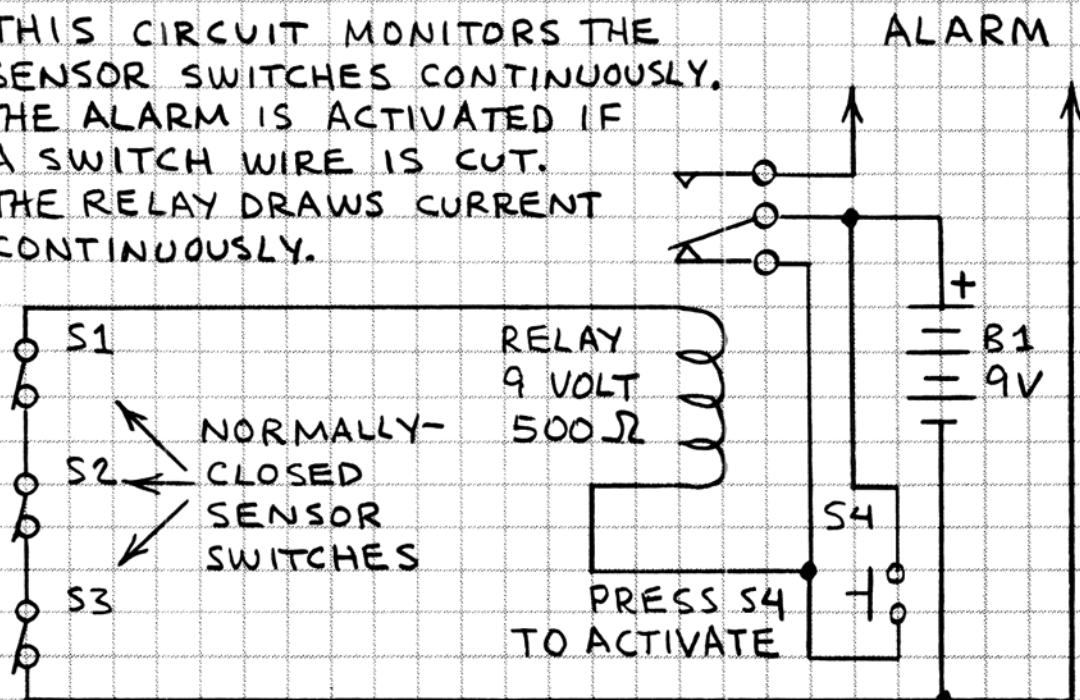THIS CIRCUIT MONITORS THE SENSOR SWITCHES CONTINUOUSLY. THE ALARM IS ACTIVATED IF A SWITCH WIRE IS CUT. THE RELAY DRAWS CURRENT CONTINUOUSLY.




INTELLIGENT SWITCH SENSOR

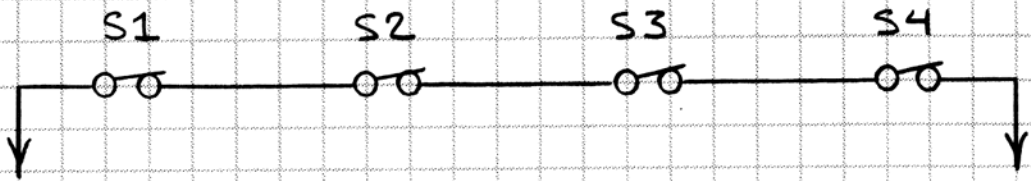WIRED SECURITY SYSTEMS ARE MORE SECURE WHEN THE SENSOR SWITCHES ARE NORMALLY-CLOSED AND CONNECTED IN SERIES LIKE THIS:



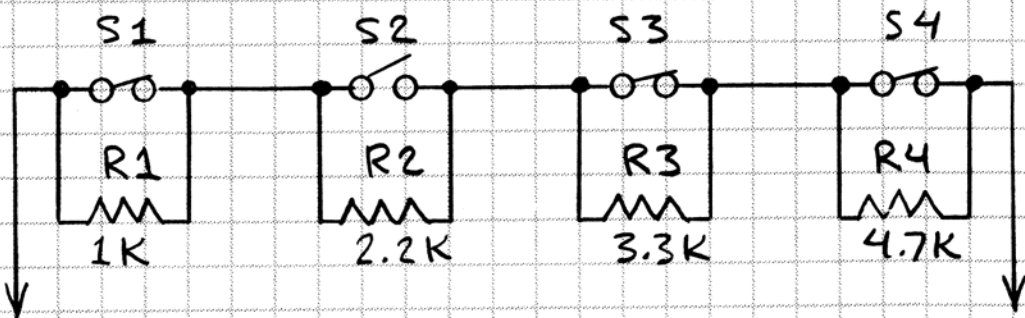WHEN A SWITCH IS OPENED AN ALARM SOUNDS OR A LAMP FLASHES ON. BUT THE CIRCUIT DOES NOT INDICATE WHICH SWITCH IS OPEN. THIS CIRCUIT DOES:




NORMALLY THE OUTPUT IS CLOSE TO 0 OHM. WHEN A SWITCH IS OPENED, A CORRESPONDING RESISTANCE APPEARS AT THE OUTPUT. WITH THE RESISTANCES ABOVE, IF THE OUTPUT IS 2.2K THEN S2 IS OPEN. THIS METHOD ALSO INDICATES WHICH OF TWO OR MORE SWITCHES ARE OPEN. WITH THE VALUES ABOVE, IF THE OUTPUT IS 5.5K, THEN SWITCHES 2 AND 3 ARE OPEN.

IMPORTANT TIPS

USE GREAT CARE WHEN DESIGNING AND INSTALLING SECURITY ALARM SYSTEMS. BE SURE BATTERIES ARE FRESH AND TEST THE SYSTEM OFTEN.

INTELLIGENT SECURITY ALARM

S1-S5: NORMALLY CLOSED MAGNET SWITCHES

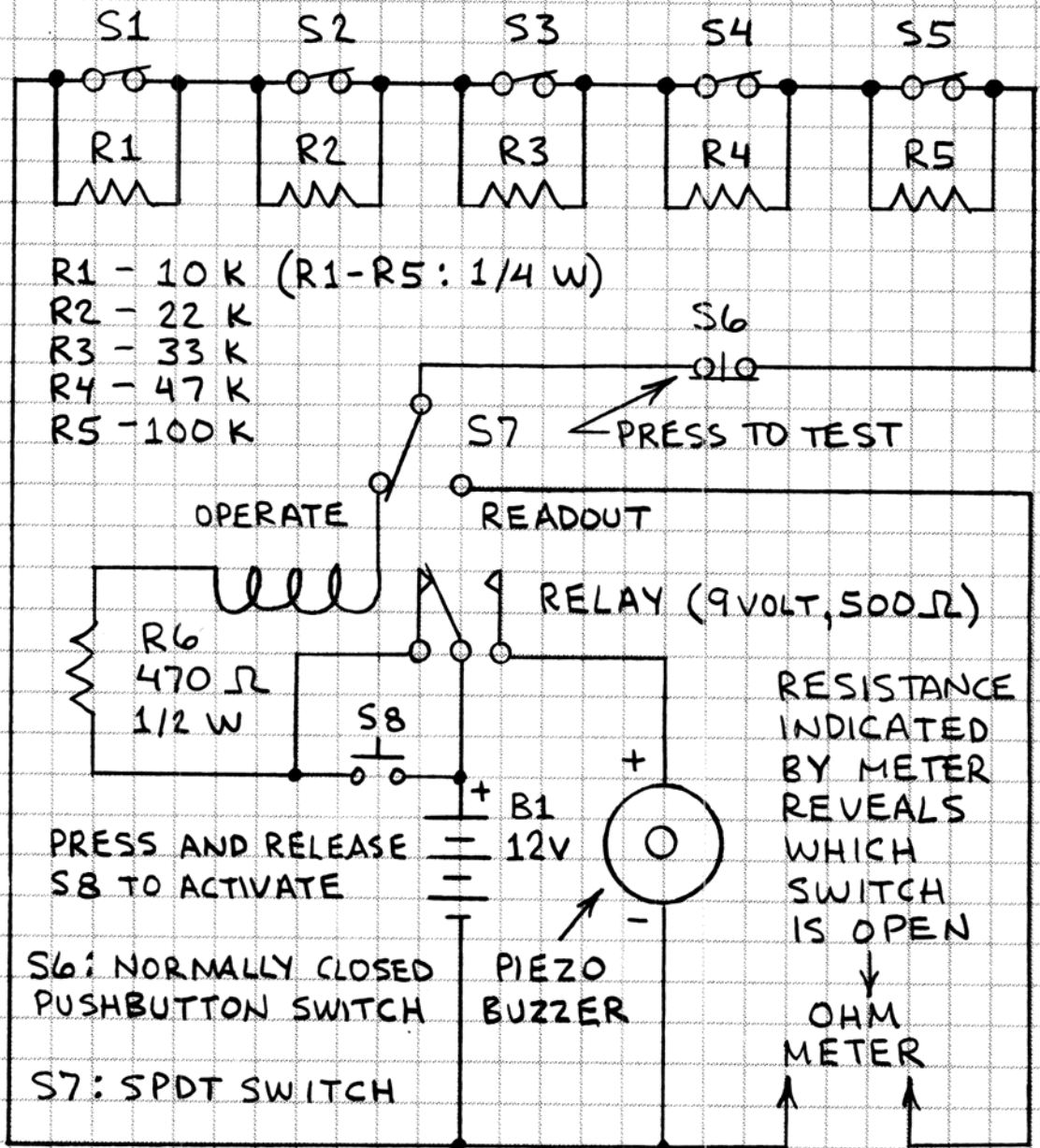

OPERATION:


1. PRESS S6 TO TEST. (BUZZER WILL SOUND.)
2. IF ALARM SOUNDS, TOGGLE S7 TO THE READOUT POSITION TO SILENCE BUZZER. THEN SWITCH ON OHM METER AND READ THE RESISTANCE. IF RESISTANCE IS ONLY A FEW OHMS, THE BATTERY IS TOO WEAK TO PULL IN THE RELAY.

FIRE OR WATER SENSOR

THIS NORMALLY-CLOSED SWITCH IS KEPT CLOSED BY A SUBSTANCE THAT MELTS WHEN HOT OR DISSOLVES WHEN WET. FOR SAFETY THE SWITCH OPENS IF IT IS DESTROYED.


FIRE: PLACE SECTION OF BIRTHDAY CANDLE IN SENSOR GAP. SWITCH WILL OPEN WHEN WAX MELTS OR IF CLOTHES PIN BURNS AWAY.

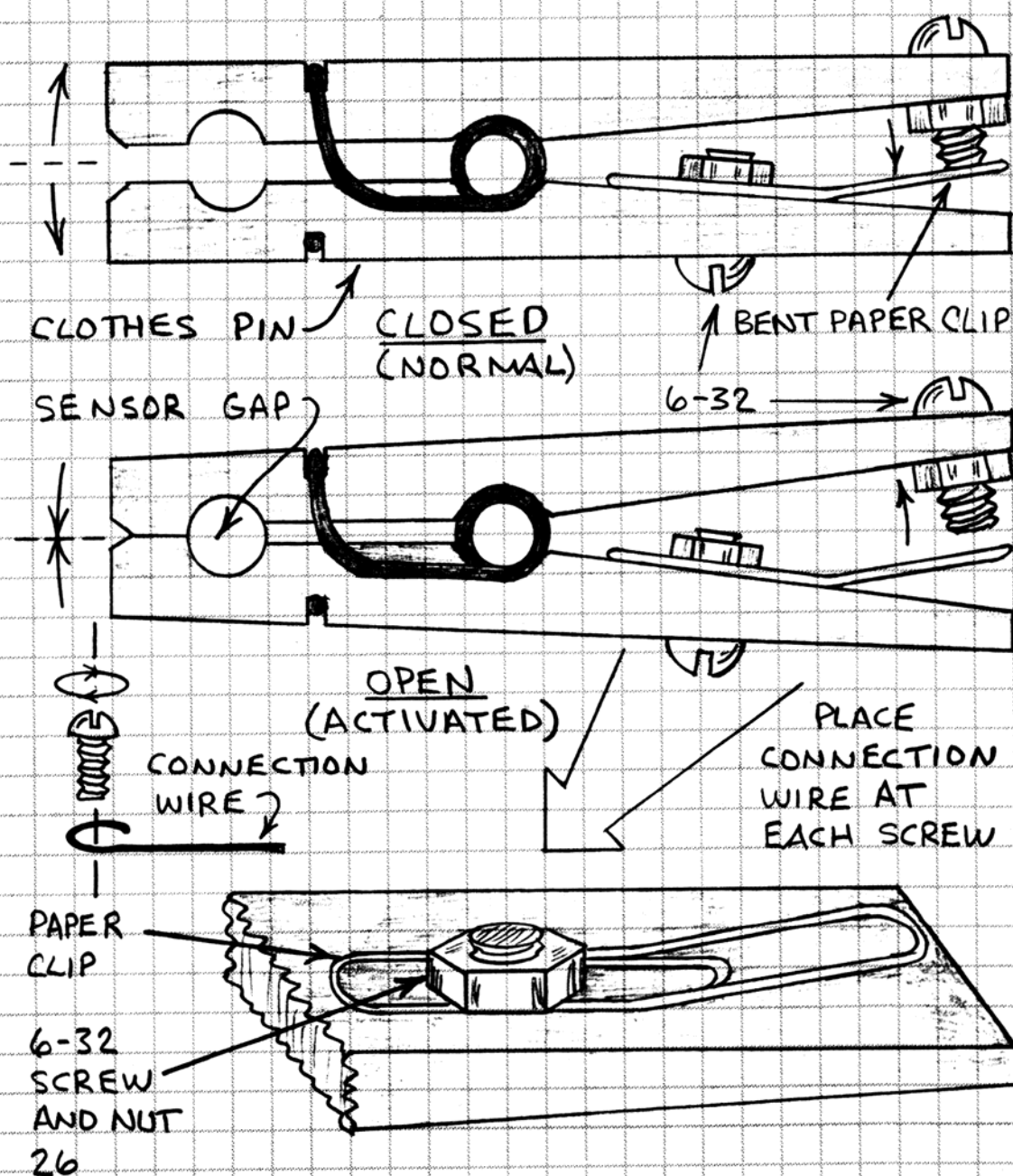WATER: PLACE ASPIRIN OR OTHER WATER SOLUBLE TABLET OR CAPSULE IN SENSOR GAP.



PULL SWITCH


USE THIS SWITCH TO ACTIVATE A LIGHT, SIREN OR BUZZER WHEN A DOOR, WINDOW OR MAIL BOX IS OPENED. THE VERSION SHOWN HERE IS NORMALLY OPEN. THIS MEANS THE SWITCH CAN BE BYPASSED BY CUTTING ITS LEADS. FOR NORMALLY CLOSED OPERATION USE THE SWITCH ON FACING PAGE AND ADJUST SCREW SO THAT IT TOUCHES THE PAPER CLIP WHEN THE PULL STRIP IS IN PLACE. A THICKER PULL STRIP MIGHT BE NECESSARY IF YOU USE THE NORMALLY CLOSED SWITCH. USE SCREWS OR CEMENT TO MOUNT SWITCH.

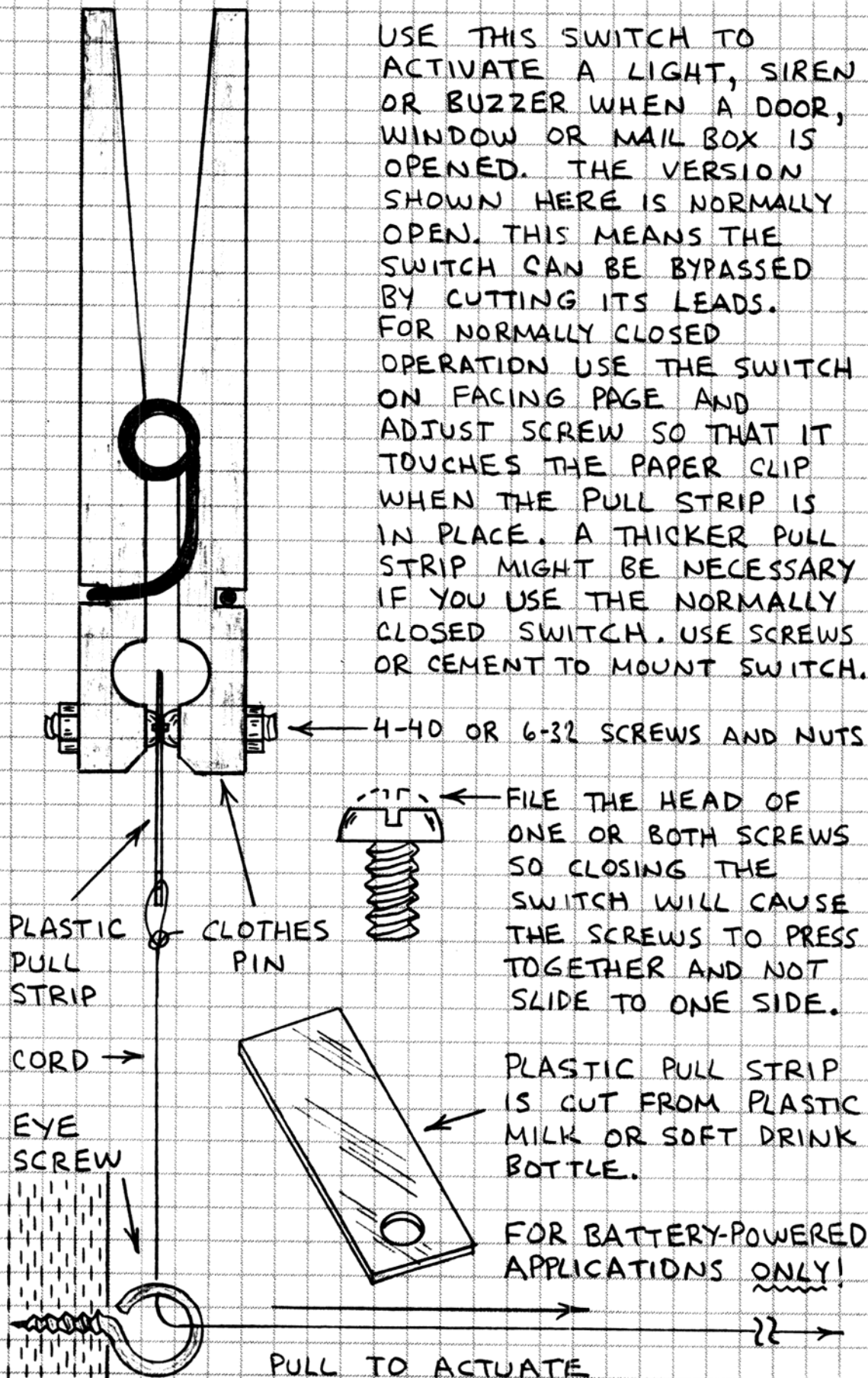

VOLTAGE SENSORS

GO-NOGO VOLTAGE SENSORS HAVE MANY USEFUL APPLICATIONS. THEY CAN BE MADE USING ZENER DIODES OR COMPARATORS.

ZENER DIODE VOLTAGE SENSOR

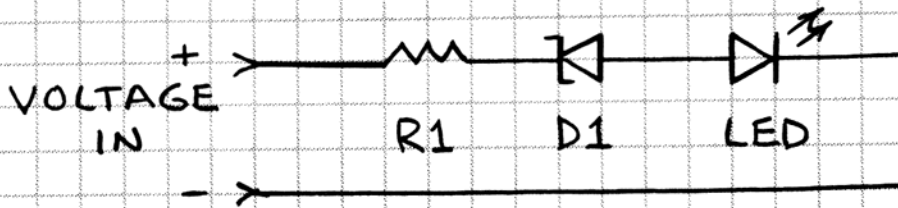


LED WILL GLOW WHEN INPUT VOLTAGE EXCEEDS BREAKDOWN VOLTAGE OF D1.

$$R1 = (\text{VOLTAGE IN} - V_{LED}) / I_{LED}$$

V_{LED} RANGES FROM ABOUT 2.0 TO 2.7 VOLTS FOR VISIBLE LEDs (SEE LED SPECIFICATIONS).

I_{LED} IS DESIRED CURRENT THROUGH LED. FOR 10 mA CURRENT, I_{LED} IS 0.01.


BARGRAPH VOLTAGE SENSOR

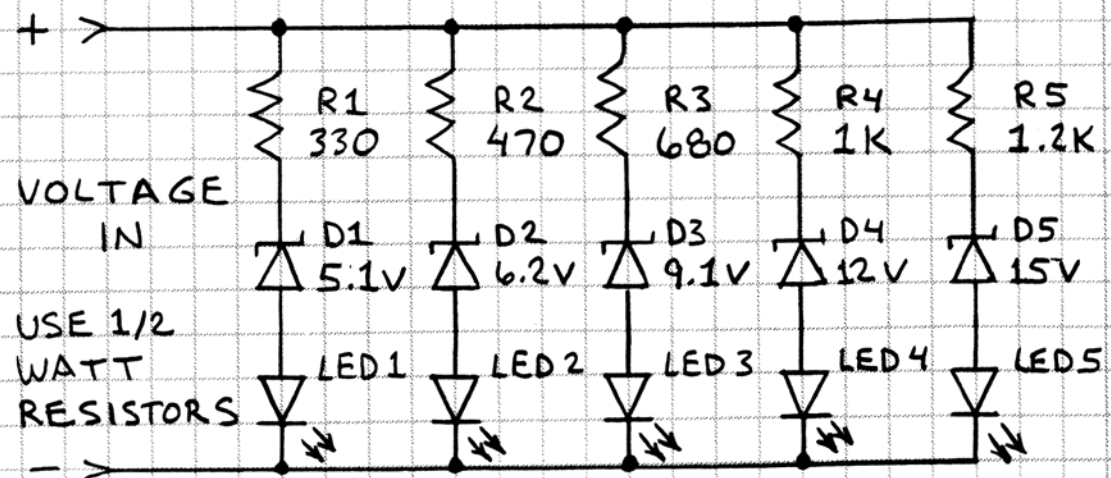


THE LEDs GLOW FROM 1 TO 5 AS INPUT VOLTAGE RISES FROM ABOUT 5 TO 15 VOLTS. OK TO USE ZENER DIODES WITH OTHER BREAKDOWN VOLTAGES.

COMPARATOR VOLTAGE SENSOR

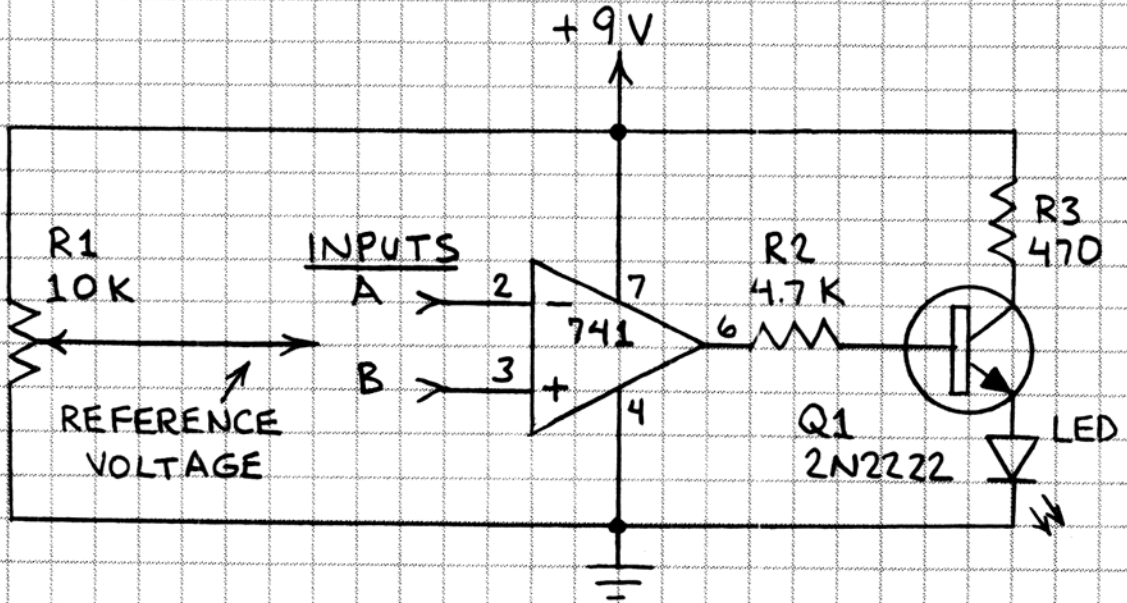
THIS BASIC COMPARATOR VOLTAGE SENSOR DETECTS PRESENCE OF A VOLTAGE ABOVE OR BELOW AN ADJUSTABLE REFERENCE VOLTAGE.



REFERENCE VOLTAGE TO INPUT B :

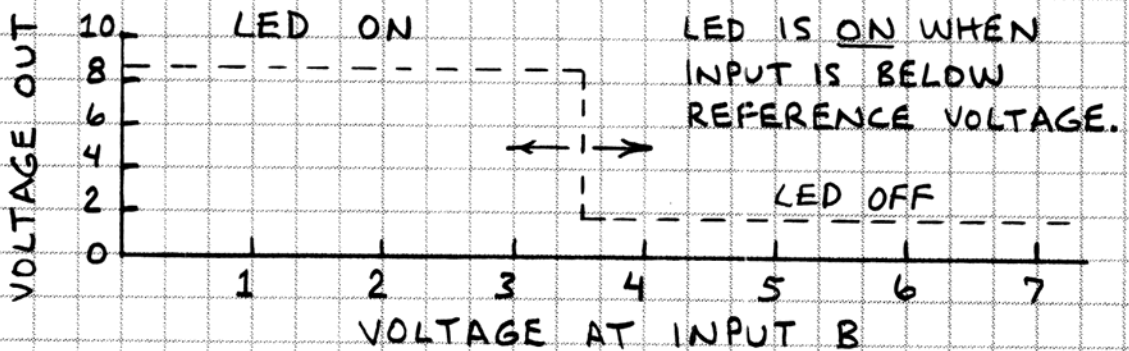


REFERENCE VOLTAGE TO INPUT A :

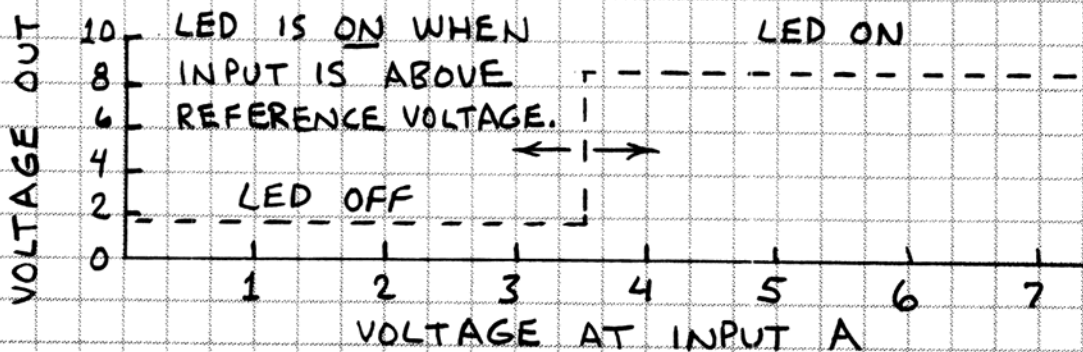

ANALOG PRESSURE SENSOR

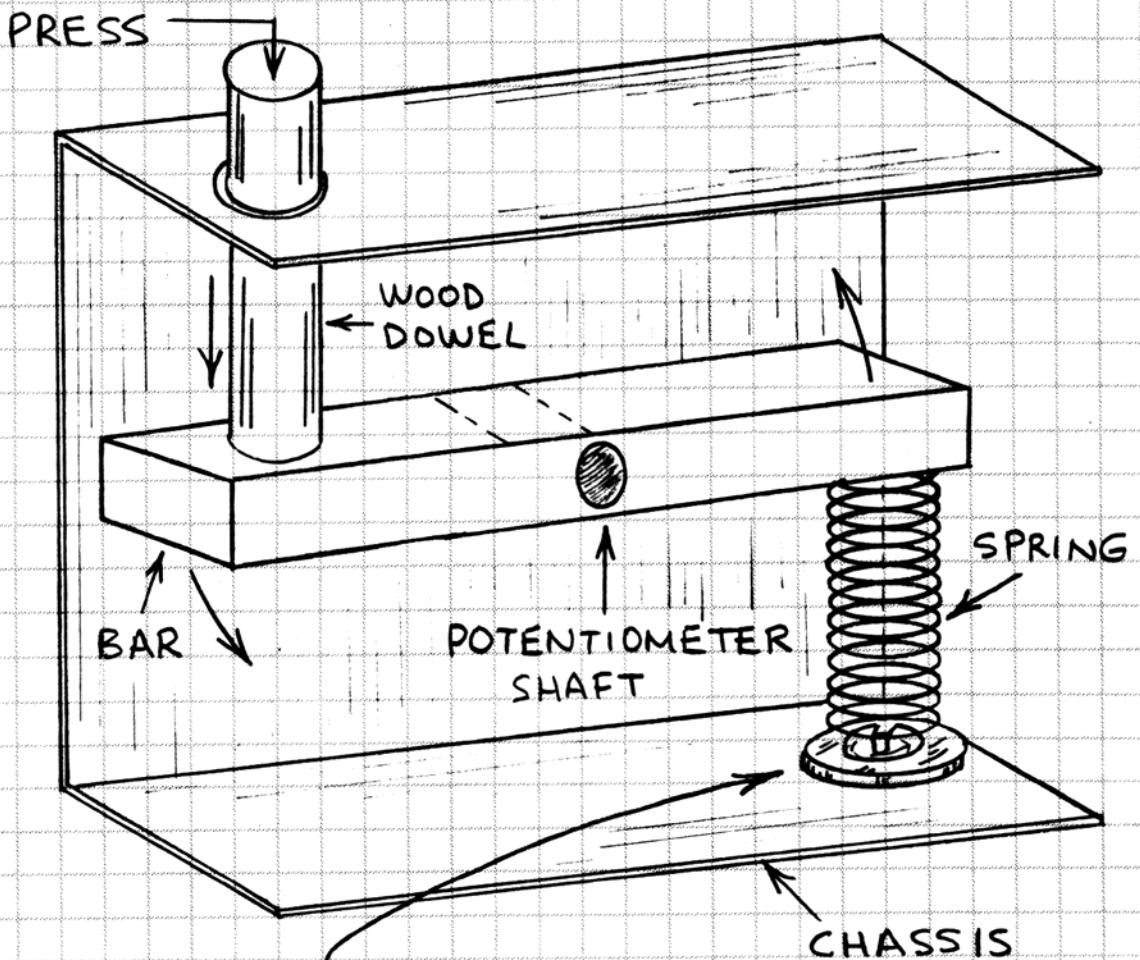
PRESSURE SENSORS ARE EASILY MADE FROM SIMPLE MATERIALS. THIS ONE CHANGES THE RESISTANCE OF A POTENTIOMETER.



ATTACH SPRING TO BAR AND CHASSIS WITH SCREW, NUT AND WASHER.

MAKE BAR FROM WOOD OR PLASTIC. SECURE TO SHAFT OF POTENTIOMETER WITH CEMENT OR SET SCREW.


CHASSIS: USE ALUMINUM ENCLOSURE.
30

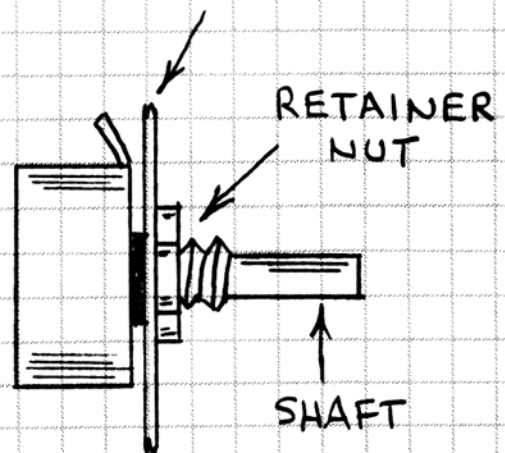

SIDE VIEW OF POTENTIOMETER INSTALLATION


SIMPLE PRESSURE SENSOR

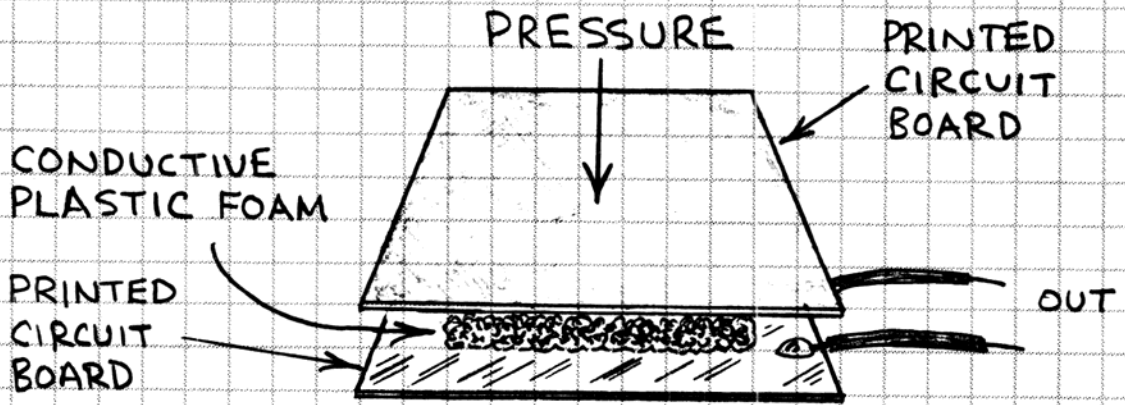THIS SIMPLE SENSOR DOES NOT PROVIDE THE CONSISTENCY OF A POTENTIOMETER, BUT IT IS VERY EASY TO MAKE.



POLISH COPPER SIDE OF BOTH BOARDS. SOLDER CONNECTION WIRES TO EACH BOARD. THEN SANDWICH CONDUCTIVE PLASTIC FOAM (USED TO PROTECT ICs) BETWEEN COPPER SIDES OF THE BOARDS. PLACE SENSOR IN SMALL PLASTIC BOX TO HOLD IT TOGETHER.




PRESSURE-TO-VOLTAGE

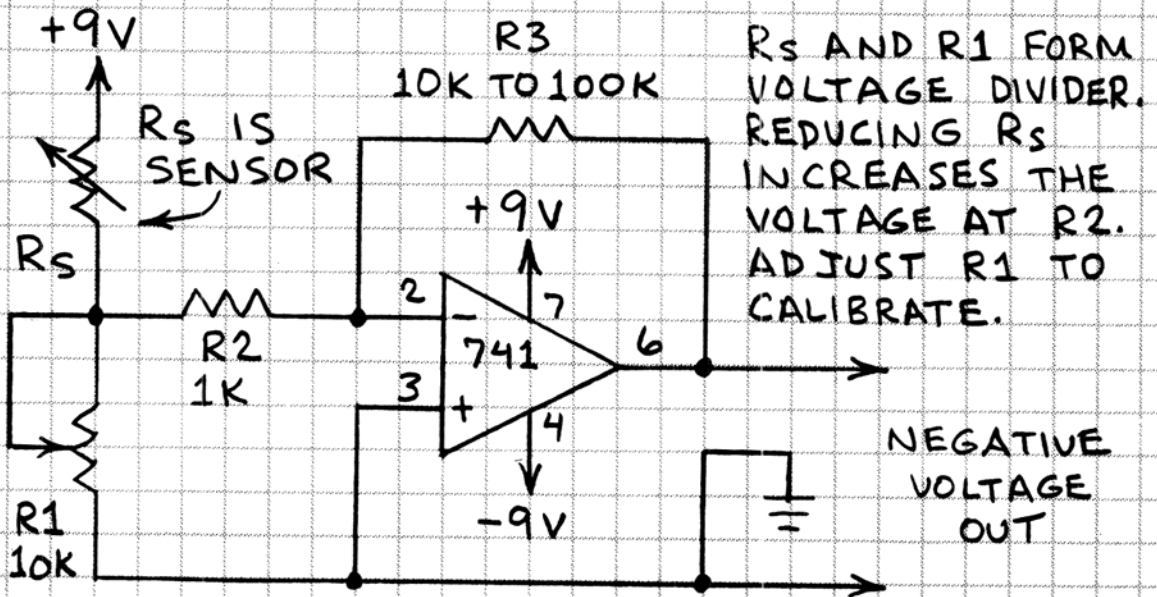

EXPERIMENT WITH VALUES OF R_1 AND R_3 TO GIVE DESIRED OUTPUT. CONNECT R_s TO -9V TO GIVE POSITIVE VOLTAGE OUT.

STRAIN SENSORS

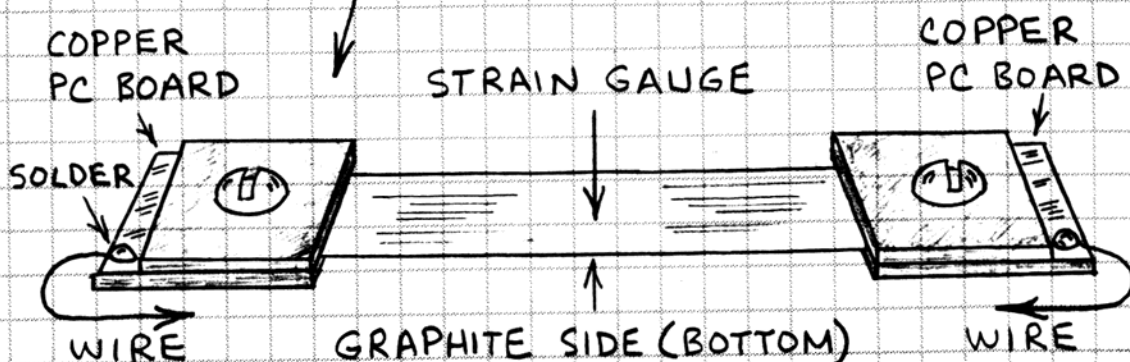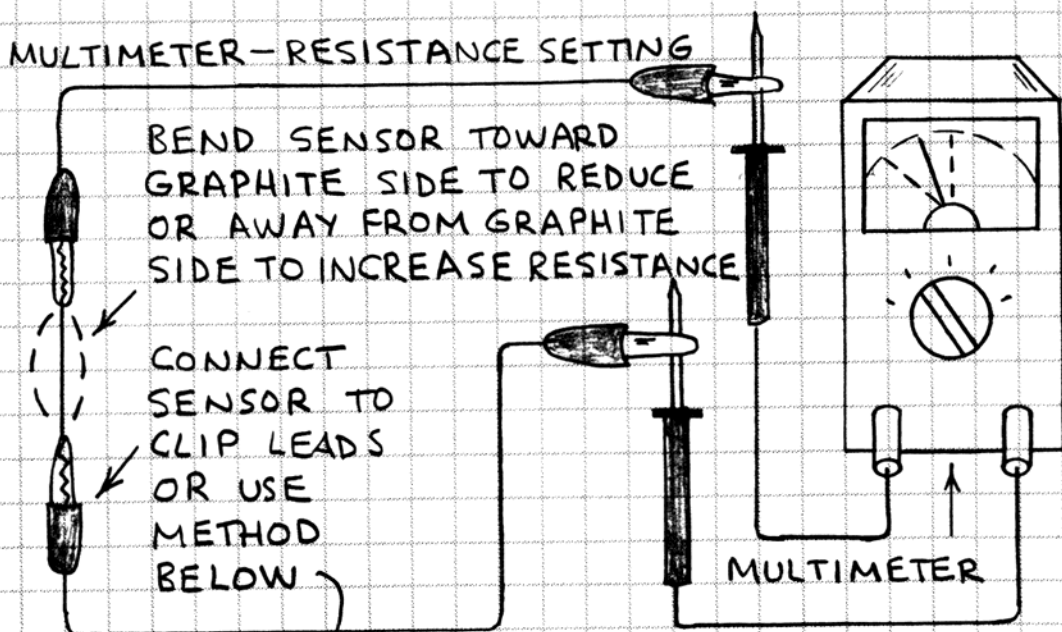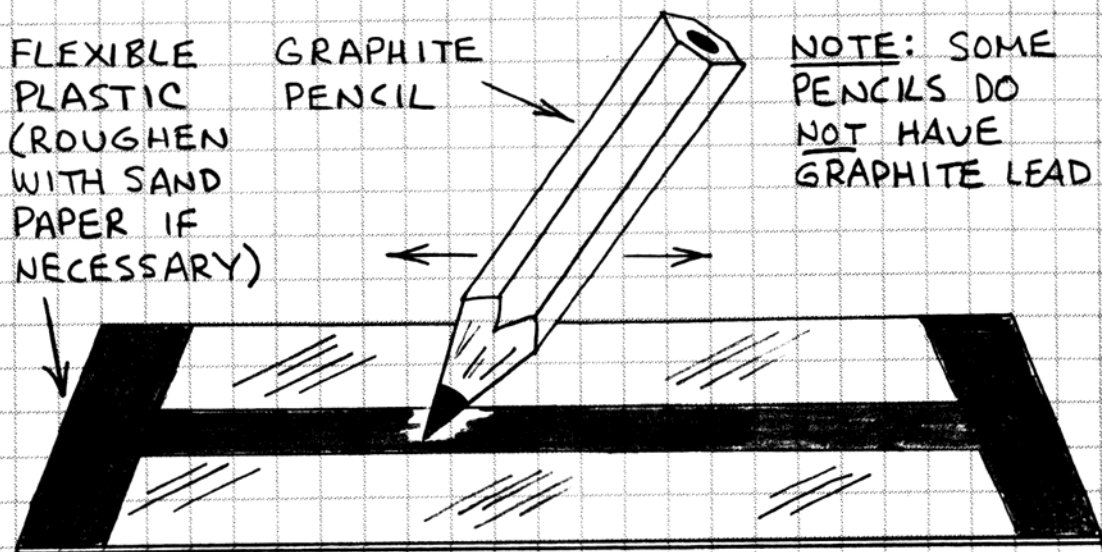A STRAIN GAUGE IS A RESISTOR HAVING A RESISTANCE WHICH CHANGES WHEN THE RESISTOR IS BENT OR TWISTED. YOU CAN EASILY MAKE A WORKING STRAIN GAUGE.



STRAIN SENSOR APPLICATIONS

MY FIRST STRAIN GAUGE PROJECT MONITORED THE MOVEMENT OF A MODEL ROCKET INSTALLED IN A WIND TUNNEL STRAPPED TO THE SIDE OF A 1966 CHEVY. IT WORKED. HERE ARE OTHER APPLICATIONS:

PRESSURE-SENSITIVE RESISTOR - USE STRAIN SENSOR TO CONTROL FREQUENCY OF AUDIO OSCILLATOR OR GAIN OF AMPLIFIER.

PRESSURE-SENSITIVE SWITCH - USE STRAIN SENSOR AS VERY SENSITIVE TOUCH SWITCH.


ACCELEROMETER - ATTACH WEIGHT TO ONE END OF STRAIN SENSOR. MOVEMENT WILL CHANGE RESISTANCE OF SENSOR.

SCALE - ATTACH STRAIN SENSOR TO BOTTOM SIDE OF FLEXIBLE PLATFORM. CALIBRATE BY PLACING ITEMS OF KNOWN WEIGHT ON PLATFORM.


EXPERIMENTAL - ROBOTICS AND DETECTION OF VIBRATION AND MOVEMENT.

STRAIN SENSOR DESIGNS

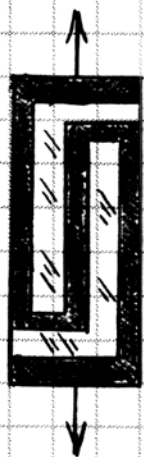TRY THESE VARIATIONS TO INCREASE SENSITIVITY OR MAKE SINGLE-ENDED SENSORS.



HIGH
SENSITIVITY

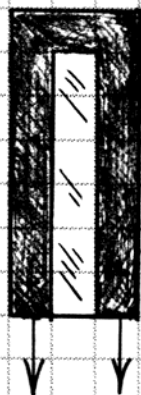


SINGLE
ENDED

CALIBRATE OR ADJUST RESISTANCE BY LIGHTLY STROKING PENCIL ERASER ACROSS GRAPHITE.

TRY COATING GRAPHITE WITH THIN LAYER OF PAINT TO PROTECT FROM UNWANTED CHANGES IN RESISTANCE.


STRAIN SENSOR RELAY

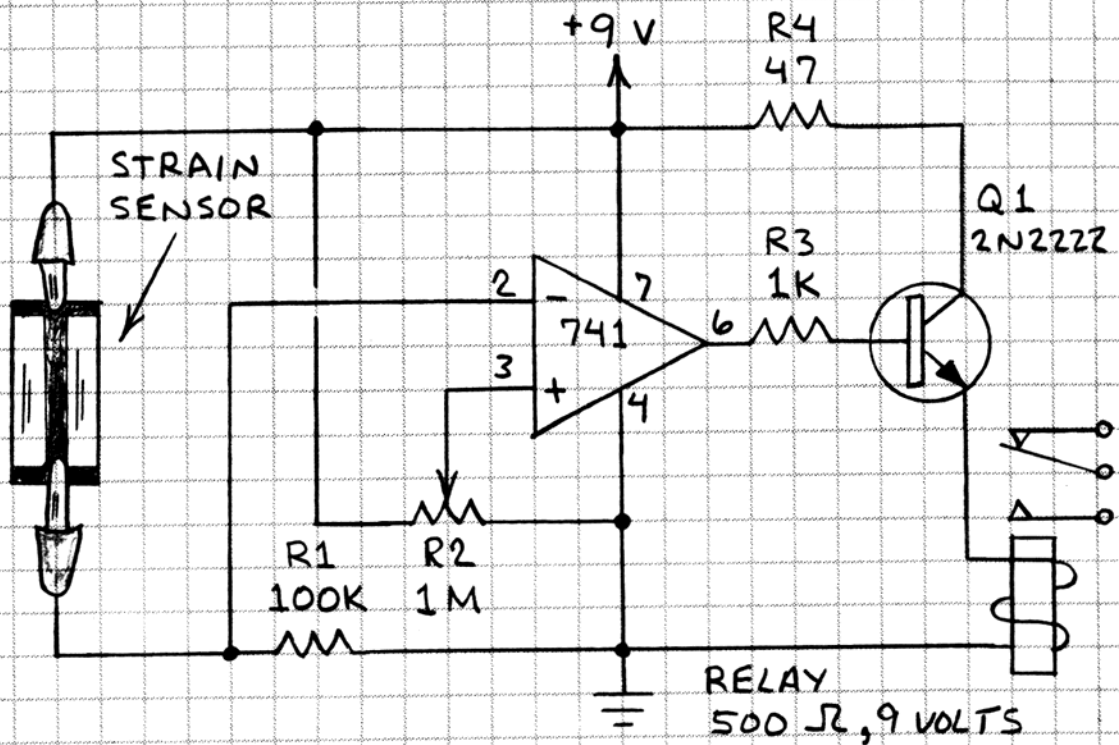THIS CIRCUIT CAN BE ADJUSTED TO PULL IN A RELAY WHEN SENSOR IS BENT OR TWISTED.




STRAIN SENSOR TONE GENERATOR

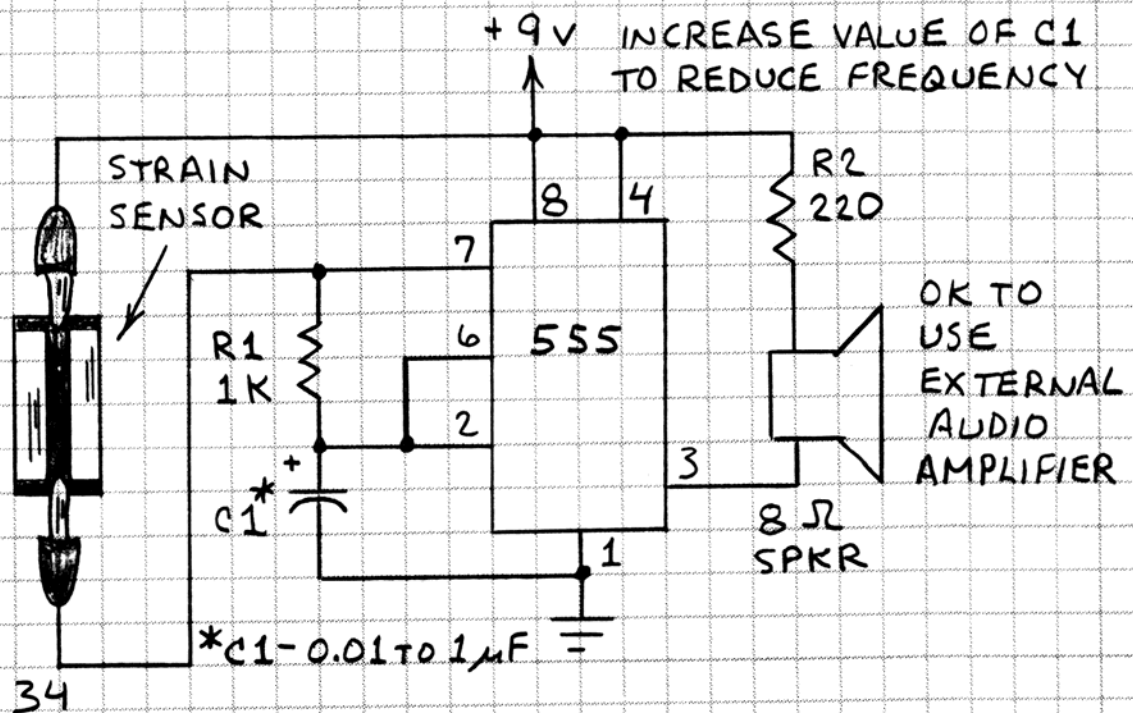THE FREQUENCY OF THE TONE FROM THE SPEAKER CHANGES WHEN THE SENSOR IS BENT OR TWISTED.




STRAIN SENSOR AMPLIFIER

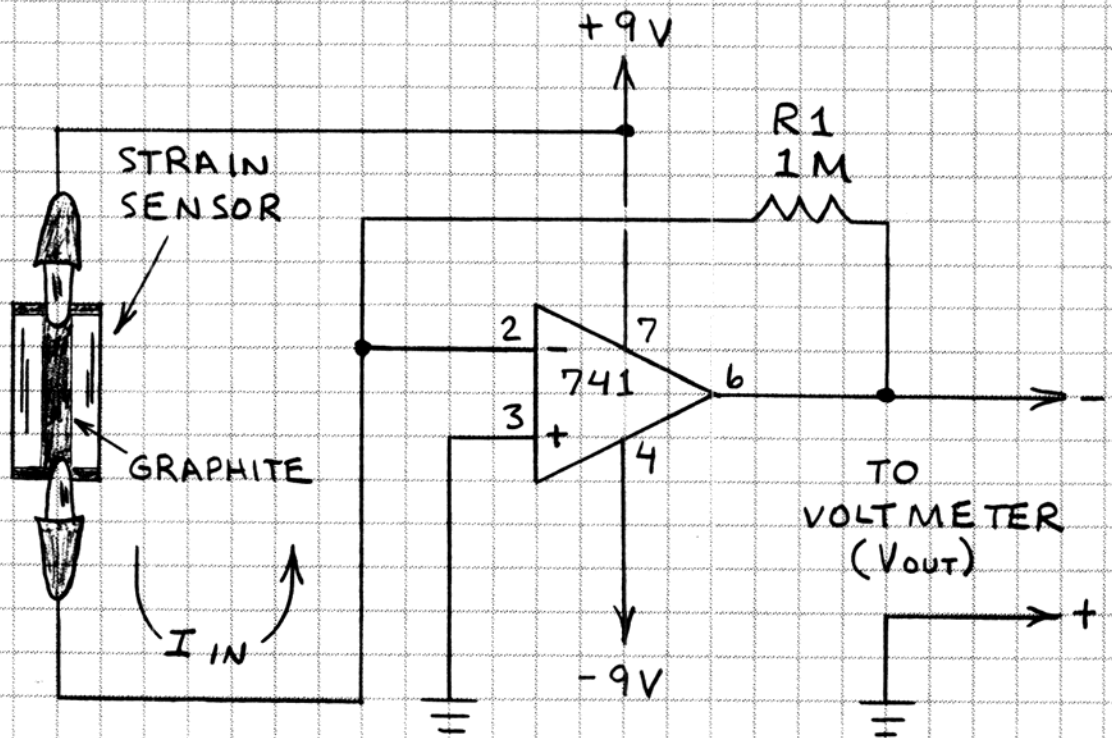THIS CIRCUIT CONVERTS THE CHANGE IN THE RESISTANCE OF A STRAIN SENSOR TO A CHANGE IN VOLTAGE.




THIS CIRCUIT AMPLIFIES THE CURRENT THROUGH THE STRAIN SENSOR (I_{IN}) BY 1,000,000. IT IS THEREFORE VERY SENSITIVE. REDUCE RESISTANCE OF $R1$ TO REDUCE GAIN ($V_{OUT} = I_{IN} \times R1$).

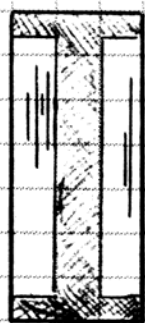RESULTS WITH TYPICAL STRAIN SENSOR (V_{OUT}):




FLAT

1.48V

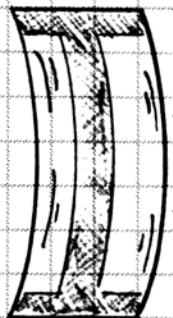

BEND OUT

1.32V

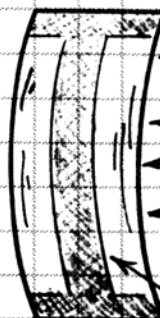

BEND IN



2.25V

PLASTIC STRIP (MYLAR™, OVERHEAD TRANSPARENCY FILM, PRODUCT PACKAGING, ETC.) ROUGHEN WITH SAND PAPER.

USE NARROW LINE WHEN GAIN IS HIGH.

MAGNETIC FIELD SENSOR

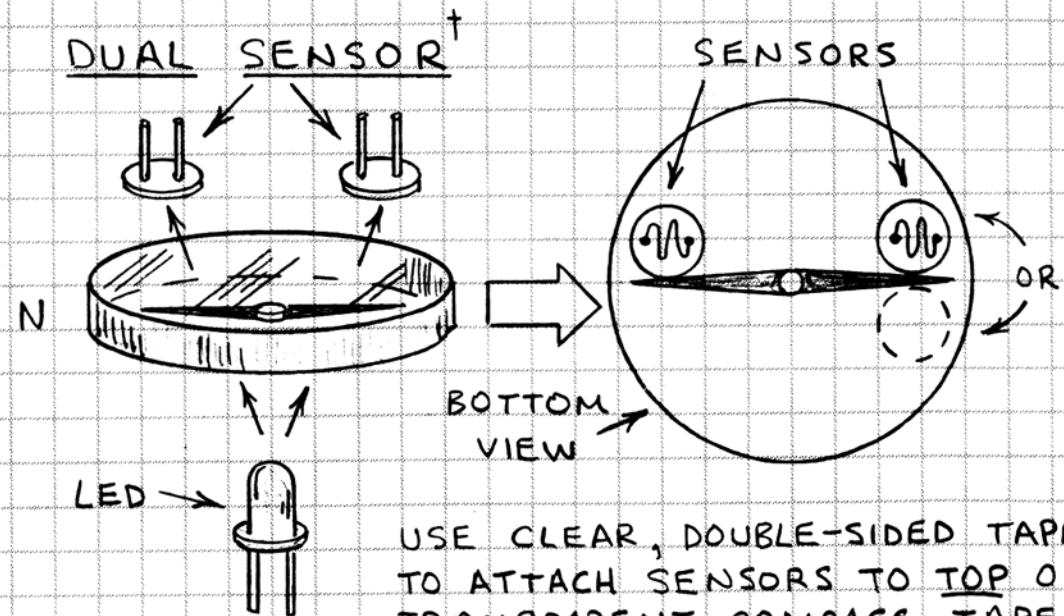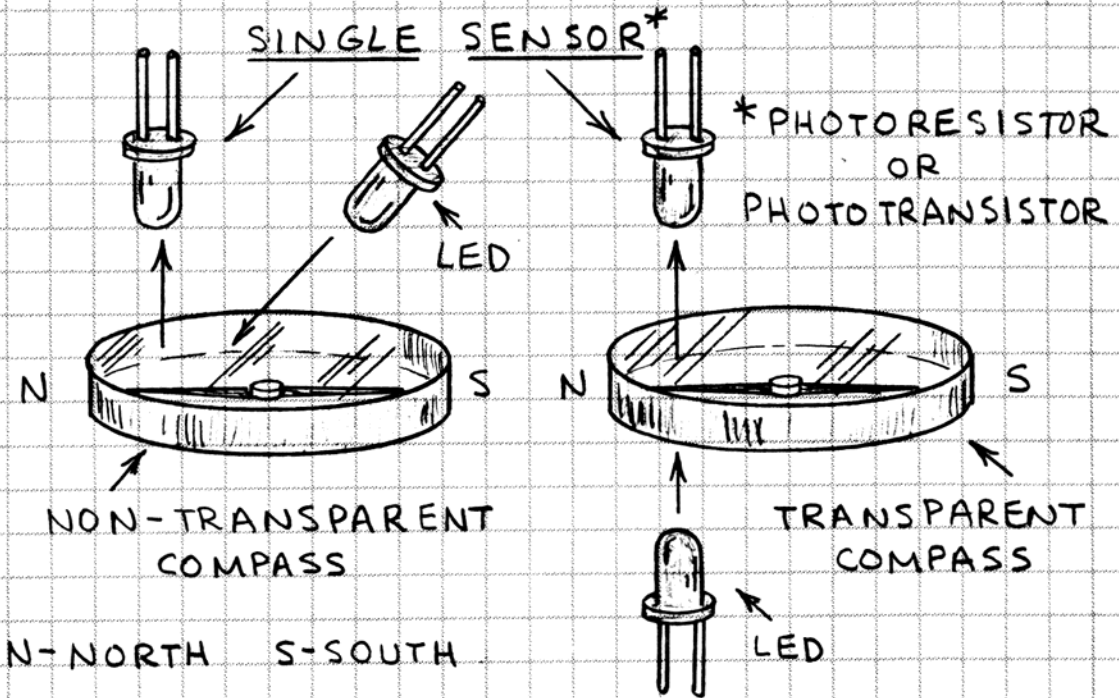A COMPASS IS A MAGNETIC FIELD SENSOR.
A LIGHT SENSOR CAN DETECT TINY MOVEMENTS
OF A COMPASS NEEDLE CAUSED BY ELECTRIC
MOTORS, MAGNETS AND SOLAR ACTIVITY.




† PHOTORESISTORS
USE CLEAR, DOUBLE-SIDED TAPE TO ATTACH SENSORS TO TOP OF TRANSPARENT COMPASS. TAPE BLACK PAPER OVER SENSORS.

TEST BY PLACING COMPASS ON CLEAR BOX ON WHITE PAPER. ROOM LIGHT WILL BE REFLECTED UPWARD. INSTALL COMPASS AND LED IN LIGHT-TIGHT BOX.

MAGNETIC FIELD SWITCH

LIGHT-TIGHT ENCLOSURE

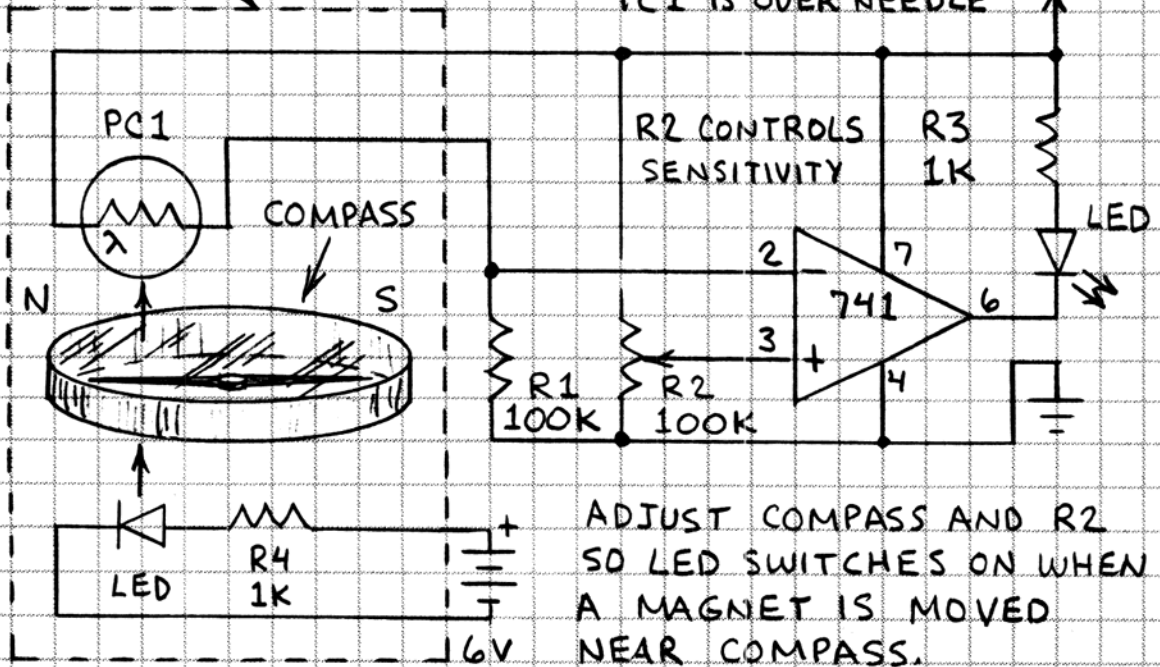
ROTATE COMPASS SO PC1 IS OVER NEEDLE
+9V
PC1 IS OVER NEEDLE



MAGNETIC FIELD AMPLIFIER


LIGHT-TIGHT ENCLOSURE

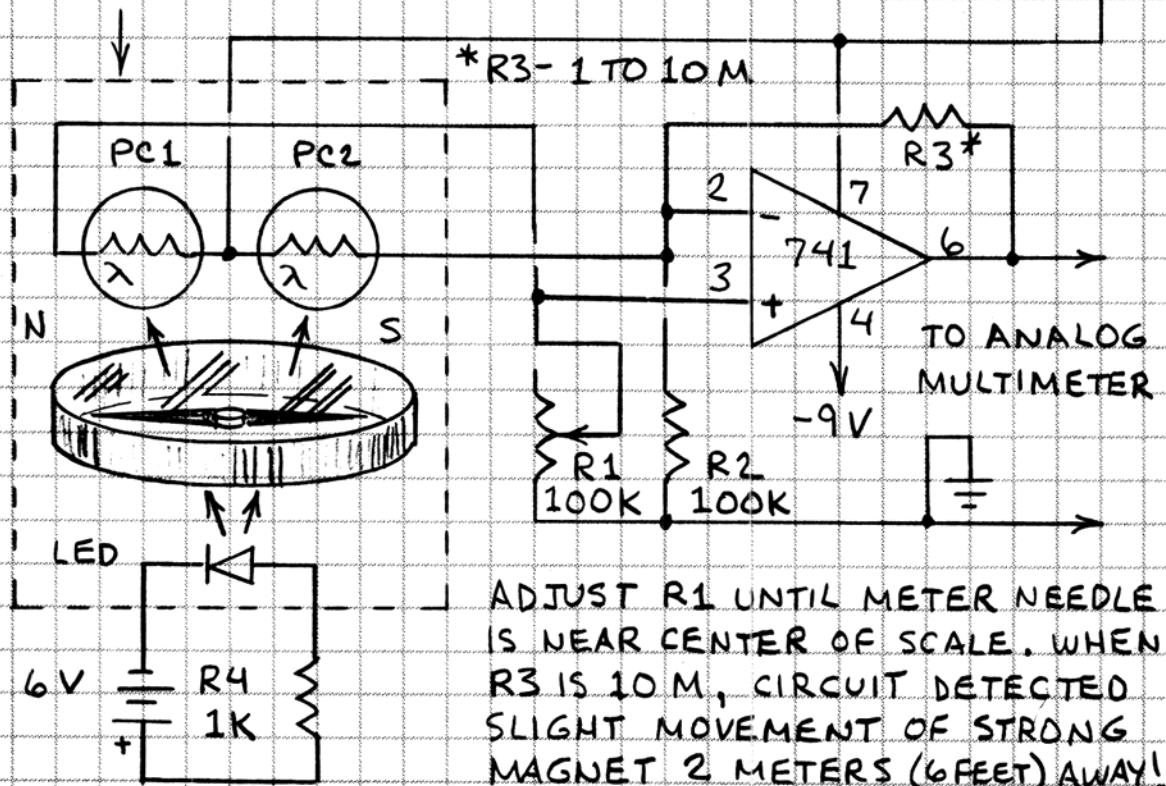ROTATE COMPASS SO PC1 AND PC2 ARE OVER NEEDLE
+9V
AND PC2 ARE OVER NEEDLE



VIDEO MONITOR SENSORS

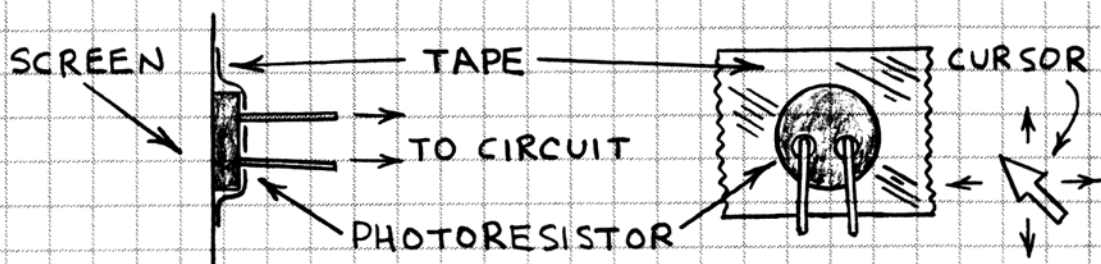TAPE A LIGHT-SENSITIVE PHOTORESISTOR, PHOTOTRANSISTOR OR SOLAR CELL TO THE SCREEN OF A VIDEO MONITOR. A SPOT OF LIGHT FLASHED ON THE SCREEN UNDER THE LIGHT SENSOR CAN THEN CONTROL A TONE GENERATOR, LIGHT OR RELAY. THUS LIGHT ON THE MONITOR'S SCREEN REPLACES CONNECTION WIRES BETWEEN THE MONITOR AND THE DEVICE BEING CONTROLLED.



1. BUSY SIGNAL - WHEN A PROGRAM TAKES LOTS OF TIME TO CRUNCH DATA, USE THE MOUSE TO MOVE THE BUSY ICON (⌂) UNTIL IT IS UNDER A LIGHT SENSOR TAPED ON THE SCREEN. CONNECT THE SENSOR TO A TONE GENERATOR. A VERY DISTINCT CHANGE IN THE SOUND OF THE TONE WILL OCCUR WHEN THE BUSY ICON CHANGES TO THE CURSOR SYMBOL. THIS WILL ALLOW YOU TO DO SOMETHING ELSE WHILE YOU ARE WAITING FOR THE COMPUTER TO COMPLETE AN OPERATION.


2. CONTROLLER - WRITE PROGRAMS IN BASIC, QBASIC OR OTHER LANGUAGES THAT PLACE BLOCKS OF LIGHT ON A BLACK BACKGROUND DIRECTLY UNDER ONE OR MORE LIGHT SENSORS. THIS WILL ALLOW YOUR COMPUTER TO CONTROL EXTERNAL LIGHTS, SOUNDS AND RELAYS UNDER PROGRAM CONTROL.

3. DRIVE SIGNAL - TAPE A LIGHT SENSOR OVER THE INDICATOR LIGHT FOR A HARD DRIVE OR CD-ROM DRIVE. CONNECT THE SENSOR TO A TONE GENERATOR. EACH TIME THE DRIVE IS ACCESSED A TONE WILL SOUND.

4. VIDEO CAMERA - VIDEO CAMERAS ARE IDEAL FOR WATCHING A SLEEPING BABY OR A FRONT PORCH. BUT YOU MUST WATCH THE MONITOR TO KNOW WHEN SOMETHING HAS HAPPENED. TAPE ONE OR MORE LIGHT SENSORS TO THE PART OF THE SCREEN WHERE MOVEMENT OR CHANGES ARE MOST LIKELY TO OCCUR. THEN CONNECT THE SENSOR TO A THRESHOLD DETECTOR. WHEN THE IMAGE ON THE MONITOR CHANGES, A BUZZER WILL SOUND.

PLEASE NOTE - WHILE ALL THESE APPLICATIONS HAVE BEEN TESTED, THEY ARE EXPERIMENTAL. THE RESULTS YOU OBTAIN WILL BE SUBJECT TO INTERFERENCE FROM AMBIENT LIGHT AND TO HOW AND WHERE YOU ATTACH THE LIGHT SENSOR TO THE MONITOR.

VIDEO MONITOR TONE GENERATOR

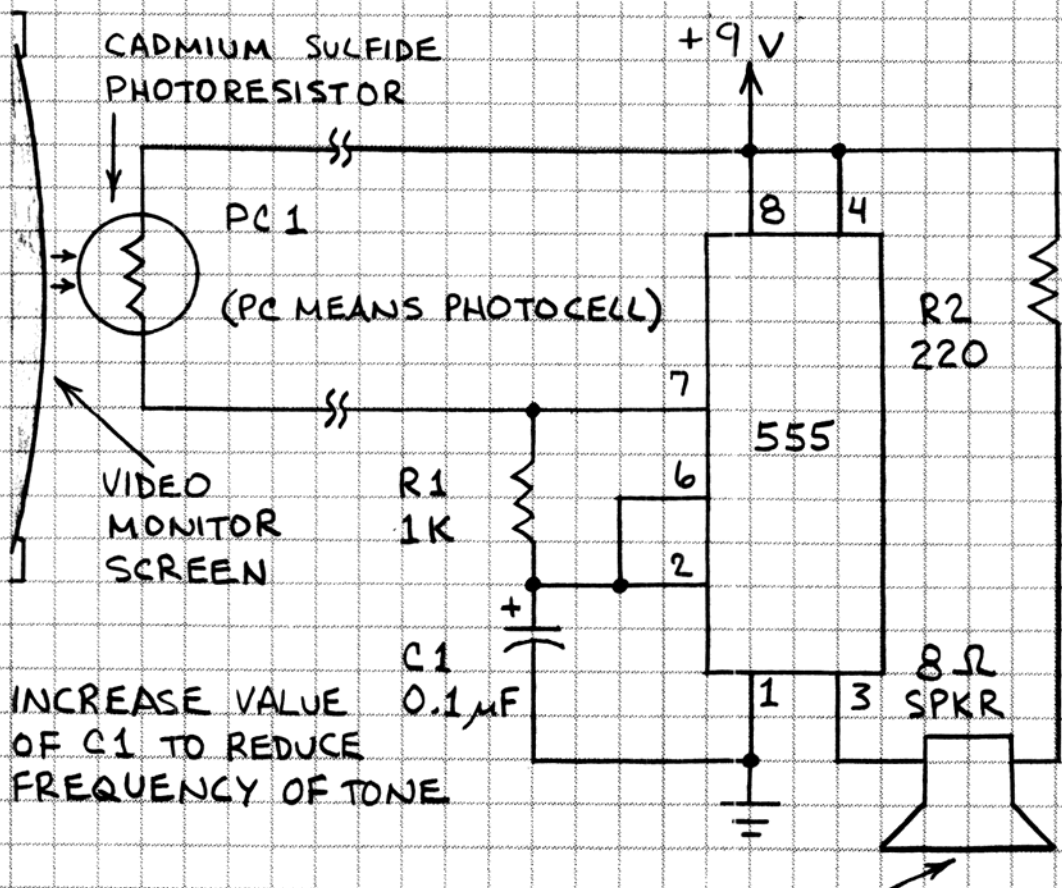


OK TO REPLACE SPEAKER WITH PIEZOELECTRIC BUZZER ELEMENT. (RED WIRE TO PIN 4 AND BLACK WIRE TO PIN 3.)

VIDEO MONITOR RELAY CIRCUITS

THESE CIRCUITS PROVIDE A SIMPLE MEANS FOR CONTROLLING EXTERNAL DEVICES WITH A VIDEO MONITOR.


LIGHT-ACTIVATED RELAY

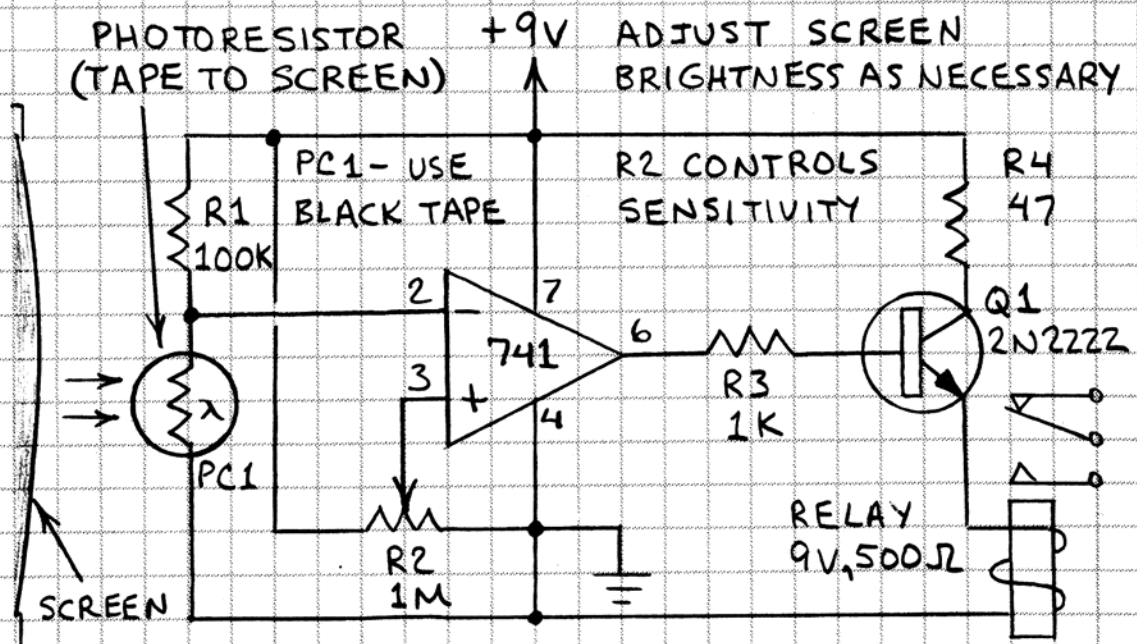RELAY DROPS OUT WHEN SCREEN AT PC1 IS BRIGHT.




DARK-ACTIVATED RELAY

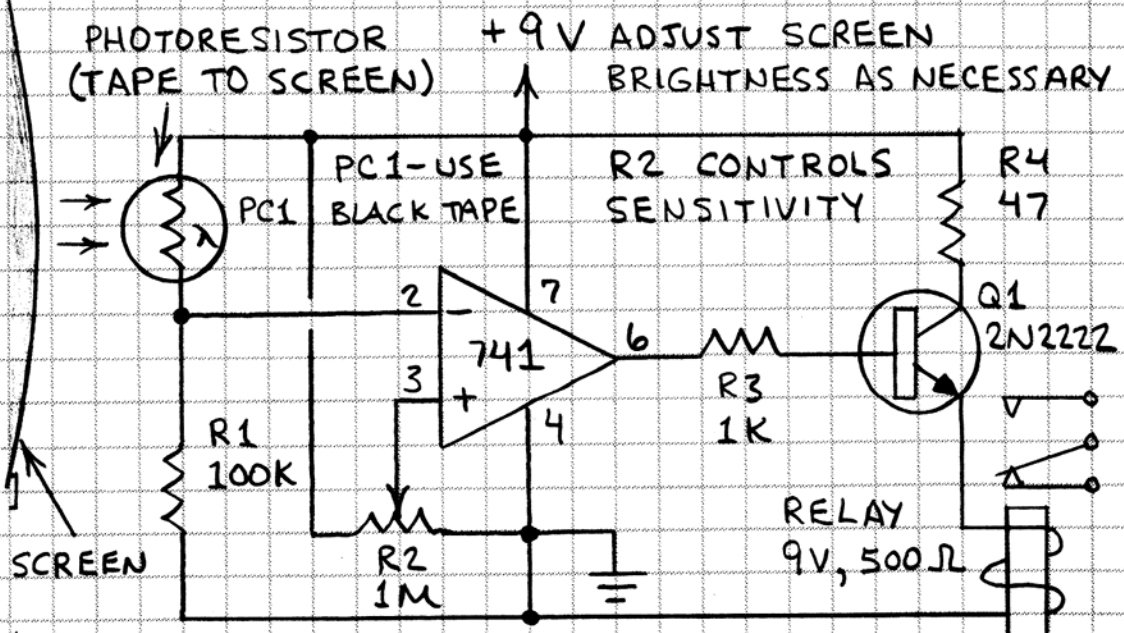RELAY PULLS IN WHEN SCREEN AT PC1 IS DARK.




IMPROVED VIDEO MONITOR RELAY

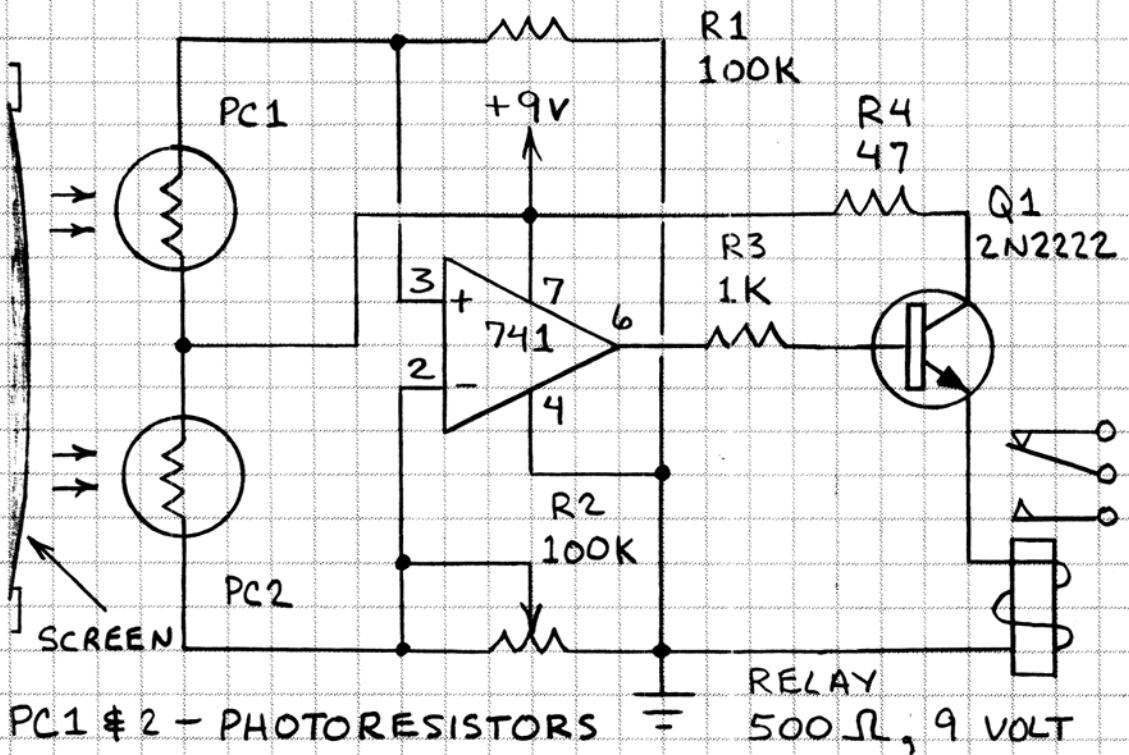THIS CIRCUIT USES DUAL PHOTORESISTORS TO PROVIDE DIFFERENTIAL OPERATION. CHANGES IN ROOM LIGHTING CAUSE THE SAME RESISTANCE CHANGE IN BOTH PHOTORESISTORS, THUS THEY CANCEL ONE ANOTHER. ONLY WHEN PC1 RECEIVES MORE LIGHT THAN PC2 IS THE CIRCUIT UNBALANCED AND THE RELAY ACTUATED.



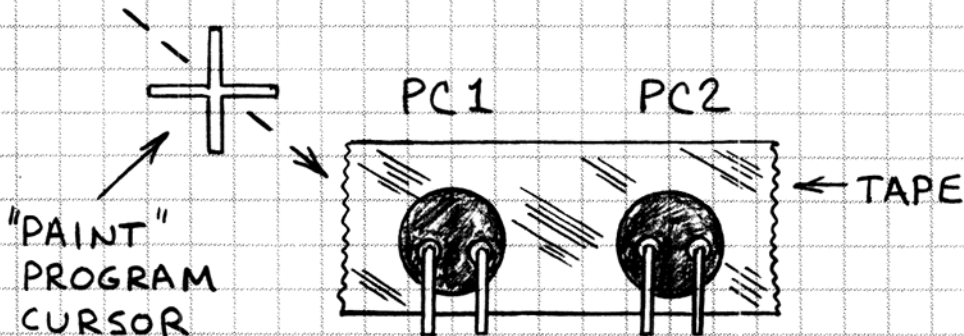ADJUST R2 TO CONTROL SWITCHING THRESHOLD.



THIS CIRCUIT EASILY RESPONDS TO VARIOUS CURSORS GENERATED BY TYPICAL PAINT PROGRAMS. THE PROTOTYPE COULD BE SET (VIA R2) TO ACTUATE THE RELAY WHEN THE TEXT CURSOR IN MICROSOFT™ PAINTBRUSH APPROACHED PC1 (WHITE ON BLACK).

VIDEO MONITOR SENSOR PROGRAMS

HERE ARE SOME SIMPLE PROGRAMS THAT DEMONSTRATE HOW A COMPUTER CAN CONTROL EXTERNAL DEVICES VIA ONE OR MORE LIGHT SENSORS THAT RECEIVE PROGRAMMED FLASHES OF LIGHT FROM THE MONITOR'S SCREEN.

THIS QBASIC PROGRAM PLACES AN "X" AT THE SAME PLACE ON THE SCREEN FOR 10 ON-OFF CYCLES:

```
REM X ON X OFF DEMO
CLS
FOR A = 1 TO 10
LOCATE 20, 50: PRINT "X"
FOR N = 1 TO 1000: NEXT N
LOCATE 20, 50: PRINT " "
FOR N = 1 TO 1000: NEXT N
NEXT A
END
```

HOW THIS PROGRAM WORKS:

FOR A = 1 TO 10 CONTROLS NUMBER OF ON-OFF CYCLES. FOR EXAMPLE, CHANGE 10 TO 100 FOR 100 CYCLES.

LOCATE 20, 50: PRINT "X" PLACES AN "X" AT ROW 20, COLUMN 50. A TYPICAL MONITOR HAS 25 ROWS AND 80 COLUMNS. YOU CAN PLACE THE "X" ANYWHERE WITHIN THIS RANGE.

FOR N = 1 TO 1000: NEXT N DETERMINES HOW LONG THE "X" STAYS ON AND OFF. INCREASE THE SECOND NUMBER TO INCREASE THE DELAY.

FOR FLASHING CURSOR, CHANGE LOCATE STATEMENTS:

```
LOCATE 20, 50, 1, 0, 7 (CURSOR ON)
```

```
;
```

```
LOCATE 20, 50, 1, 1, 0 (CURSOR OFF)
```

THIS PROGRAM ALTERNATELY FLASHES AN "X"
AT TWO ADJACENT LOCATIONS TO CONTROL
TWO LIGHT SENSORS.

```
REM DUAL FLASHER ROUTINE
CLS
FOR A = 1 TO 10
LOCATE 20, 50 : PRINT "X"
LOCATE 20, 40 : PRINT " "
FOR N = 1 TO 1000 : NEXT N
LOCATE 20, 50 : PRINT " "
LOCATE 20, 40 : PRINT "X"
FOR N = 1 TO 1000 : NEXT N
NEXT A
END
```

NOTE: THIS PROGRAM AND THE ONE ON
FACING PAGE WILL WORK WITH BASIC IF
YOU PLACE A CONSECUTIVE NUMBER BEFORE
EACH LINE. (TRY 10, 20, 30, ETC. SO YOU
CAN INSERT NEW LINES LATER.)

MODIFYING THE SCREEN SYMBOL

LOCATE IS THE SIMPLEST COMMAND FOR
PLACING A CHARACTER AT A DESIRED PLACE
ON THE SCREEN. IF "X" OR OTHER KEYBOARD
CHARACTERS DO NOT PROVIDE ENOUGH LIGHT
OR CONTRAST TO ACTIVATE YOUR SENSOR,
INCREASE THE SCREEN BRIGHTNESS OR TRY USING
AN ASCII CHARACTER ACCESSED BY THE CHR\$
STATEMENT. FOR EXAMPLE:

```
LOCATE 20, 20 : PRINT CHR$(178)
```


PLACES A WHITE BOX ON THE SCREEN.
OTHER SUITABLE ASCII SYMBOLS INCLUDE:

▣ - 176	- 179	≠ - 216	▣ - 220	o - 249
▣ - 177	+ - 197	▣ - 219	▣ - 223	° - 250

SEE PROGRAM MANUALS FOR COMPLETE LIST.


LIGHTNING SENSOR

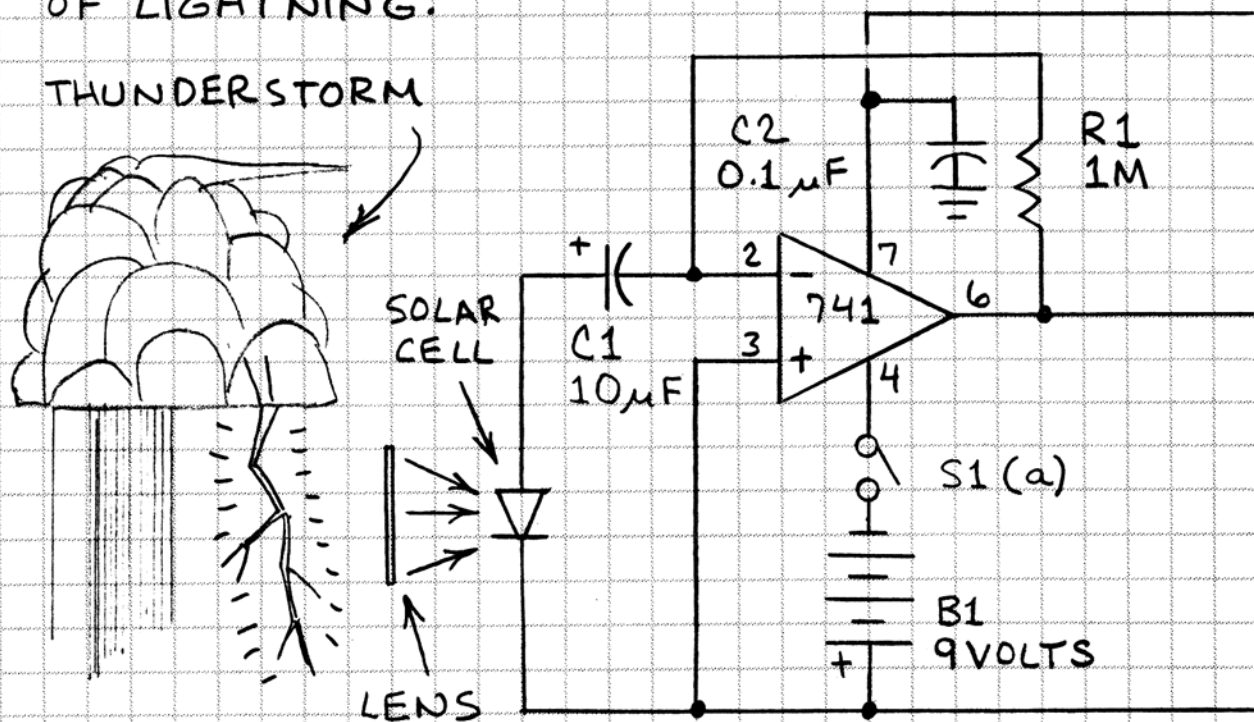USE THIS CIRCUIT TO
DETECT DISTANT FLASHES
OF LIGHTNING.



SINCE A LIGHTNING BOLT IS A GIANT RADIO TRANSMITTER, A TRANSISTOR RADIO CAN DETECT LIGHTNING. BUT THE POPS AND CRACKLES YOU HEAR DO NOT REVEAL THE DIRECTION OF THE LIGHTNING. THIS CIRCUIT INDICATES THE GENERAL DIRECTION OF LIGHTNING BOLTS DURING THE DAY WHEN IT MAY BE TOO BRIGHT TO SEE THE FLASHES. AT NIGHT IT WILL DETECT DISTANT LIGHTNING THAT MAY BE TOO FAINT TO SEE.

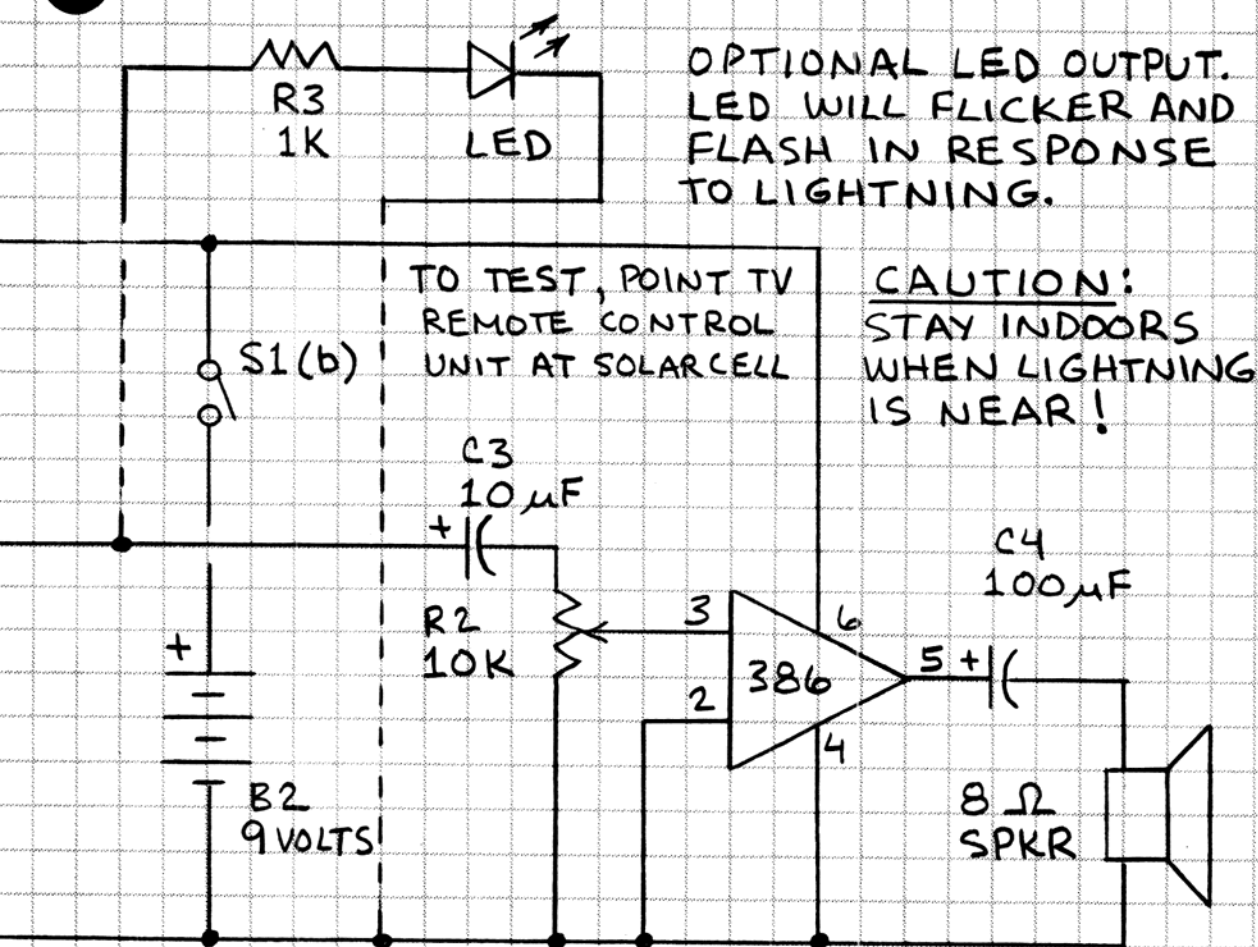
FOR BEST RESULTS MOUNT THE SOLAR CELL BEHIND A MAGNIFYING LENS. A LARGE PLASTIC FRESNEL LENS SUCH AS THE FLAT PLASTIC LENSES SOLD AS PAGE MAGNIFIERS WORKS WELL. THE LENS WILL COLLECT MUCH MORE LIGHT THAN THE SOLAR CELL ALONE AND IT WILL MAKE THE SENSOR VERY DIRECTIONAL.




TO MAKE A DIRECTIONAL LIGHTNING SENSOR, CEMENT A SOLAR CELL TO THE INSIDE OF EACH SIDE OF A CLEAR SQUARE PLASTIC BOX. ASSEMBLE FOUR SENSOR CIRCUITS WITH AN LED OUTPUT (LESS 386 AUDIO OUTPUT STAGE) ON A CIRCUIT BOARD AND INSTALL BOARD AND BATTERY INSIDE THE PLASTIC BOX. SELECT A DIFFERENT COLOR (RED, YELLOW, ORANGE AND GREEN) FOR EACH LED. INSTALL THE LEDs ON THE SAME SIDE OF THE BOX SO THEY CAN BE SEEN FROM A DISTANCE. MARK EACH SIDE OF THE BOX WITH THE FOUR COMPASS DIRECTIONS (NORTH, EAST, SOUTH AND WEST) AND NOTE THE LED COLOR FOR EACH DIRECTION. PLACE THE SENSOR IN AN OPEN FIELD SO THAT ITS NORTH SIDE FACES NORTH AND WHERE YOU CAN SEE IT FROM INSIDE YOUR HOUSE. COLOR OF FLASHING LED OR LEDS WILL INDICATE THE APPROXIMATE DIRECTION OF LIGHTNING BOLTS.

INFRARED SENSOR

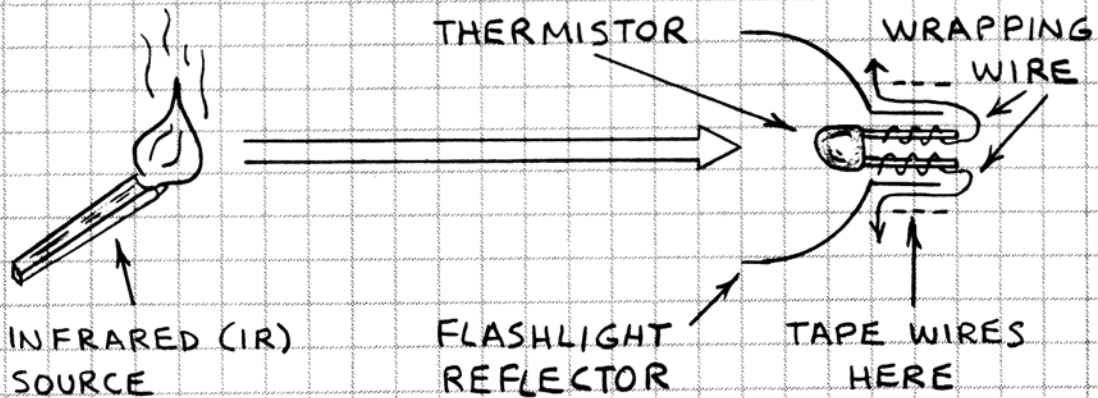A THERMISTOR IS A TEMPERATURE-SENSITIVE RESISTOR. INSTALL A THERMISTOR AT THE FOCAL POINT OF A FLASHLIGHT REFLECTOR TO DETECT INFRARED RADIATION FROM HEAT SOURCES.




INFRARED SWITCH

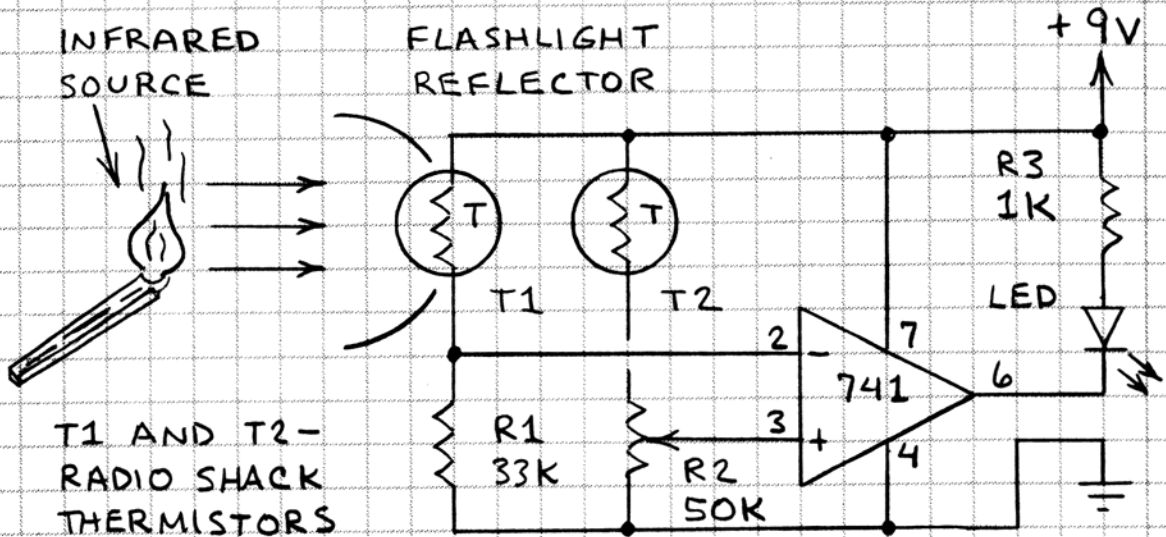

CONNECT BATTERY AND WAIT SEVERAL SECONDS TO ALLOW THERMISTORS TO STABILIZE. ADJUST R2 UNTIL LED JUST SWITCHES OFF. PLACE YOUR HAND NEAR REFLECTOR AND LED SHOULD TURN ON. A MATCH WILL TRIGGER THE CIRCUIT FROM UP TO 1 METER (ABOUT 3 FEET) OR MORE. NOTE THAT CHANGES IN AIR TEMPERATURE CAUSE EQUAL CHANGES IN T1 AND T2. BUT AN INFRARED SOURCE AFFECTS ONLY T1. TO ADD RELAY SEE SIMILAR CIRCUITS IN THIS BOOK.

INFRARED AMPLIFIER

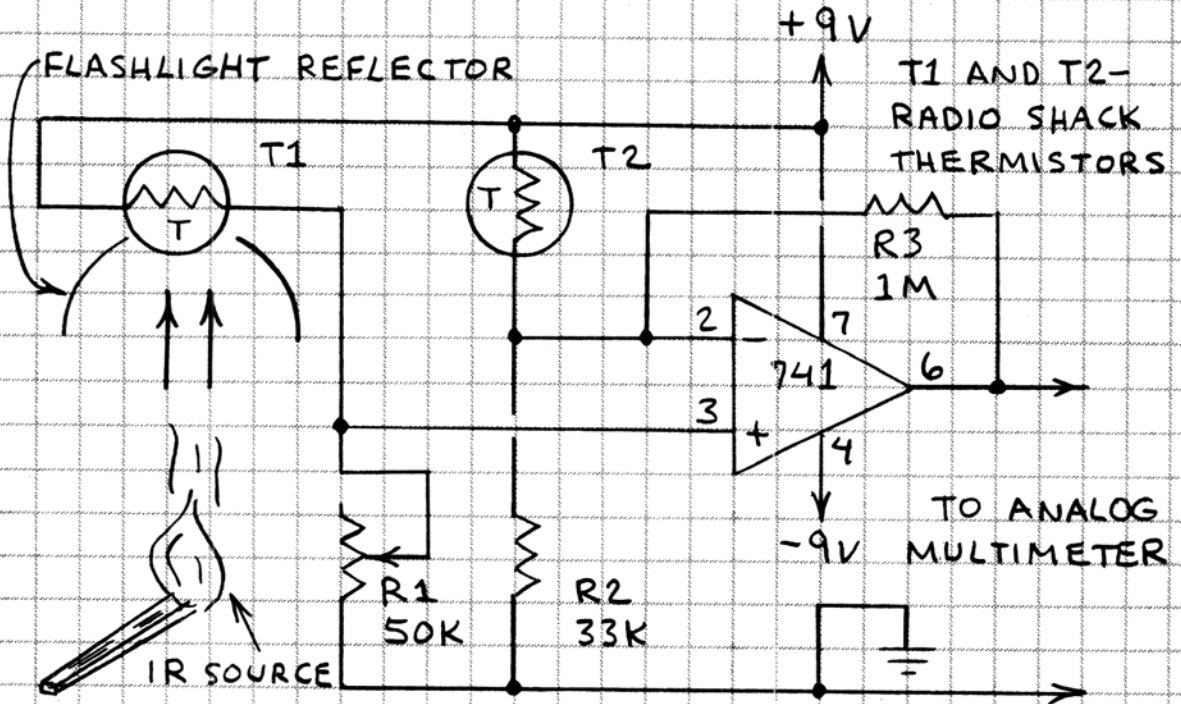THIS CIRCUIT WILL INDICATE THE PRESENCE OF A FLAME OR HOT SOLDERING IRON. THE OUTPUT VOLTAGE (V_{out}) INCREASES AS INFRARED INCREASES.




SET MULTIMETER TO 0-5 OR 0-10 VOLTS DC. ADJUST R1 UNTIL METER NEEDLE IS NEAR CENTER OF METER SCALE. AN INFRARED SOURCE WITHIN FIELD OF VIEW OF REFLECTOR WILL CAUSE THE METER NEEDLE TO DEFLECT UPWARD (TO RIGHT). REMOVE IR SOURCE AND THE METER NEEDLE WILL MOVE DOWNWARD (TO LEFT). CORRECT ALIGNMENT OF T1 INSIDE THE REFLECTOR IS IMPORTANT.

REFLECTOR ALIGNMENT

THERMISTOR MUST BE AT REFLECTOR FOCAL POINT. THE FOCAL POINT IS WHERE FILAMENT OF FLASHLIGHT BULB WOULD BE. LOOK INTO REFLECTOR AND SEE




MISALIGNED

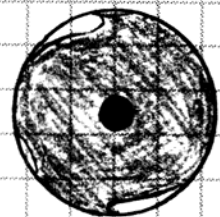

ALIGNED

POLARIZED LIGHT

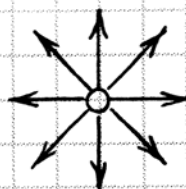WAVES OF ORDINARY LIGHT VIBRATE IN MANY DIRECTIONS. LIGHT WAVES THAT TRAVEL TO YOUR EYES FROM THE CIRCLE BELOW VIBRATE LIKE THIS:



UNPOLARIZED LIGHT

RAY OF REFLECTED LIGHT AND LIGHT THAT PASSES THROUGH SOME MATERIALS VIBRATE IN ONLY ONE DIRECTION. IF THEY VIBRATE IN ONLY ONE DIRECTION, THE LIGHT IS POLARIZED:



POLARIZED LIGHT


SUNLIGHT REFLECTED FROM WATER, ICE, GLASS AND METAL IS PARTIALLY OR EVEN COMPLETELY POLARIZED. SUNGLASSES WITH POLARIZING LENSES BLOCK THE GLARE OF REFLECTED SUNLIGHT, WHICH MAKES THEM POPULAR WITH PEOPLE WHO FISH OR SKI. THE SKY 90° AWAY FROM THE SUN IS PARTIALLY POLARIZED. YOU CAN SEE THIS YOURSELF WITH THE HELP OF POLARIZED SUNGLASSES.

THE MOST POLARIZED SECTION OF THE SKY APPEARS AS A DARK BAND WHEN VIEWED THROUGH POLARIZED SUNGLASSES. WITH YOUR BACK TO THE SUN, LOOK AT THE SKY 90° AWAY FROM THE SUN TO SEE THIS: THE POLARIZED BAND IS BEST SEEN NEAR SUNRISE OR SUNSET WHEN IT IS STRAIGHT OVER HEAD AND FORMS A NEARLY NORTH-SOUTH BAND.




POLARIZED LIGHT SENSOR

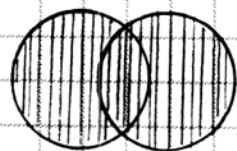
POLARIZING FILTERS ARE AVAILABLE FROM CAMERA AND SCIENCE STORES. OR USE LENSES FROM INEXPENSIVE POLARIZING SUNGLASSES. CROSSING TWO POLARIZERS BLOCKS MOST LIGHT.



UNCROSSED

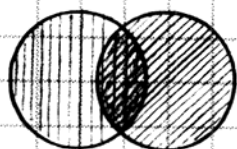


PARTIALLY CROSSED

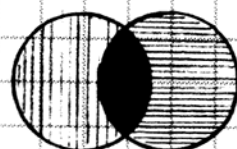

CROSSED

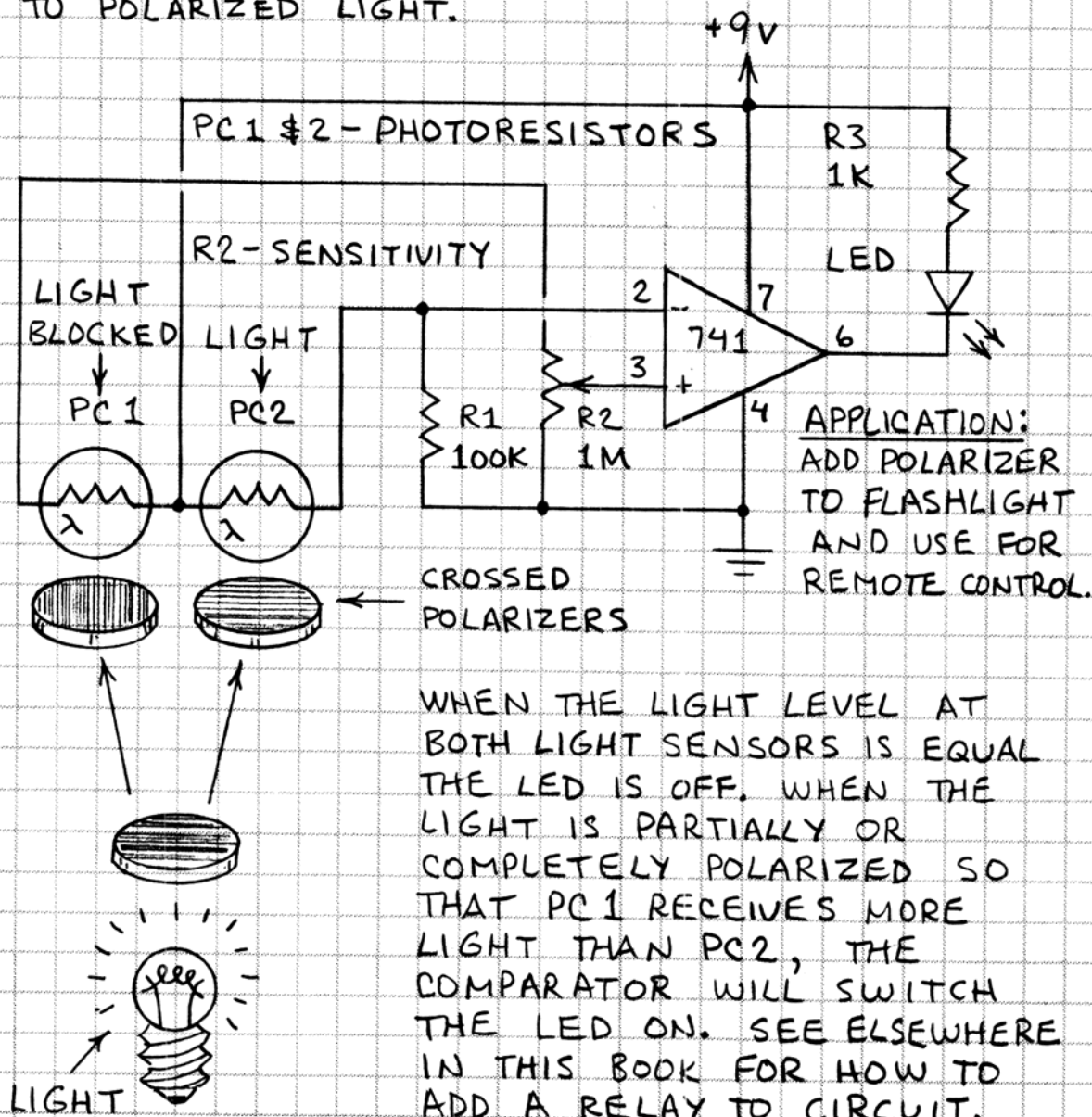THIS PRINCIPLE CAN BE USED TO MAKE SENSORS WHICH IGNORE ORDINARY LIGHT WHILE RESPONDING TO POLARIZED LIGHT.





WHEN THE LIGHT LEVEL AT BOTH LIGHT SENSORS IS EQUAL THE LED IS OFF. WHEN THE LIGHT IS PARTIALLY OR COMPLETELY POLARIZED SO THAT PC1 RECEIVES MORE LIGHT THAN PC2, THE COMPARATOR WILL SWITCH THE LED ON. SEE ELSEWHERE IN THIS BOOK FOR HOW TO ADD A RELAY TO CIRCUIT.

INTEGRATED LIGHT SENSORS

INTEGRATED LIGHT SENSORS COMBINE A LIGHT-SENSITIVE PHOTODIODE AND AMPLIFIER OR OSCILLATOR IN A MINIATURE PACKAGE WITH A BUILT-IN WINDOW OR LENS. SOME ARE ENCAPSULATED IN DYED PLASTIC THAT TRANSMITS NEAR INFRARED WHILE BLOCKING VISIBLE LIGHT.

LIGHT-TO-TONE SENSOR

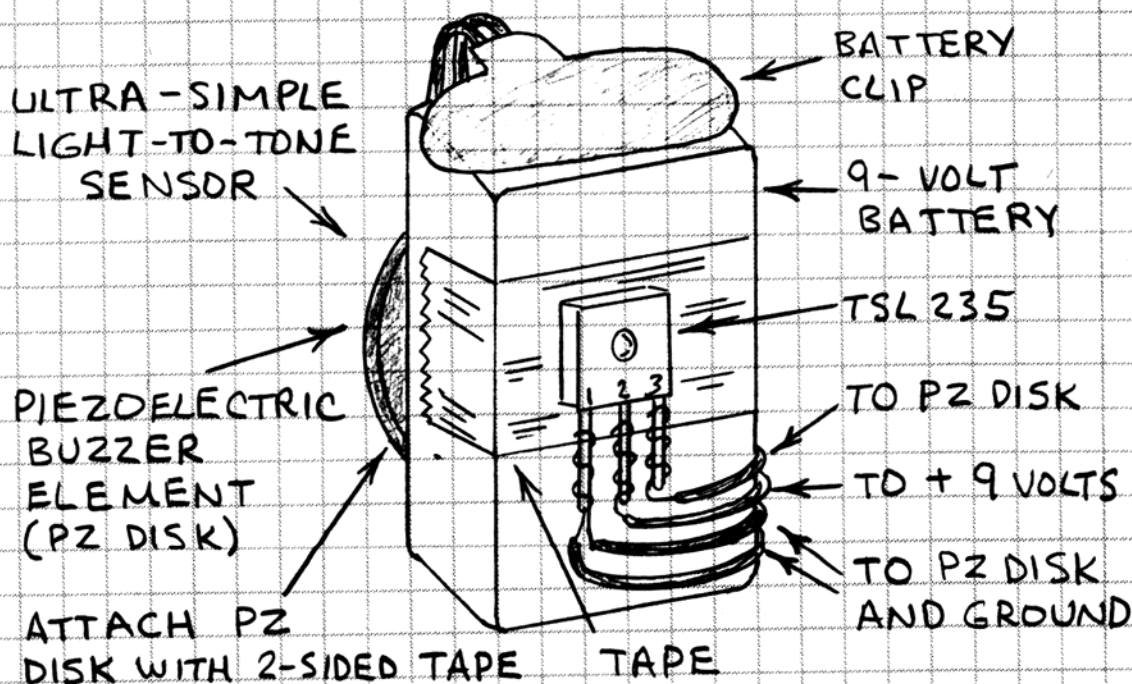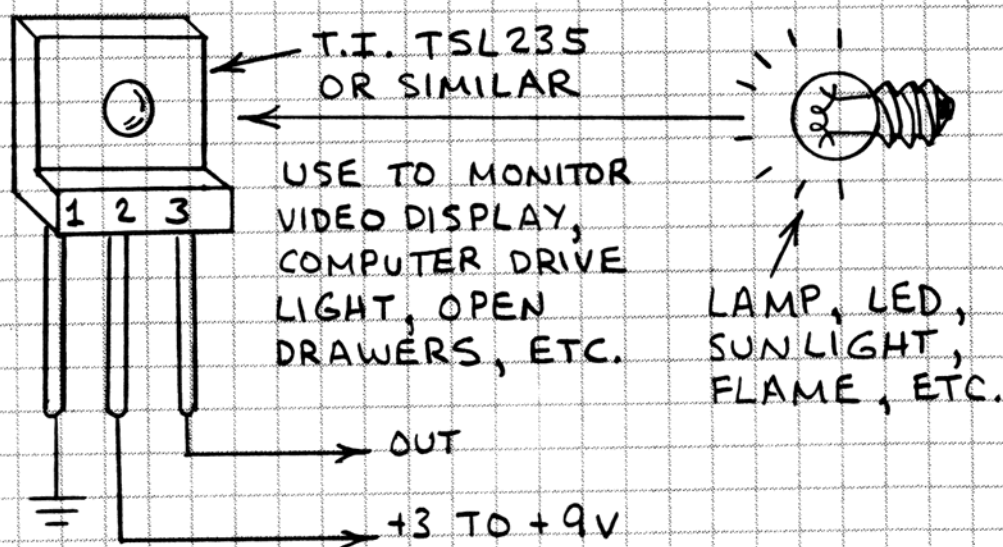


DARK TAPE ON TSL235 WILL REDUCE SENSITIVITY.

IR REMOTE CONTROL SENSOR

LED WILL GLOW OR PULSATE IF IR REMOTE CONTROL TRANSMITTER IS TRANSMITTING.


TV OR STEREO
REMOTE CONTROL

T.I. TSL250 LIGHT-TO-VOLTAGE
CONVERTER

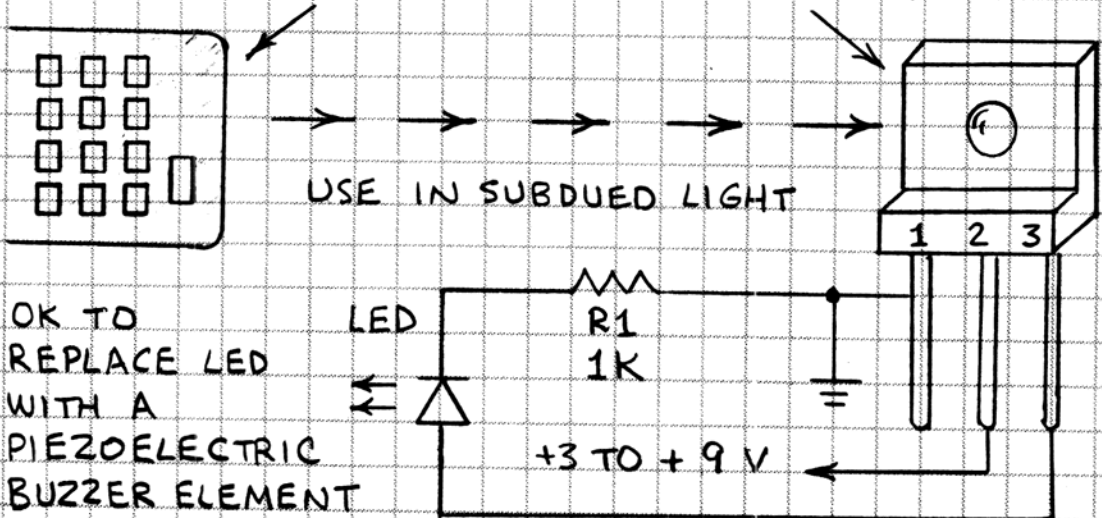

LIGHT-ACTIVATED RELAY

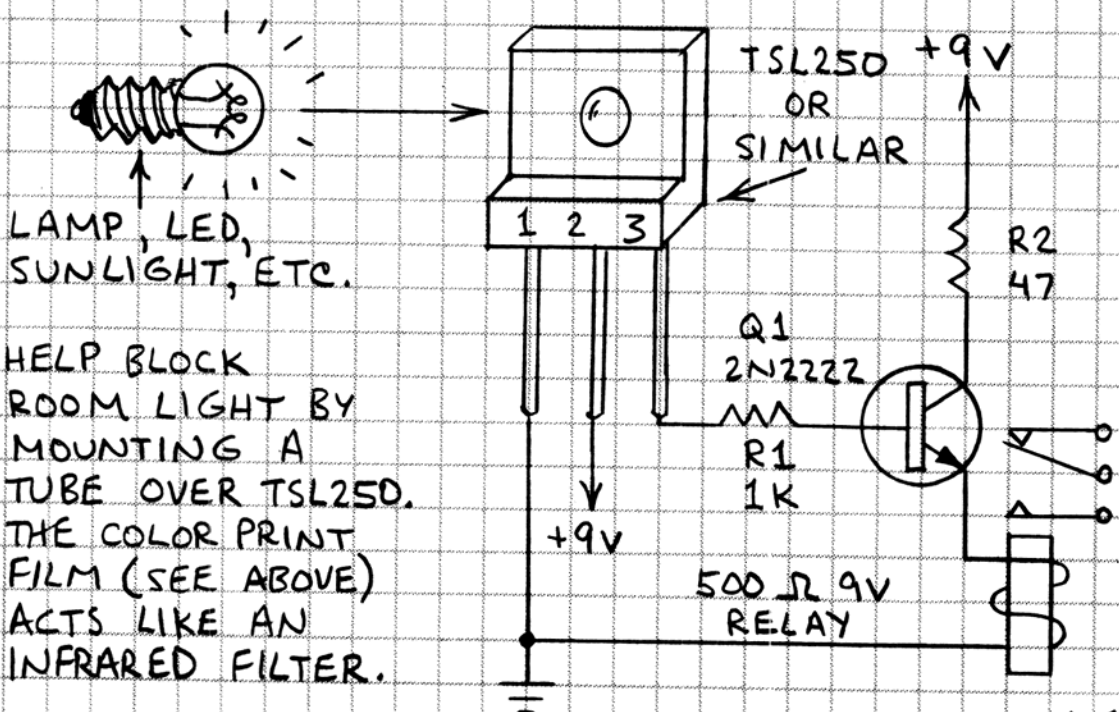
USE THIS CIRCUIT TO SENSE PEOPLE, OBJECTS, CARS, ETC. WORKS BEST AT NIGHT OR IN SUBDUED LIGHT. TO HELP BLOCK VISIBLE LIGHT PLACE PROCESSED COLOR PRINT FILM OVER TSL250.




OPTICAL LEVEL SENSORS

THESE OPTICAL LEVEL SENSORS HAVE AUDIBLE OUTPUTS. FOR BEST RESULTS ILLUMINATE SIDE OF LEVEL VIAL WITH LED AND PLACE LIGHT SENSOR BELOW VIAL. INSTALL IN LIGHT-TIGHT BOX.

VARIABLE TONE LEVEL SENSOR

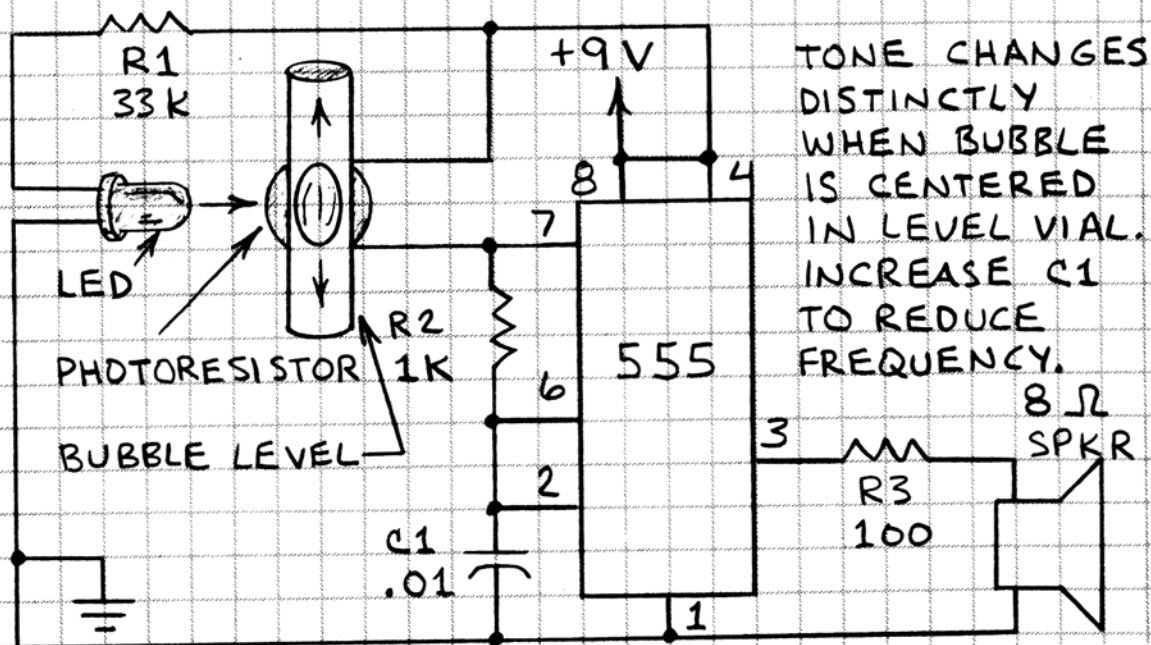

SWITCHED TONE LEVEL SENSOR

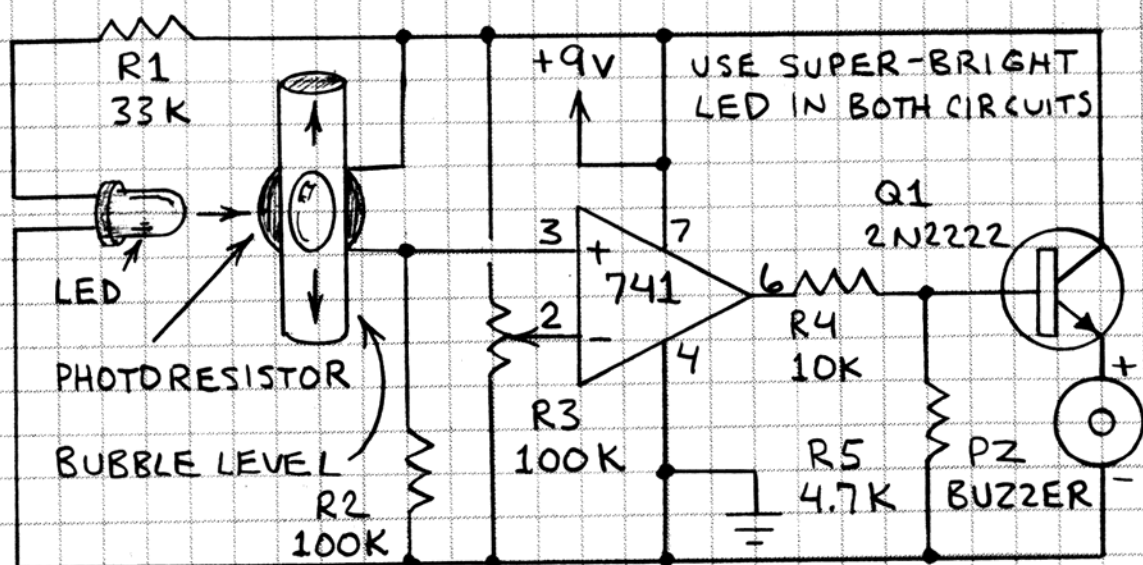


ADJUST R3 UNTIL PIEZOELECTRIC (PZ) BUZZER SOUNDS WHEN BUBBLE IS CENTERED IN VIAL.

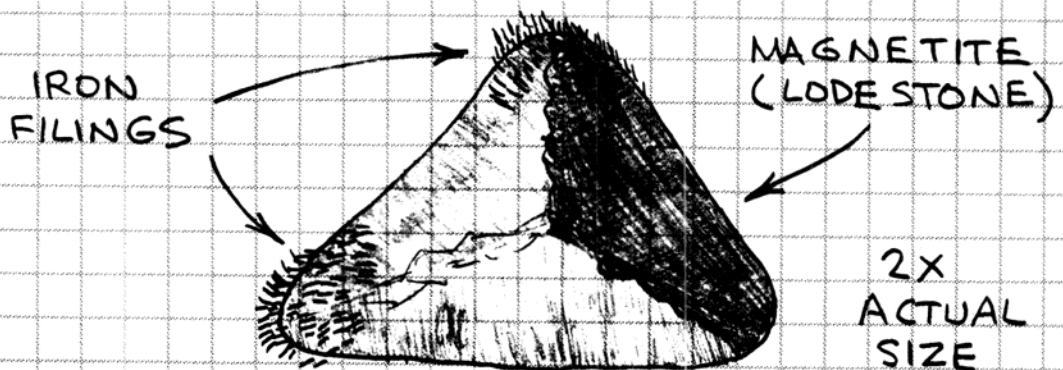II. MAGNET SENSOR PROJECTS

OVERVIEW

THERE IS A ROCK THAT ATTRACTS IRON. THIS MINERAL IS THE IRON OXIDE (Fe_3O_4), ALSO KNOWN AS MAGNETITE. PIECES OF THIS MINERAL ARE NATURAL MAGNETS. HERE IS A SKETCH OF A PIECE OF MAGNETITE ON MY DESK AS I WRITE:





NATURAL MAGNETS ARE CALLED LODESTONES. THIS NAME COMES FROM "LEADING STONE," WHICH REFERS TO THE FACT THE SAME SIDE OF A LODESTONE SUSPENDED FROM A STRING ALWAYS POINTS NORTH. THIS DISCOVERY LED TO THE INVENTION OF THE COMPASS, THE FIRST WIDESPREAD APPLICATION FOR NATURAL MAGNETS. THE COMPASS GAVE SAILORS AND EXPLORERS A VITALLY IMPORTANT NAVIGATIONAL TOOL.

THERE ARE AT LEAST TWO STORIES ABOUT THE ORIGIN OF THE WORD "MAGNET." ACCORDING TO THE ROMAN WRITER LUCRETIUS¹ THE WORD COMES FROM MAGNESIA, THE GREEK PROVINCE WHERE LODESTONES WERE FOUND. PLINY THE ELDER² WROTE THAT THE NAME CAME FROM MAGNES, A GREEK SHEPHERD. THE NAILS IN HIS SHOES AND THE IRON TIP OF HIS STAFF WERE ATTRACTED TO A FIELD OF MAGNETITE AS HE WALKED.

¹ 96 to 55 B.C. ² A.D. 23 to 79

MAGNETIC FIELDS

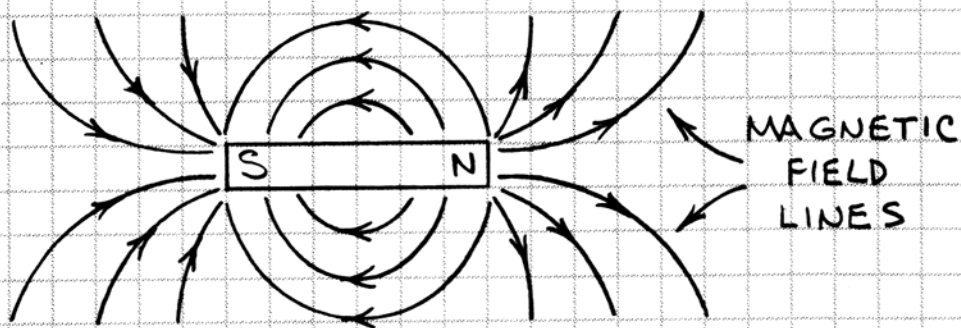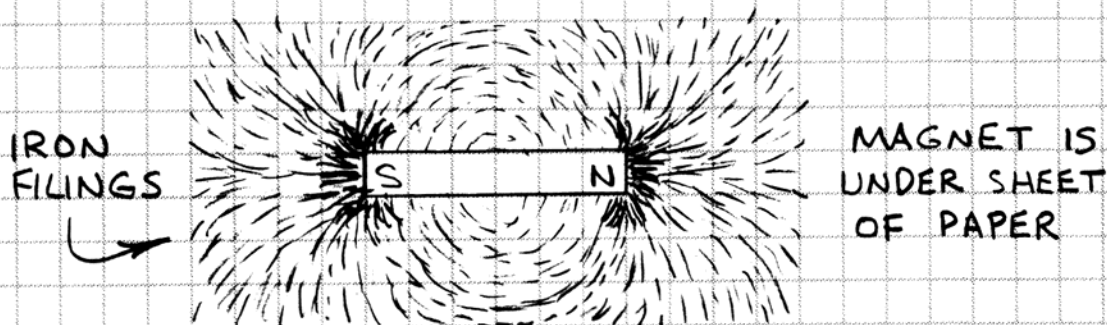THE REGION AROUND A MAGNET THAT INFLUENCES EXTERNAL OBJECTS IS THE MAGNETIC FIELD OF THE MAGNET. THE MAGNETIC FIELD AROUND A MAGNET FORMS AN ORGANIZED PATTERN. THIS PATTERN CAN BE MADE VISIBLE BY SPRINKLING IRON FILINGS ON A SHEET OF WHITE PAPER LYING ON A BAR MAGNET.




MAGNETIC FIELD LINES ARE MAPPED WITH A COMPASS.

MAGNETIC POLES


A MAGNET'S FORCE IS CONCENTRATED AT POINTS CALLED POLES. IF A BAR MAGNET IS HUNG FROM A STRING, ONE END WILL EVENTUALLY POINT NORTH. THIS END IS THE MAGNET'S NORTH POLE. THE END OF THE MAGNET THAT POINTS SOUTH IS THE SOUTH POLE.

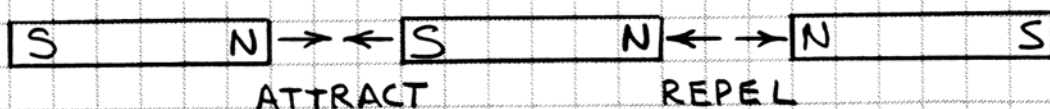THE OPPOSITE POLES OF TWO MAGNETS ATTRACT ONE ANOTHER. LIKE POLES REPEL.



MAGNETIC FIELD INTENSITY

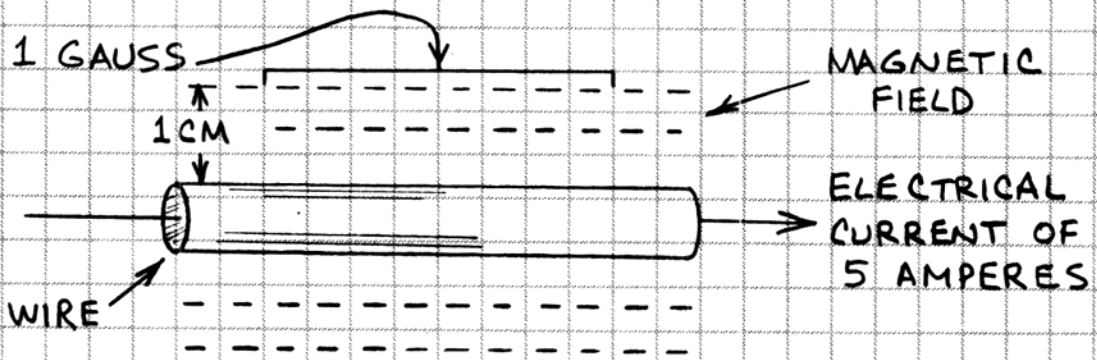THE INTENSITY OF A MAGNETIC FIELD IS MEASURED IN GAUSS. THE MAGNETIC FIELD 1 CENTIMETER FROM A STRAIGHT LENGTH OF WIRE THROUGH WHICH A CURRENT OF 5 AMPERES IS FLOWING IS 1 GAUSS. THE MAGNETIC FIELD OF VARIOUS MAGNETS CAN BE HUNDREDS OR EVEN THOUSANDS OF GAUSS.



THE TERM GAUSS HONORS CARL FRIEDRICH GAUSS (1777 TO 1855), THE GREAT MATHEMATICIAN.

IS THE EARTH A MAGNET?

EARTH HAS A MAGNETIC FIELD, BUT EARTH IS NOT A MAGNET. THE EARTH'S CORE IS BELIEVED TO BE MOLTEN METAL THAT IS MUCH TOO HOT TO BE MAGNETIC. THE MOST POPULAR THEORY IS THAT EARTH'S MAGNETIC FIELD IS CAUSED BY ELECTRICAL CURRENTS GENERATED BY ROTATION OF THE LIQUID CORE.

EARTH'S MAGNETIC FIELD


THE FORCE OF EARTH'S MAGNETIC FIELD IS ABOUT 0.3 GAUSS NEAR THE EQUATOR AND ABOUT 0.7 GAUSS NEAR THE POLES. THOUGH VERY WEAK, THE FIELD IS EASILY DETECTED BY A COMPASS.

EARTH'S GEOGRAPHIC POLES

EARTH ROTATES ABOUT AN IMAGINARY AXIS. THE POINTS WHERE THE AXIS MEETS EARTH'S SURFACE ARE THE NORTH AND SOUTH POLES.

EARTH'S MAGNETIC POLES

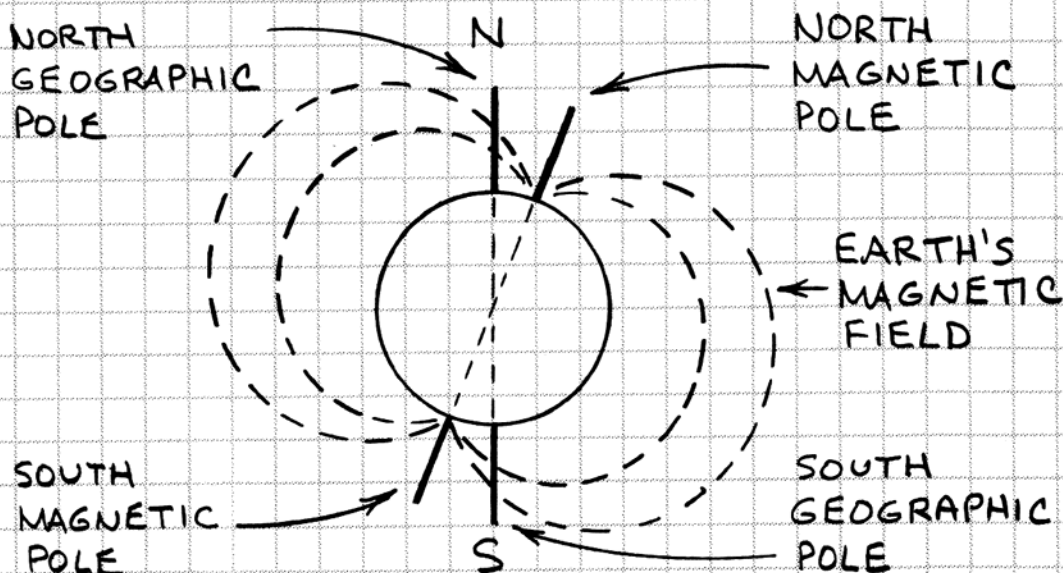EARTH ALSO HAS MAGNETIC POLES. THE MAGNETIC POLES DO NOT MATCH THE GEOGRAPHIC POLES. THE NORTHERNMOST MAGNETIC POLE IS NORTH OF CANADA'S HUDSON BAY. THE SOUTHERNMOST MAGNETIC POLE IS IN ANTARCTICA SOUTH OF TASMANIA.



EARTH'S CHANGING FIELD


THE FORCE OF EARTH'S MAGNETIC FIELD FLUCTUATES ON A DAILY BASIS. THE CHANGE NEAR THE EQUATOR IS ABOUT 0.0002 GAUSS EACH DAY. AT THE POLES THE CHANGE IS 0.0005 GAUSS EACH DAY. THE CHANGE IS SOMETIMES GREATER THAN THIS WHEN THE SUN IS VERY ACTIVE.

LIVING MAGNETS

THE BODIES OF MANY ANIMALS INCLUDE BITS OF MAGNETITE. RECENT DISCOVERIES HAVE SHOWN THAT MAGNETITE MAY ACT AS A KIND OF COMPASS THAT ASSISTS THE NAVIGATION OF VARIOUS BIRDS, INSECTS, FISH AND EVEN BACTERIA.

MAGNETIC BACTERIA

IN 1975 RICHARD BLACKMORE NOTICED THAT SOME BACTERIA FROM THE MUDDY BOTTOMS OF MARSHES ALWAYS MIGRATE TO ONE SIDE OF A DROP OF WATER. WHEN HE PLACED A MAGNET NEARBY, THE BACTERIA SWAM TOWARD THE SOUTH-SEEKING POLE AND AWAY FROM THE NORTH-SEEKING POLE. LATER IT WAS DISCOVERED THAT MAGNETIC BACTERIA ALIGN THEMSELVES WITH A MAGNETIC FIELD EVEN WHEN THEY ARE DEAD. MORE THAN A DOZEN KINDS OF MAGNETIC BACTERIA HAVE BEEN DISCOVERED. MOST LIVE IN MUD OR SILT UNDER BODIES OF WATER, AND SOME LIVE IN SOIL. THEY ARE COLLECTIVELY KNOWN AS MAGNETOTAXIC BACTERIA. THEY INCLUDE A STRING OF MICROSCOPIC MAGNETS CALLED MAGNETOSOMES.

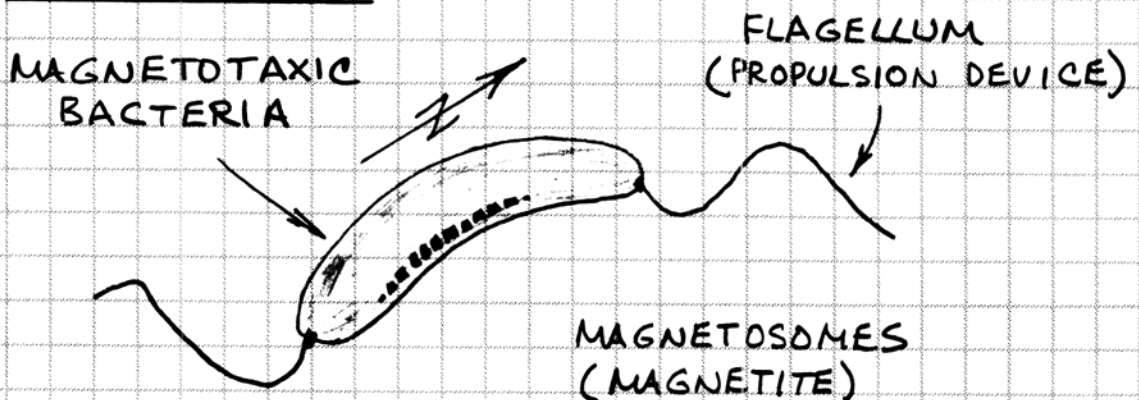

MAGNETOTAXIC BACTERIA IN THE NORTHERN HEMISPHERE SWIM NORTH. THOSE IN THE SOUTHERN HEMISPHERE SWIM SOUTH. THOSE NEAR THE EQUATOR SWIM IN EITHER DIRECTION.


APPLICATIONS FOR MAGNETS

1. DIRECT CURRENT (DC) MOTORS
2. ELECTRICAL GENERATORS
3. AUDIO SPEAKERS
4. AUDIO EAR AND HEAD PHONES
5. SEPARATING IRON AND STEEL SCRAP FROM NON-MAGNETIC MATERIALS
6. RETRIEVE IRON AND STEEL OBJECTS LOST IN BODIES OF WATER
7. RETRIEVE BROKEN DRILL HEADS FROM OIL AND GAS WELLS
8. COLLECT FILING CHIPS FROM DRILLED HOLES
9. TRAP BITS OF METAL IN STOMACHS OF COWS ("COW MAGNETS")
10. ERASE DATA STORED ON MAGNETIC TAPE
11. CABINET LATCHES
12. TEMPORARILY MOUNT ANTENNA ON CAR ROOF
13. TEMPORARILY MOUNT SIGNS ON CARS
14. MOUNTING, SUPPORTING AND HOLDING SIGNS, GADGETS AND OBJECTS IN HOMES AND OFFICES
15. COLLECTING NAILS LOST IN SOIL
16. PAPER CLIP HOLDER
17. SCIENTIFIC RESEARCH AND DEVELOPMENT
18. I'VE USED A MAGNET TO FIND BITS OF IRON METEORITE INSIDE A LARGE METEOR CRATER


MAGNET CONFIGURATIONS

AMONG THE MANY MAGNET CONFIGURATIONS
ARE THESE:

BAR

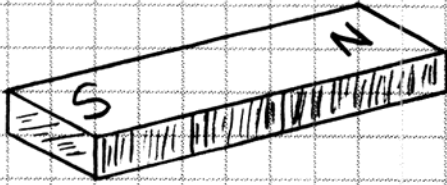


DISK

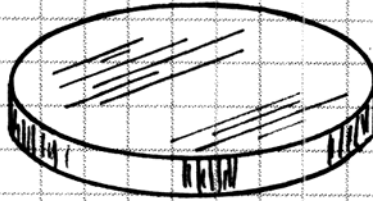


HORSE SHOE




CYLINDER

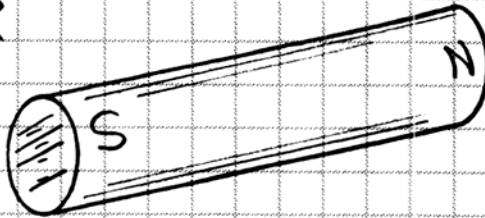

RING

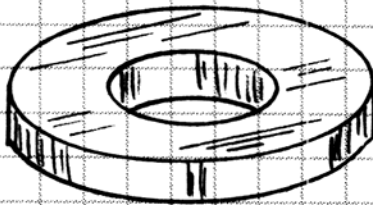


FLEXIBLE

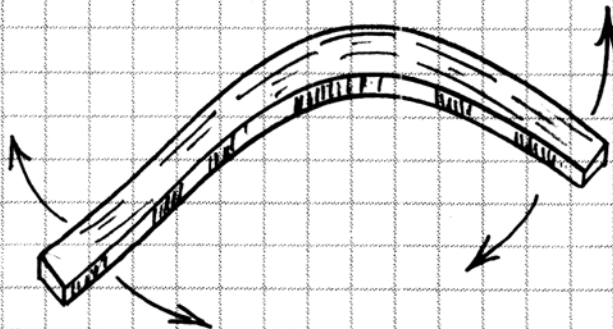

TEMPORARY MAGNETS

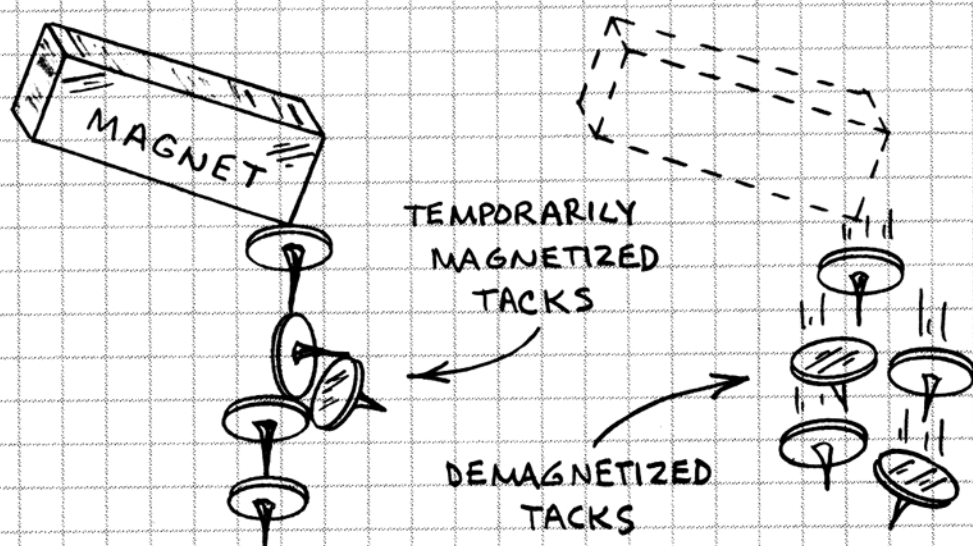SOFT IRON AND STEEL CAN BE MAGNETIZED, BUT DO NOT NECESSARILY STAY MAGNETIZED.



PERMANENT MAGNETS

HARDENED IRON AND STEEL AND CERTAIN METAL ALLOYS STAY MAGNETIZED INDEFINITELY. CERAMIC MAGNETS AND MAGNETIC RUBBER AND PLASTIC CONTAIN PARTICLES OF MAGNETIC MATERIAL. HERE ARE SOME COMMON PERMANENT MAGNET MATERIALS AND THE STRENGTH OF THEIR MAGNETIC FIELD:

ALNICO (VARIOUS ALLOYS OF ALUMINUM, NICKEL AND COBALT) — 5,500 TO 13,100 GAUSS

CHROMIUM STEEL — 9,700 GAUSS

RARE EARTH COBALT — 8,100 GAUSS

CERAMIC — 2,200 TO 3,500 GAUSS


PLASTIC — 1,400 GAUSS

RUBBER — 1,300 TO 2,300 GAUSS

DATA: "HANDBOOK OF CHEMISTRY AND PHYSICS" (CRC PRESS).

USING AND CARING FOR MAGNETS

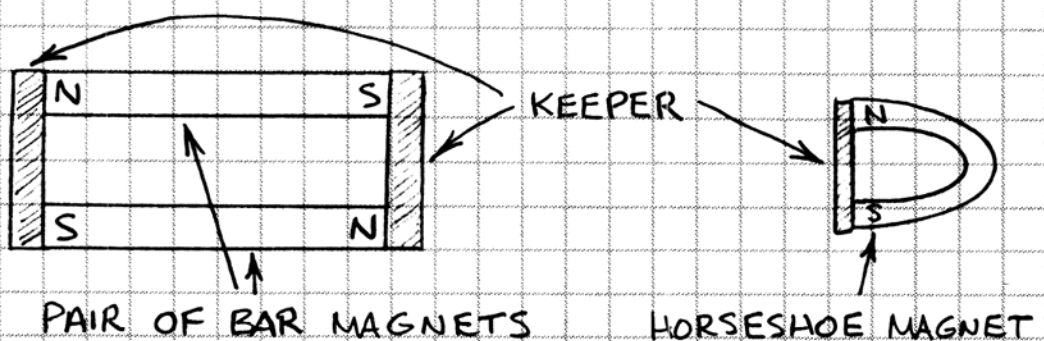
1. THE ABILITY OF A MAGNET TO LIFT A LOAD IS REDUCED BY SOIL, DUST, PAINT AND RUST ON THE MAGNET OR LOAD.
2. LIFTING ABILITY IS REDUCED WHEN THE LOAD IS VERY THIN (CANS, ETC.) OR HAS A ROUGH OR IRREGULAR SURFACE.
3. AVOID DROPPING OR STRIKING A MAGNET. IT MIGHT BREAK OR BECOME DEMAGNETIZED.
4. FORCING THE SAME POLES OF TWO MAGNETS TOGETHER CAN PARTIALLY DEMAGNETIZE BOTH MAGNETS.
5. ALWAYS SEPARATE TWO MAGNETS BY PULLING THEM AWAY FROM ONE ANOTHER. DO NOT SLIDE ONE MAGNET AGAINST ANOTHER TO SEPARATE THEM AS THIS MIGHT SHARPLY DEMAGNETIZE ONE OR BOTH MAGNETS. TRY TO KEEP SEPARATED MAGNETS FROM SLAMMING BACK TOGETHER.
6. AVOID PLACING A MAGNET NEAR A STRONG MAGNETIC FIELD FROM A MOTOR.
7. A "KEEPER" OF SOFT IRON WILL EXTEND THE LIFE OF A MAGNET.



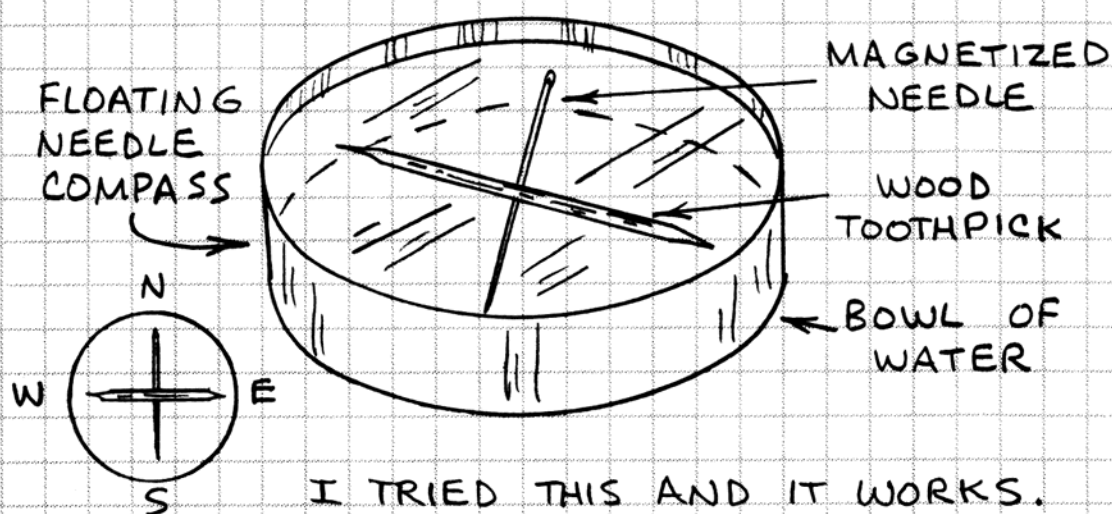8. CAUTION! KEEP MAGNETS AWAY FROM MAGNETIC MEDIA (COMPUTER DISKS, CREDIT CARDS, RECORDING TAPE, ETC.)! ALSO KEEP MAGNETS AWAY FROM MECHANICAL WATCHES.

THE COMPASS


THE SIMPLEST COMPASS IS A MAGNETIZED IRON NEEDLE OR POINTER FREE TO ROTATE ABOUT A PIVOT. THE NEEDLE WILL ALIGN ITSELF ALONG THE EARTH'S MAGNETIC FIELD. SOME HISTORIANS BELIEVE THE FIRST COMPASS WAS A LODESTONE ATOP A SMALL PIECE OF WOOD FLOATING IN A BOWL OF WATER. I TRIED THIS BY PLACING A LODESTONE ON A SMALL SQUARE OF WOOD FLOATING ON WATER IN A PLASTIC BOX. BUT THIS "COMPASS" WORKS ONLY WHEN THE WATER IS STILL. IT MIGHT WORK ON LAND, BUT IT WOULD NOT WORK WELL IN A BOAT. THE FIRST PRACTICAL COMPASSES ARE BELIEVED TO HAVE BEEN MAGNETIZED NEEDLES INSERTED CROSSWAYS THROUGH A FLOATING REED OR SPLINTER. THE NEEDLE WAS MAGNETIZED BY STROKING IT AGAINST A LODESTONE.



I TRIED THIS AND IT WORKS. FIRST I STROKED A STEEL SEWING NEEDLE AGAINST A LODESTONE. SINCE THE NEEDLE ATTRACTED IRON FILINGS, IT WAS MAGNETIZED. I USED PLIERS TO FORCE THE NEEDLE THROUGH A WOOD TOOTHPICK. CAUTION: USE CARE TO AVOID BREAKING THE NEEDLE OR PRESSING IT INTO A FINGER! WHEN FLOATED ON WATER, THE NEEDLE AND TOOTHPICK ARRANGEMENT WILL SLOWLY ROTATE UNTIL THE NEEDLE POINTS NORTH AND SOUTH AND THE TOOTHPICK EAST AND WEST.

MAPPING A MAGNETIC FIELD

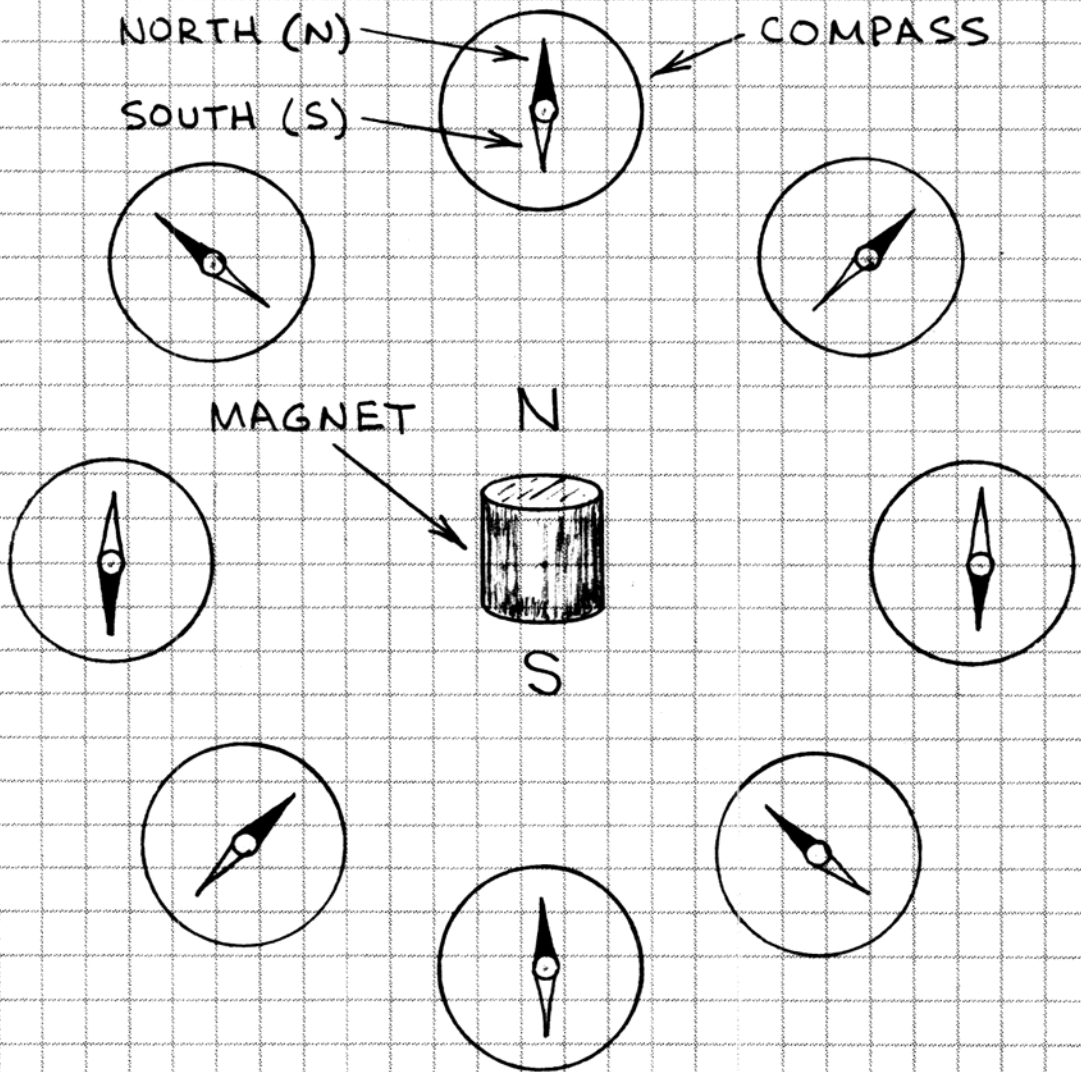A COMPASS CAN BE USED TO MAP A MAGNET'S FIELD. THIS IS OFTEN MORE PRACTICAL THAN USING IRON FILINGS.



NOTICE HOW THE NORTH END OF THE COMPASS NEEDLE POINTS TO THE SOUTH POLE OF THE MAGNET.


TIP: OPPOSITES ATTRACT, UNLIKES REPEL.

A COMPASS WILL RESPOND TO A MAGNET UP TO 30 CENTIMETERS (ABOUT 1 FOOT) AWAY.




ELECTROMAGNET

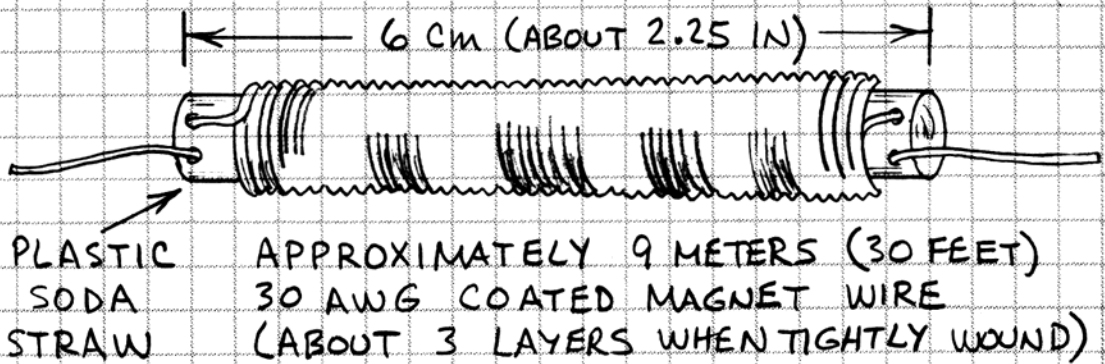AN ELECTRICAL CURRENT FLOWING THROUGH A LOOP OF WIRE CREATES A MAGNETIC FIELD. THE WEAK FIELD OF A SINGLE LOOP CAN BE GREATLY INCREASED BY WINDING A COIL OF MANY LOOPS.



INSERT STEEL* INSIDE THIS COIL AND CONNECT A 6-VOLT LANTERN BATTERY TO WIRE LEADS. USE FLAME OR FINE GRIT SAND PAPER TO REMOVE INSULATION FROM ENDS OF WIRE. *NAIL, ETC.


SOLENOID

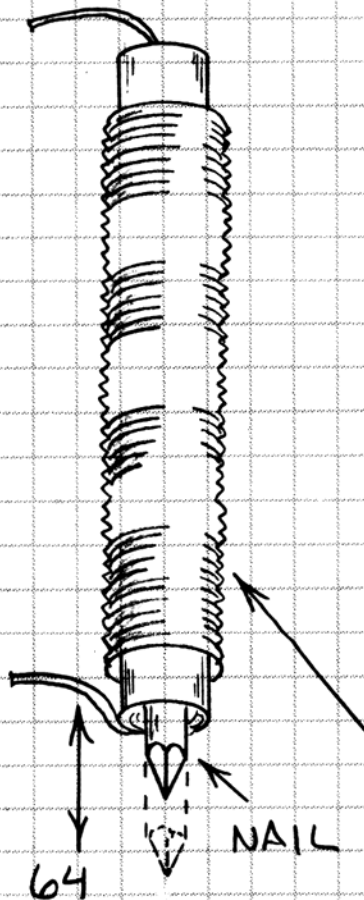


THE ELECTROMAGNET SHOWN ABOVE CAN ALSO FUNCTION AS A SOLENOID OR "SUCTION MAGNET." PLACE COIL IN A VERTICAL POSITION. ALLOW NAIL TO TOUCH SURFACE BELOW COIL. WHEN CURRENT IS APPLIED TO THE COIL, THE NAIL WILL BE RAPIDLY PULLED UP INTO THE COIL BY THE COIL'S MAGNETIC FIELD. SOLENOIDS RELEASE LATCHES, CLOSE VALVES, LOCK DOORS, ETC.

RESISTANCE OF PROTOTYPE COIL IS 3.1Ω . AT 6 VOLTS THE CURRENT IS $6/3.1$ OR 1.9 AMPS. USE SOLENOID SPARINGLY TO PRESERVE BATTERY LIFE.

ELECTROMAGNETIC RELAY

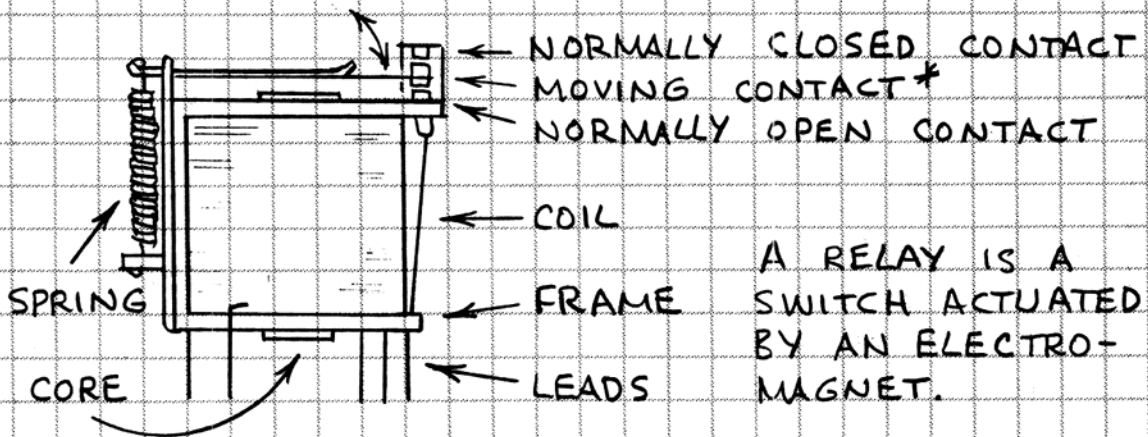

* OPERATING POINT

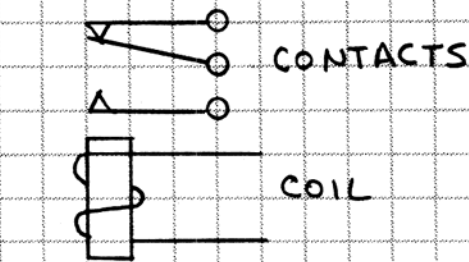


RELAY DIAGRAM

RELAYS CAN BE ACTUATED BY LOW-VOLTAGE TRANSISTOR AND IC CIRCUITS. THEIR CONTACTS CAN CONTROL VOLTAGES AND CURRENTS THAT WOULD DESTROY TRANSISTORS AND ICs.

RELAY DRIVER

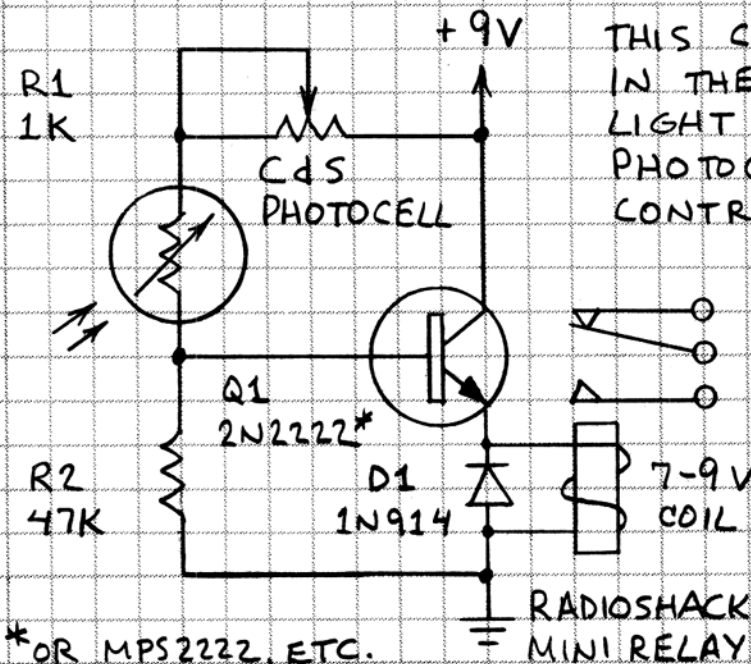THIS CIRCUIT SHOWS HOW A SINGLE TRANSISTOR CAN CONTROL A RELAY.




THIS CIRCUIT PULLS IN THE RELAY WHEN LIGHT STRIKES THE PHOTOCELL. R1 CONTROLS SENSITIVITY.

D1 PROTECTS Q1 FROM HIGH VOLTAGE SPIKE THAT OCCURS WHEN RELAY IS SWITCHED OFF.


*OR MPS2222, ETC.

MAGNET SWITCHES

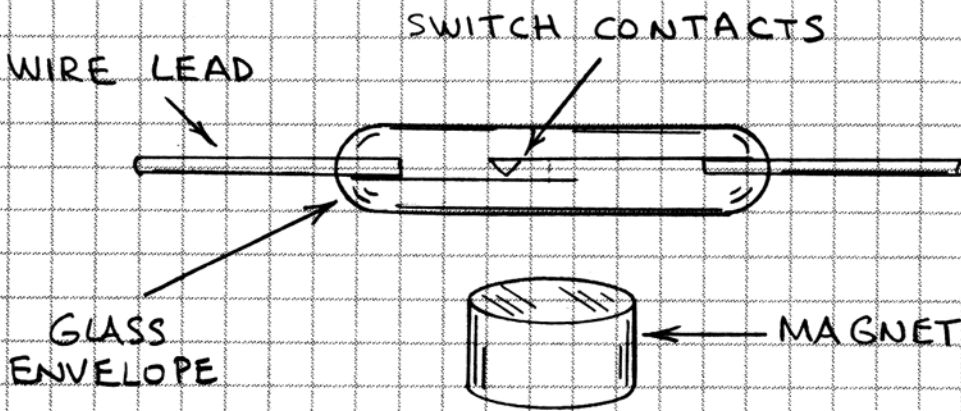A MAGNET SWITCH IS A REED SWITCH THAT HAS A FLEXIBLE MEMBER THAT BENDS TOWARD OR AWAY FROM A RIGID MEMBER WHEN A MAGNET IS NEAR.



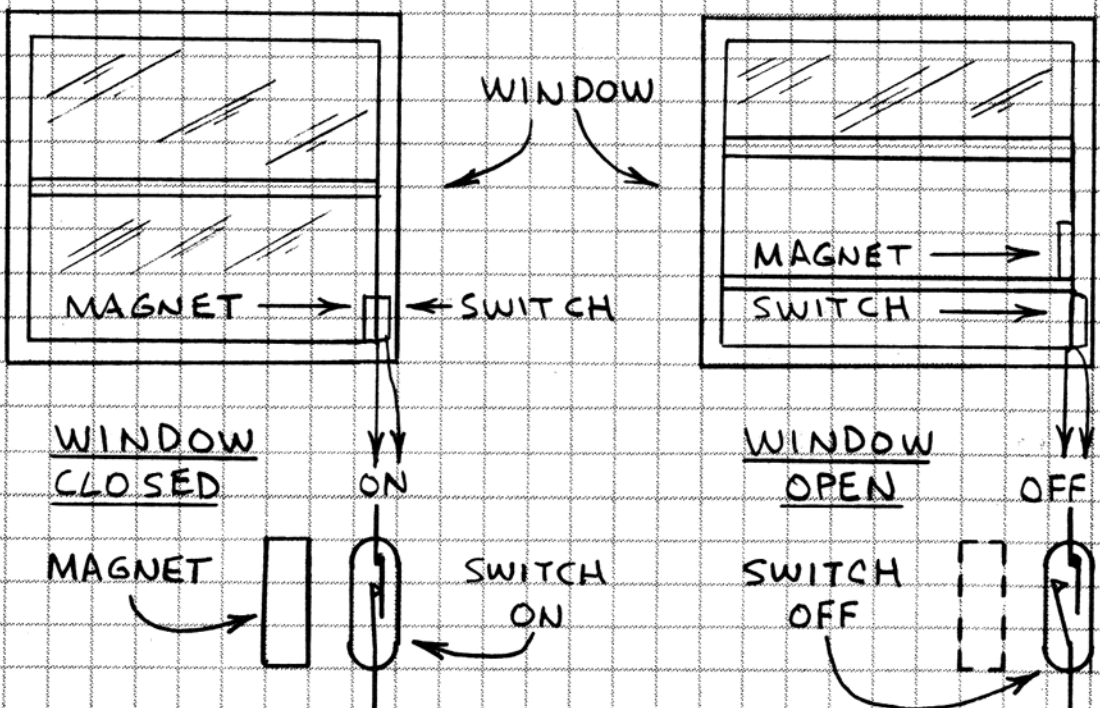
MAGNET SWITCHES ARE VERY RELIABLE AND REQUIRE NO POWER SUPPLY. THEY ARE OFTEN USED TO DETECT OPEN DOORS AND WINDOWS IN SECURITY ALARM SYSTEMS. FOR THESE USES THE SWITCH IS USUALLY INSTALLED IN A PLASTIC HOUSING WITH EXTERNAL WIRE LEADS OR SCREW TERMINALS. THE ACTUATING MAGNET IS INSTALLED IN A SIMILAR HOUSING.



MAGNET SWITCH INTERFACE

THIS SIMPLE TRANSISTOR CIRCUIT WILL SWITCH ON LED 2 WHEN A MAGNET IS NEAR SW1. LED 1 IS SWITCHED ON WHEN THE MAGNET IS REMOVED.

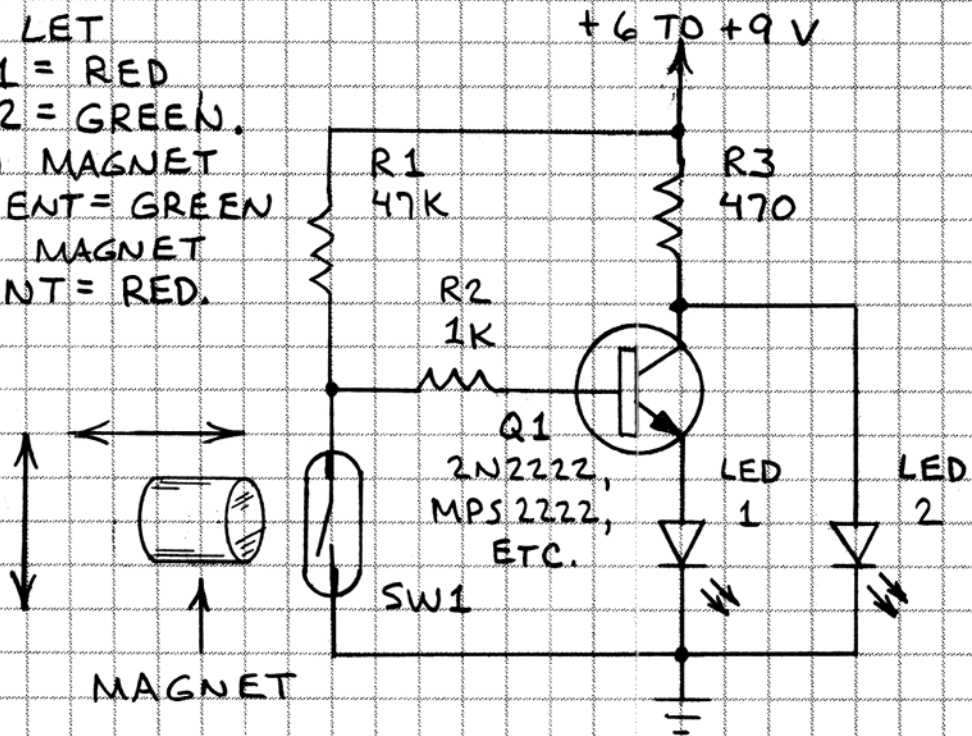
TIP: LET
LED 1 = RED
LED 2 = GREEN.
THEN MAGNET
PRESENT = GREEN
AND MAGNET
ABSENT = RED.



MAGNET	LED 1	LED 2
YES	OFF	ON
NO	ON	OFF

SWITCH WILL RESPOND TO EITHER NORTH OR SOUTH POLE OF MAGNET.


MAGNET ACTUATED TONE

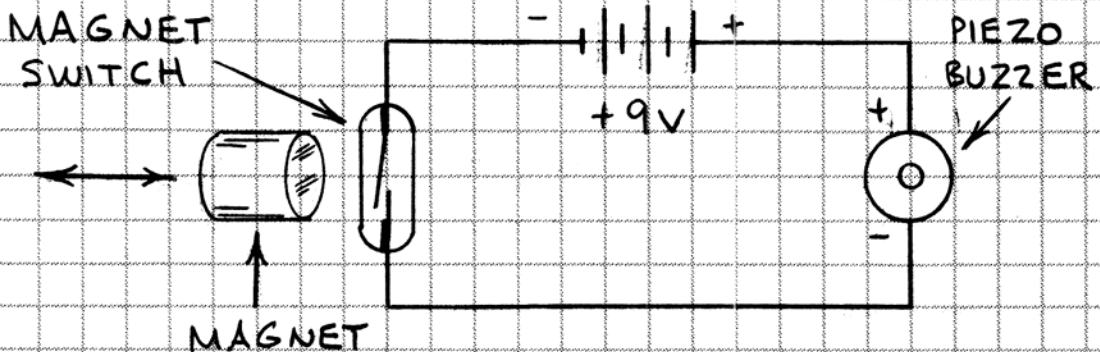

PLACE MAGNET NEAR SWITCH TO ACTIVATE TONE. OK TO USE LAMP INSTEAD OF BUZZER.

THE HALL EFFECT

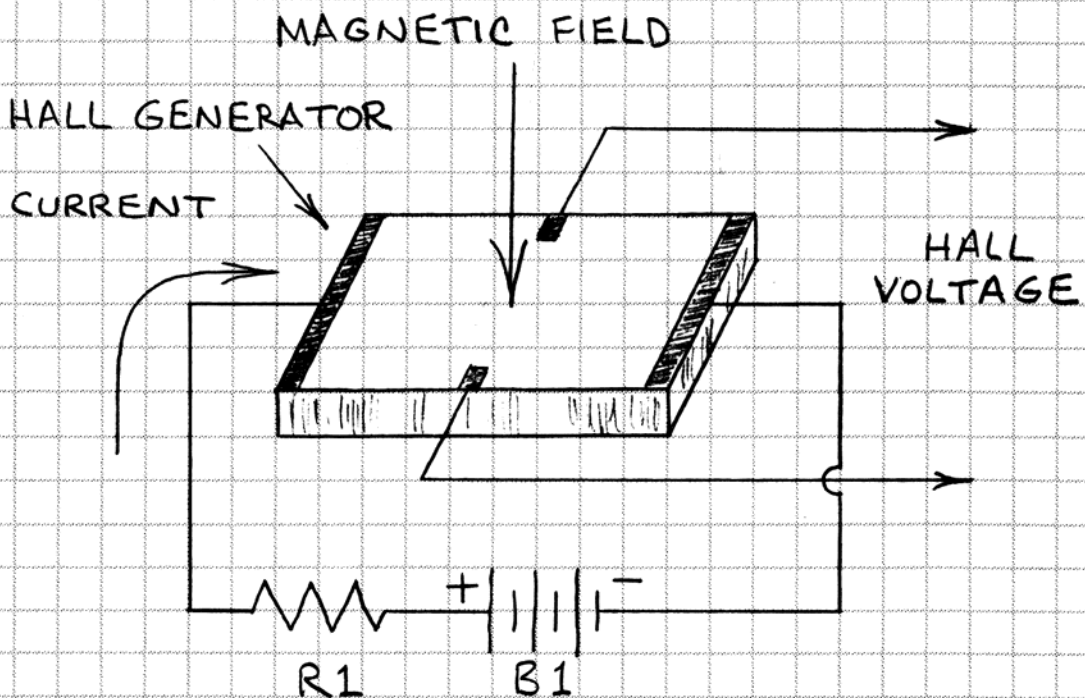IN OCTOBER 1879, THE PHYSICIST EDWARD HALL DISCOVERED THE EFFECT THAT BEARS HIS NAME. HALL FOUND THAT A STRONG MAGNETIC FIELD CAUSED A VOLTAGE TO APPEAR ACROSS A THIN FILM OF GOLD THROUGH WHICH AN ELECTRICAL CURRENT WAS FLOWING. THIS VOLTAGE IS CALLED THE HALL VOLTAGE. IT IS PROPORTIONAL TO THE MAGNETIC FIELD TIMES THE CURRENT.



RESISTOR R1 LIMITS (RESTRICTS) THE CURRENT FROM BATTERY B1 TO A SAFE VALUE. TOO MUCH CURRENT WILL OVERHEAT AND DAMAGE THE HALL GENERATOR.


THE HALL EFFECT OCCURS IN CONDUCTORS AND SEMICONDUCTORS. THE HALL VOLTAGE PRODUCED BY CONDUCTORS IS MUCH TOO SMALL FOR PRACTICAL APPLICATIONS. THE HALL VOLTAGE IS MUCH HIGHER IN SEMICONDUCTORS. GALLIUM ARSENIDE AND OTHER SEMICONDUCTORS PRODUCE THE MOST VOLTAGE. BUT SILICON IS PREFERRED SINCE IT IS STURDIER AND EASIER TO MANUFACTURE.

APPLICATIONS FOR HALL SENSORS

HALL SENSORS HAVE MANY APPLICATIONS IN ELECTRONICS AND SENSING. THEY CAN BE USED INSTEAD OF LIGHT SENSORS IN APPLICATIONS WHERE THE SENSOR MIGHT BECOME DIRTY OR EXPOSED TO BRIGHT LIGHT. HERE ARE SOME OF THE MOST COMMON APPLICATIONS:


MAGNETIC FIELD SENSOR

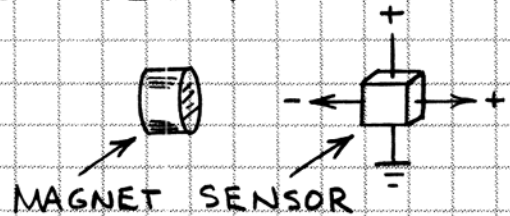HALL SENSORS CAN DETECT PRESENCE OR ABSENCE OF SMALL MAGNETS.




ELECTROMAGNETIC FIELD SENSOR

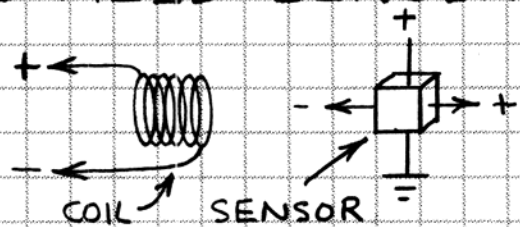HALL SENSORS CAN DETECT MAGNETIC FIELD CAUSED BY ELECTRICAL CURRENT.




BOUNCELESS SWITCH

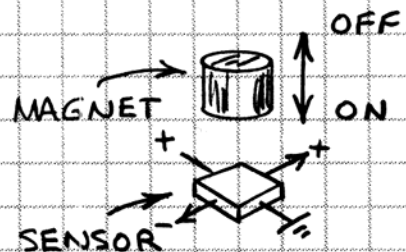SWITCH MADE WITH HALL SENSOR DOES NOT HAVE MECHANICAL "BOUNCE" OF CONVENTIONAL SWITCH.




FERROUS METAL DETECTOR

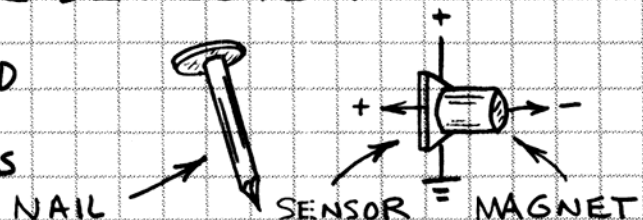HALL SENSOR BACKED BY SMALL MAGNET WILL DETECT FERROUS METAL.



GEAR TOOTH SENSOR

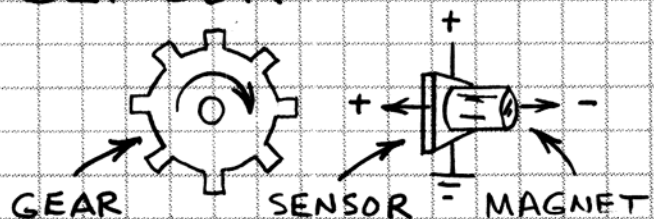
HALL SENSOR BACKED BY SMALL MAGNET WILL DETECT TEETH ON A GEAR.




HALL SENSOR BASICS

MOST HALL SENSORS ARE MANUFACTURED WITH A BUILT-IN AMPLIFIER OR LOGIC CIRCUIT TO MAKE THEM EASIER TO USE. IT'S HELPFUL TO UNDERSTAND HOW THE SENSOR IS CONNECTED TO THESE INTERFACE CIRCUITS.

BASIC HALL SENSOR

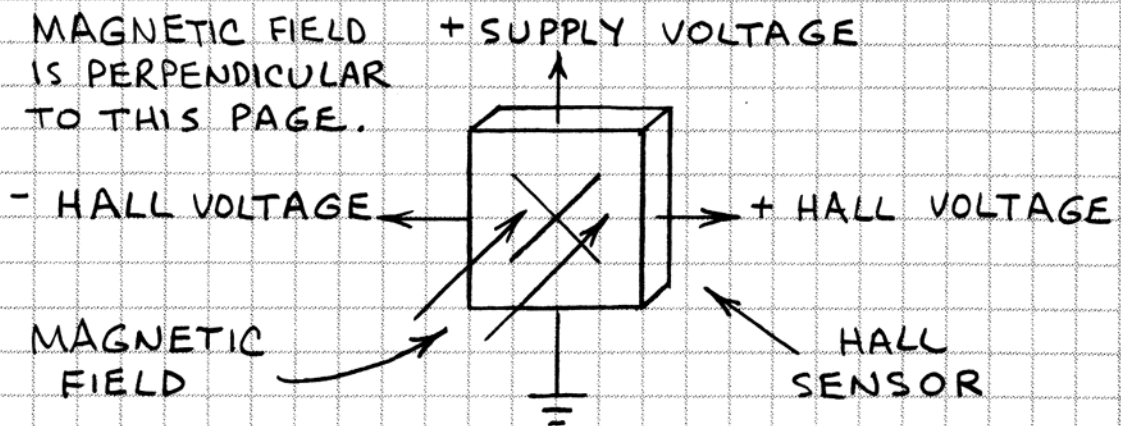

BASIC HALL SENSOR CIRCUIT

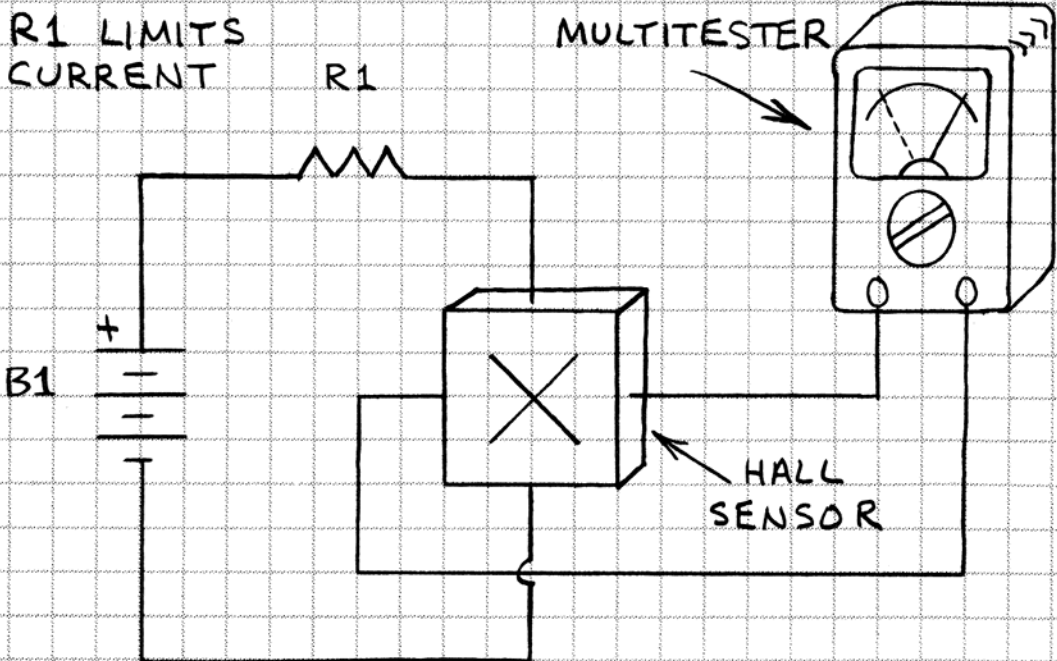

THIS CIRCUIT GENERATES AN OUTPUT VOLTAGE WHEN A MAGNET IS PLACED NEAR THE HALL EFFECT SENSOR.

HALL SENSOR OUTPUT VOLTAGE

THE HALL VOLTAGE IS PROPORTIONAL TO THE APPLIED MAGNETIC FIELD ACCORDING TO:

$$V_H = R_H \times \left(\frac{I}{t} \times B \right)$$

WHERE,

V_H IS THE HALL VOLTAGE,


R_H IS THE HALL EFFECT COEFFICIENT,

I IS THE CURRENT THROUGH THE SENSOR,


t IS THE THICKNESS OF THE SENSOR, AND

B IS THE PERPENDICULAR MAGNETIC FIELD.

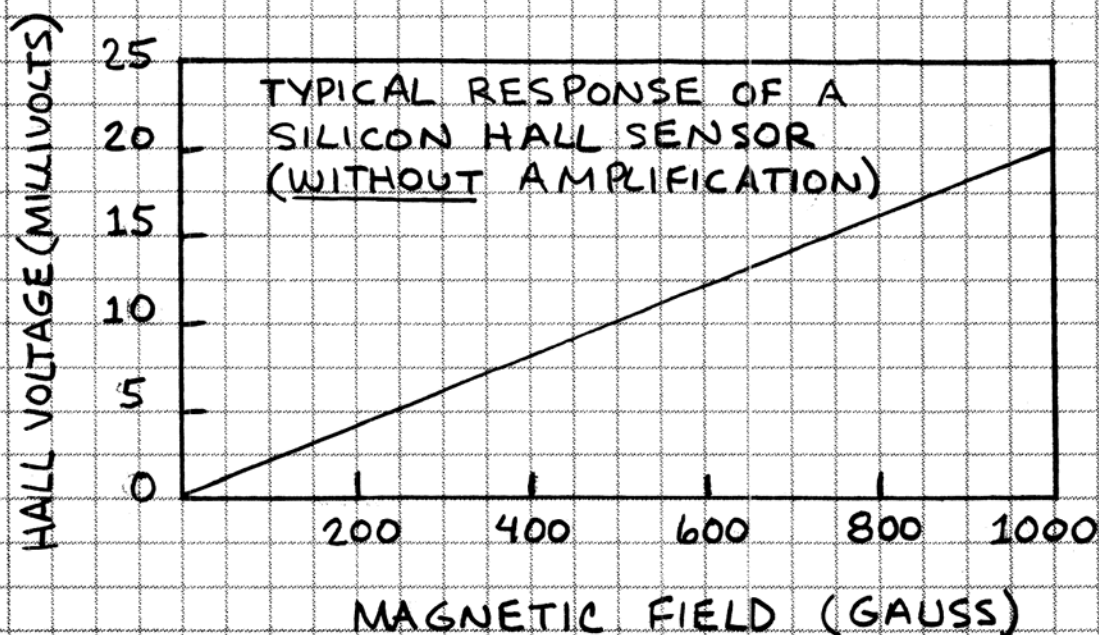
IN PRACTICAL TERMS, THE HALL VOLTAGE IN A TYPICAL SILICON HALL SENSOR IS ABOUT 18 MICROVOLTS (0.000018 VOLT) PER GAUSS WHEN THE SUPPLY IS 3 VOLTS. THIS IS SUCH A SMALL VOLTAGE THAT HALL SENSORS ARE USUALLY MANUFACTURED WITH A BUILT-IN AMPLIFIER OR LOGIC CIRCUIT.



HALL SENSOR + LOGIC CIRCUIT

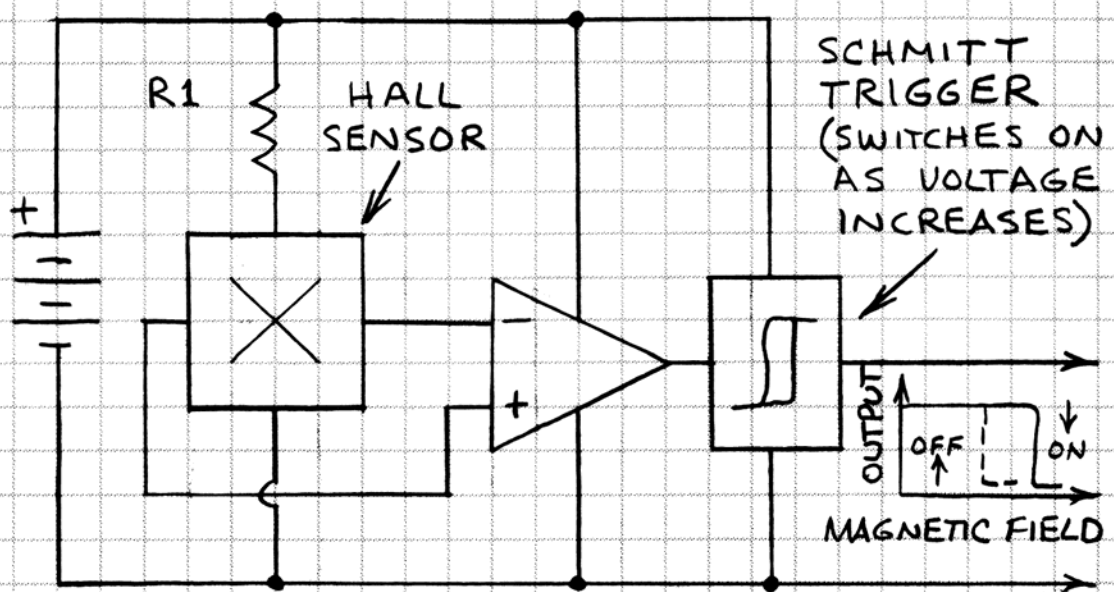

INTEGRATED DIGITAL HALL SENSOR

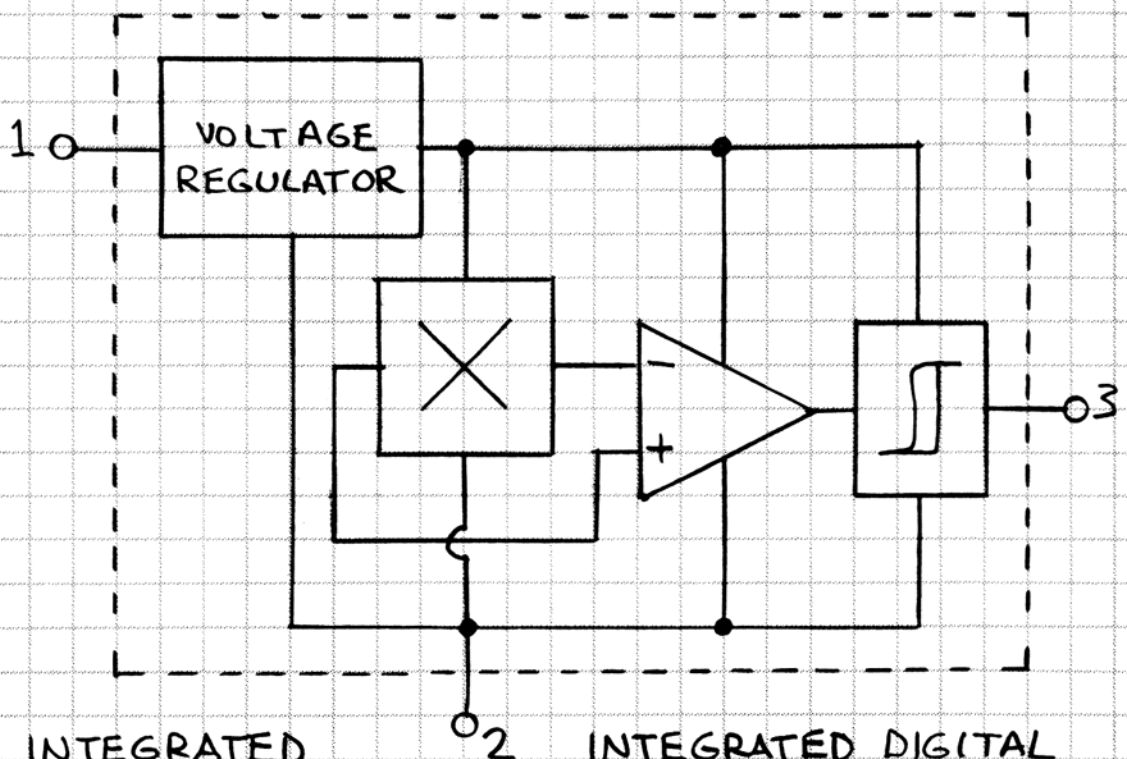


INTEGRATED
DIGITAL HALL
SENSOR PIN
DESIGNATIONS:




1. + SUPPLY
2. GROUND
3. OUTPUT

INTEGRATED DIGITAL
HALL SENSORS USUALLY
INCLUDE AN OUTPUT
TRANSISTOR BETWEEN
THE SCHMITT TRIGGER.
SOME STAY "ON" (LATCHED)
WHEN MAGNET REMOVED.

HALL SENSOR + AMPLIFIER

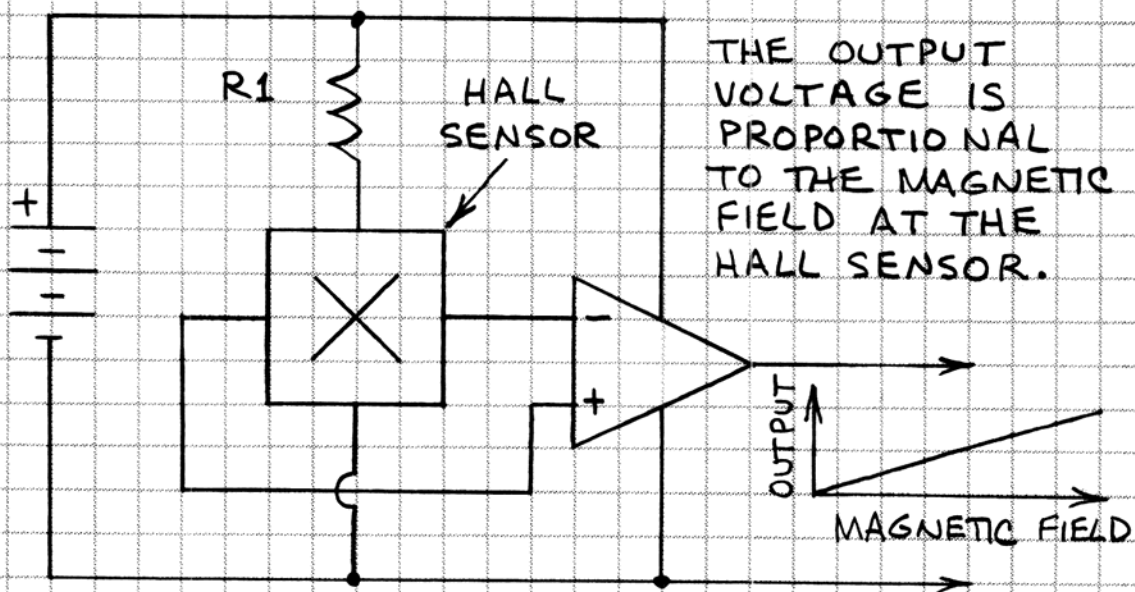

INTEGRATED LINEAR HALL SENSOR

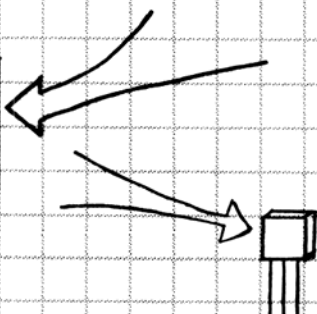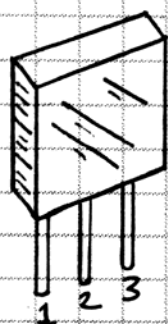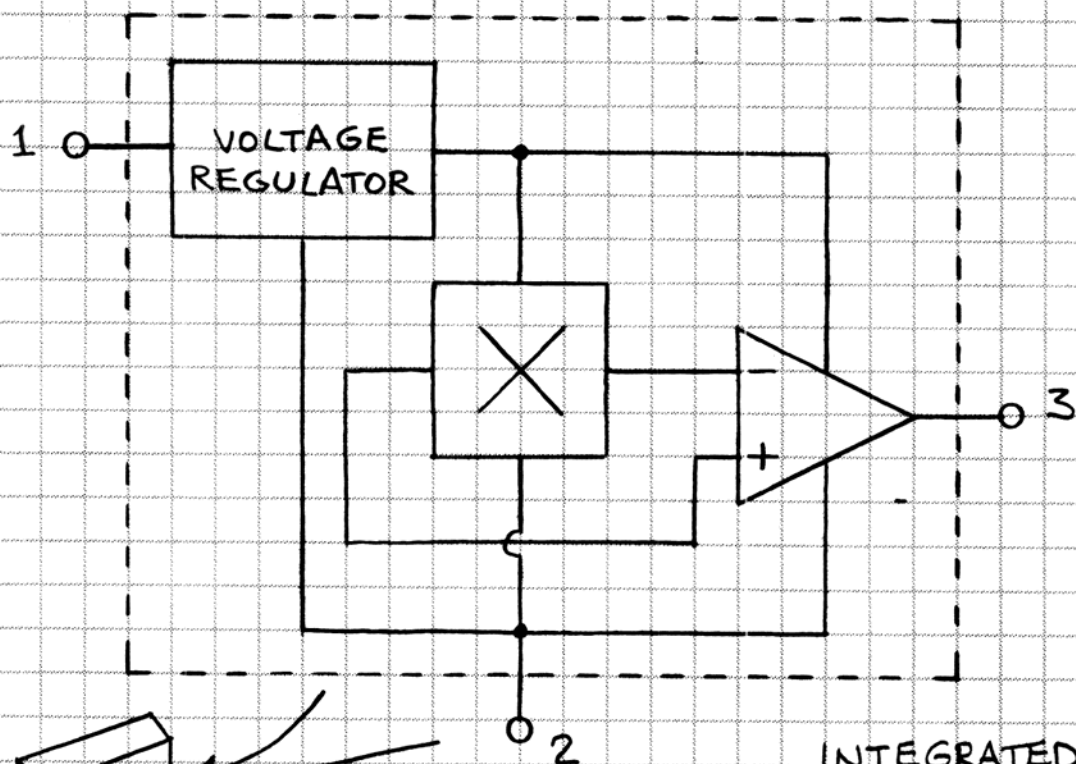


ACTUAL
SIZE
HALL
SENSOR

INTEGRATED
LINEAR HALL
SENSOR PIN
DESIGNATIONS:
1. + SUPPLY
2. GROUND
3. OUTPUT

HALL SENSOR SPECIFICATIONS

HERE ARE KEY SPECIFICATIONS FOR SOME OF THE MOST POPULAR HALL SENSORS.


ALL SENSORS CAN ACCEPT UNLIMITED MAGNETIC FLUX DENSITY. DO NOT EXCEED MAXIMUM SUPPLY VOLTAGE.	MINIMUM SUPPLY (VOLTS)	MAXIMUM SUPPLY (VOLTS)	OUTPUT CURRENT (mA)
A3515 RATIOMETRIC SENSOR	4.5	8	10
A3141 UNIPOLAR SWITCH	4.5	24	25
UGX3132 BIPOLAR SWITCH	4.5	24	25
A3187 LATCHING SWITCH	3.8	30	25
UGQ5140 POWER SWITCH	4.5	24	300
A3422 DIRECTION SENSOR	4.5	18	30
ATS610 GEAR TOOTH SENSOR	4.5	16	25

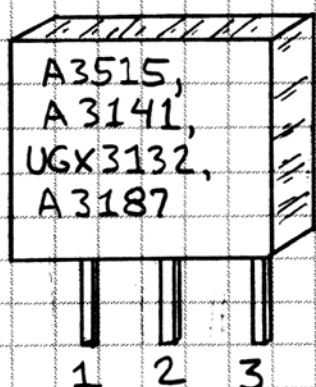

- 1 - POSITIVE (+) SUPPLY
- 2 - GROUND
- 3 - OUTPUT

PIN OUTLINE SHOWN FROM BRANDED (FRONT) SIDE. NOTE THAT ONLY PART OF SENSOR NUMBER MAY BE MARKED ON THE IC. SUFFIX MAY BE PRESENT (e.g. A3141LL IS A3141 WITH "LONG LEADS").

BASIC GAUSS METER

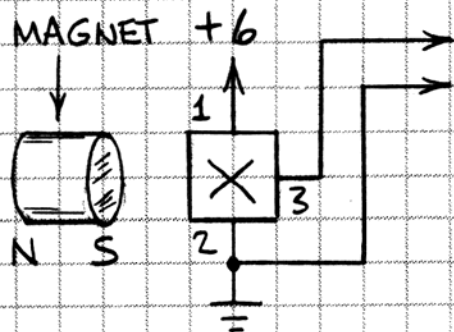


USE THE A3515 RATIOMETRIC HALL SENSOR. WITH NO MAGNET THE OUTPUT IS 1/2 THE SUPPLY VOLTAGE. THE N POLE OF A MAGNET INCREASES THE OUTPUT. THE S POLE DECREASES THE OUTPUT.

OUTPUT CHANGES 25 MILLIVOLTS PER GAUSS.

POWER HALL SENSOR


MOST HALL SENSORS CANNOT DIRECTLY DRIVE AN INCANDESCENT LAMP, RELAY, SMALL MOTOR OR OTHER DEVICE THAT DRAWS MORE THAN 10 TO 25 mA. FOR THESE LOADS AN EXTERNAL DRIVE TRANSISTOR IS REQUIRED. THE UGQ5140 HALL SENSOR INCLUDES A BUILT-IN DRIVE TRANSISTOR THAT CAN CONTINUOUSLY SINK UP TO 300 mA. THIS POWER HALL SENSOR WILL BRIEFLY SINK UP TO 900 mA TO ALLOW TIME FOR A LAMP TO WARM UP TO ITS RATED OPERATING CURRENT.

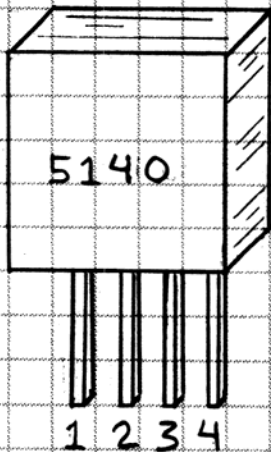

PIN 1 - SUPPLY (+4.5 TO 28V)
PIN 2 - OUTPUT (300 mA MAXIMUM)
PIN 3 - DIODE *
PIN 4 - GROUND

* THE DIODE PIN CAN BE USED FOR AN OPTIONAL LAMP TEST FUNCTION.

HALL LAMP DRIVER

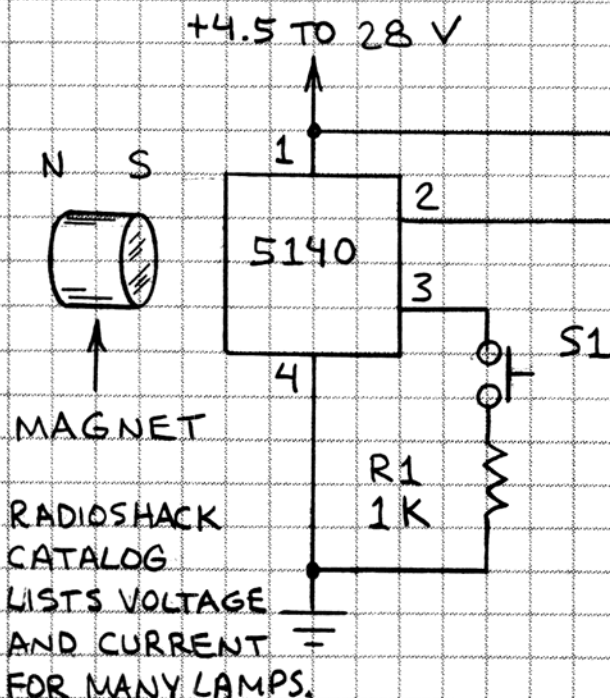

PRESS S1 TO TEST LAMP L1. (R1 AND S1 ARE OPTIONAL.) L1 MUST NOT CONSUME MORE THAN 300 mA WHEN WARMED UP.


HALL SENSOR OPERATING TIPS

HALL SENSORS ARE VERY EASY TO USE. THEY ARE UNAFFECTED BY DIRT AND GREASE THAT CAN DISABLE OPTOELECTRONIC SENSORS. THEY WORK OVER A VERY WIDE TEMPERATURE RANGE (TYPICALLY -40°C TO $+85^{\circ}\text{C}$). EXTREMELY HIGH MAGNETIC FIELD INTENSITIES WILL NOT HARM HALL SENSORS.

HALL SENSORS ARE VERY SENSITIVE TO MECHANICAL STRESS AND EXCESS SUPPLY VOLTAGE. THEREFORE IT'S VERY IMPORTANT TO OBSERVE THE FOLLOWING GUIDELINES WHEN INSTALLING AND USING HALL SENSORS:

POWER SUPPLY — IT'S BEST TO POWER HALL SENSORS AT THE LOWEST ALLOWABLE VOLTAGE. NEVER EXCEED THE MAXIMUM ALLOWABLE!

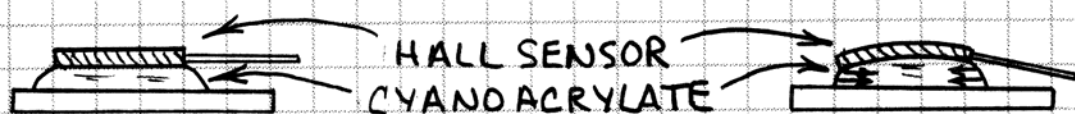MOUNTING HALL SENSORS — HALL SENSORS ARE OFTEN ATTACHED TO A SURFACE WITH ADHESIVE. FOR BEST RESULTS, USE A FILLED EPOXY. NEVER USE CYANOACRYLATE GLUE! THIS GLUE SHRINKS AND CAN EASILY CAUSE ENOUGH MECHANICAL STRAIN TO CHANGE THE HALL SENSOR'S OUTPUT.




ORIGINAL PLACEMENT
OF HALL SENSOR

CEMENT SHRINKS AND
BENDS HALL SENSOR

ENCAPSULATING HALL SENSORS — AS WHEN CEMENTING HALL SENSORS TO A SURFACE, ENCAPSULATING A HALL SENSOR IN POTTING COMPOUND OR EPOXY CAN CAUSE MECHANICAL STRESS THAT ALTERS THE SENSOR'S OUTPUT. CHANGING THE TEMPERATURE OF ENCAPSULATED HALL SENSORS CAN ALSO CAUSE MECHANICAL STRESS. THEREFORE IT'S BEST NOT TO ENCAPSULATE HALL SENSORS.


HALL SENSOR - MAGNET SEPARATION

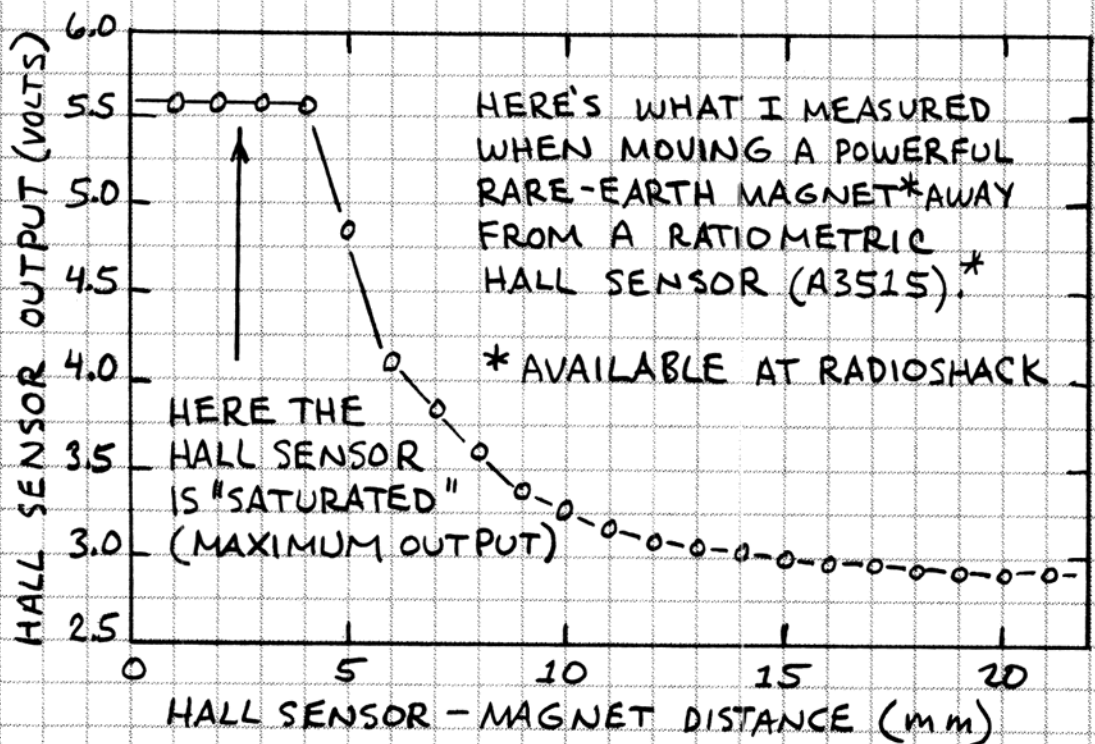IDEALLY, THE STRENGTH OF A MAGNETIC FIELD IS INVERSELY PROPORTIONAL TO THE SQUARE OF THE DISTANCE FROM THE MAGNET. AT 3 CM THE STRENGTH OF THE FIELD SHOULD BE ABOUT $1/3^2$ OR $1/9$ THE VALUE AT 1 CM. AS THIS GRAPH SHOWS, IN THE "REAL WORLD" THIS RELATIONSHIP IS NOT SO IDEAL - OR AT LEAST NOT EASILY MEASURED.



FLUX CONCENTRATORS

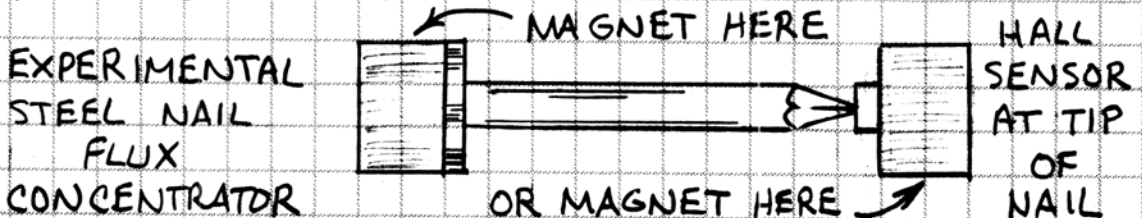
FLUX CONCENTRATORS, MADE FROM LOW-CARBON STEEL GUIDE, OR CONCENTRATE A MAGNETIC FIELD. STEEL NAILS CAN BE USED AS EXPERIMENTAL FLUX CONCENTRATORS. FOR BEST RESULTS, THE DIAMETER OF THE CONSTRICTED END OF A FLUX CONCENTRATOR SHOULD APPROXIMATE THAT OF THE HALL SENSOR CHIP.




BEST MAGNET ARRANGEMENTS

IT'S IMPORTANT TO PLAN AHEAD WHEN DESIGNING HALL EFFECT CIRCUITS. IT'S USUALLY BEST TO MAKE A TEST CIRCUIT BEFORE BUILDING YOUR FINAL DESIGN. THIS WILL ALLOW YOU TO TEST THE CIRCUIT'S RESPONSE TO VARIOUS MAGNETS AND MAGNETIC FIELDS.


HEAD-ON OPERATION

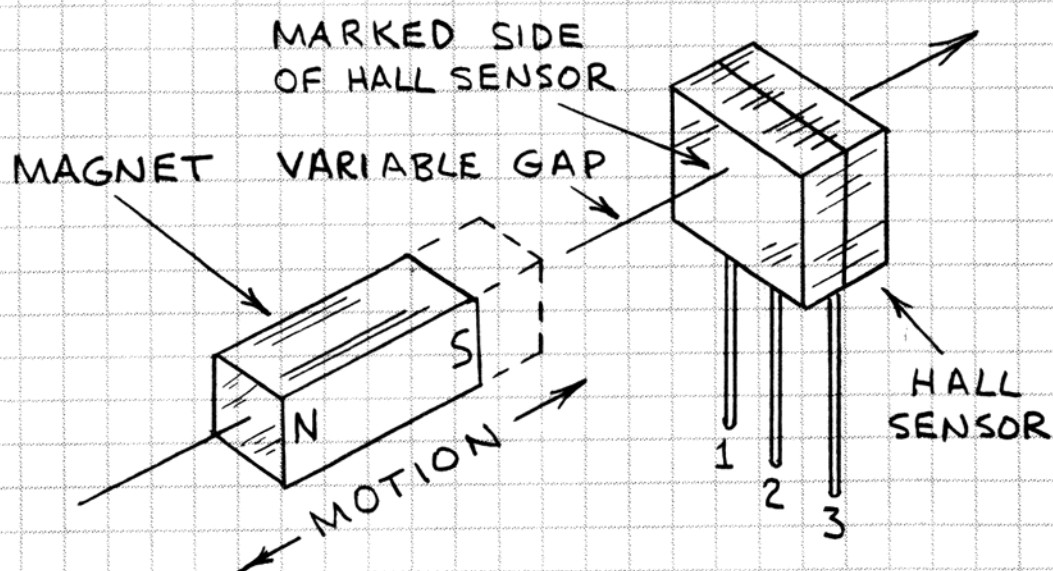

SLIDE-BY OPERATION

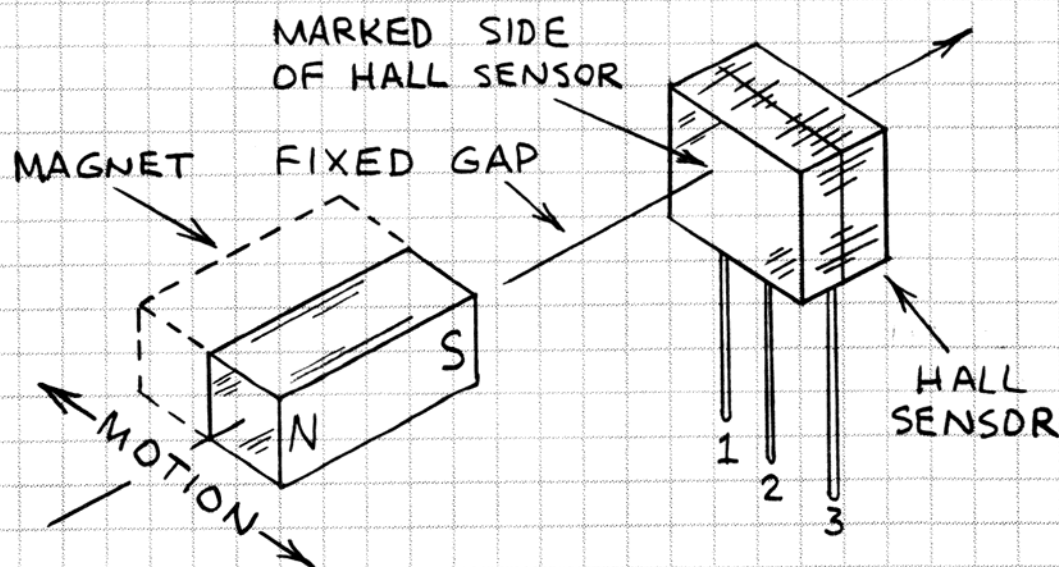

PUSH-PUSH OPERATION

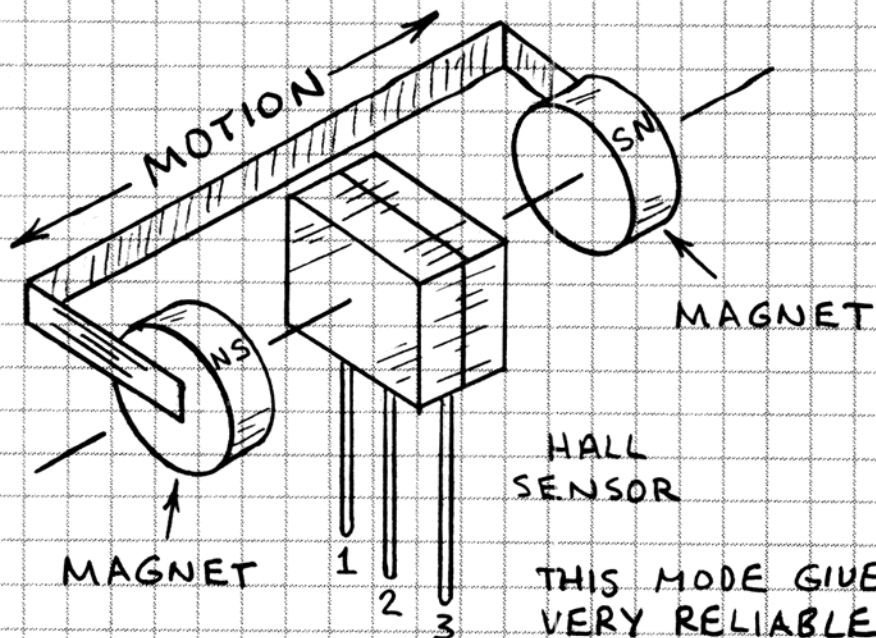


HALL
SENSOR

THIS MODE GIVES
VERY RELIABLE
SWITCHING.



INSTALL
MAGNETS ON
MOVABLE
FRAME. OK TO
GLUE MAGNETS
TO THE FRAME.

PUSH-PULL OPERATION

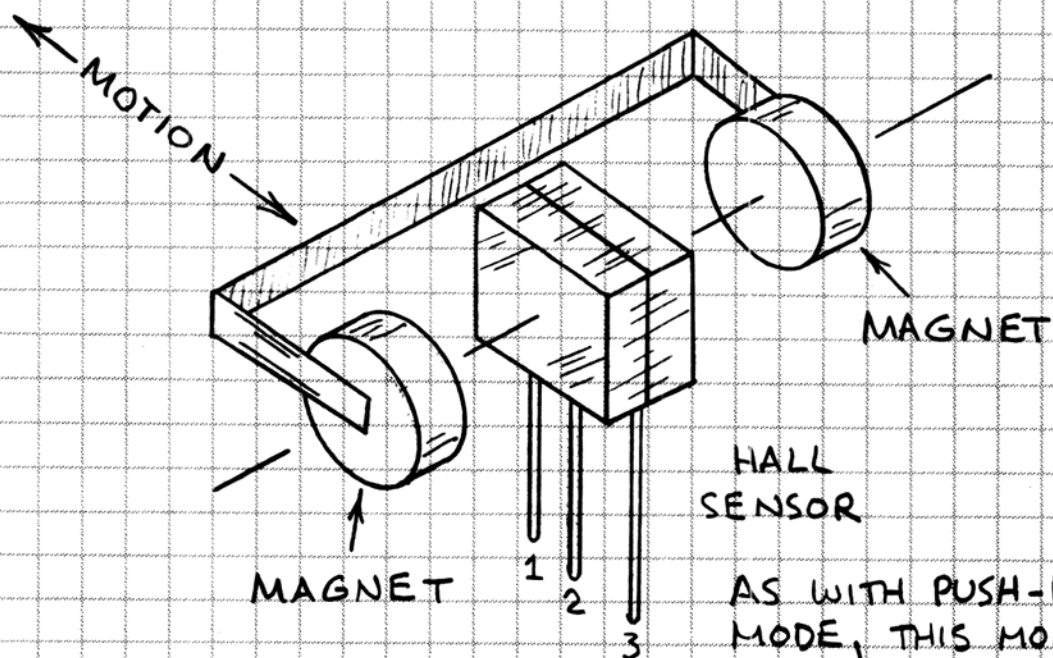


HALL
SENSOR

AS WITH PUSH-PUSH
MODE, THIS MODE
GIVES VERY
RELIABLE SWITCHING.

INTERFACING DIGITAL HALL SENSORS

APPLICATIONS SHOWN HERE DESCRIBE OPERATION WITH UGX3132. THESE INTERFACE CIRCUITS ALSO WORK WITH A3141, A3187, ETC.

LED INTERFACE

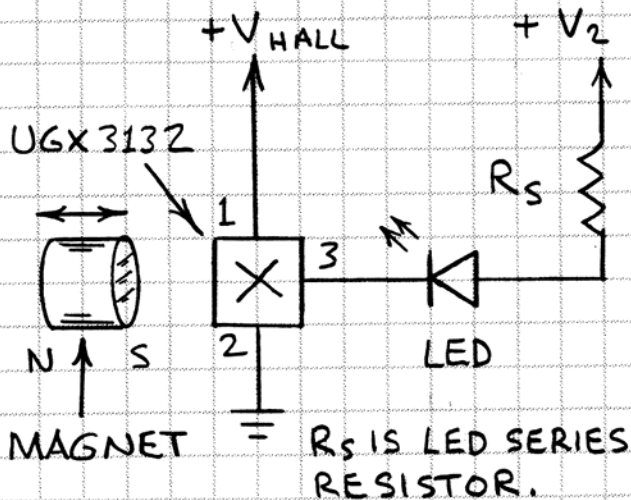


THE LED GLOWS WHEN SOUTH POLE OF MAGNET IS NEAR THE HALL SENSOR. LED SWITCHES OFF WHEN NORTH POLE OF MAGNET IS NEAR THE HALL SENSOR.

$$R_S = \frac{V_2 - V_{LED}}{I_{LED}}$$


V_{LED} FOR MOST VISIBLE LEDs IS 2 TO 3 VOLTS. FOR I_{LED} (LED CURRENT) OF 10 mA AND V₂ OF 6 VOLTS, $R_S = (6V - 3V) / 0.01 = 300 \text{ OHMS}$. OK TO USE 270 TO 330 OHMS IN MOST APPLICATIONS.

TRANSISTOR INTERFACE

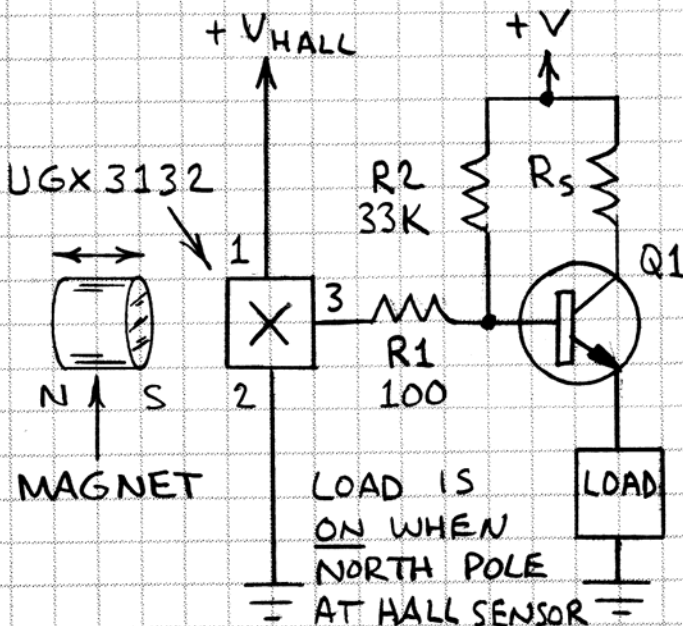


Q1 IS NPN SWITCHING TRANSISTOR (2N2222, MPS2222, ETC.). LOAD IS LAMP, RELAY, ETC. SELECT R_S TO KEEP CURRENT THROUGH Q1 BELOW MAXIMUM ALLOWABLE. LOAD SWITCHES OFF WHEN SOUTH POLE OF MAGNET IS NEAR HALL SENSOR.

TTL LOGIC INTERFACE

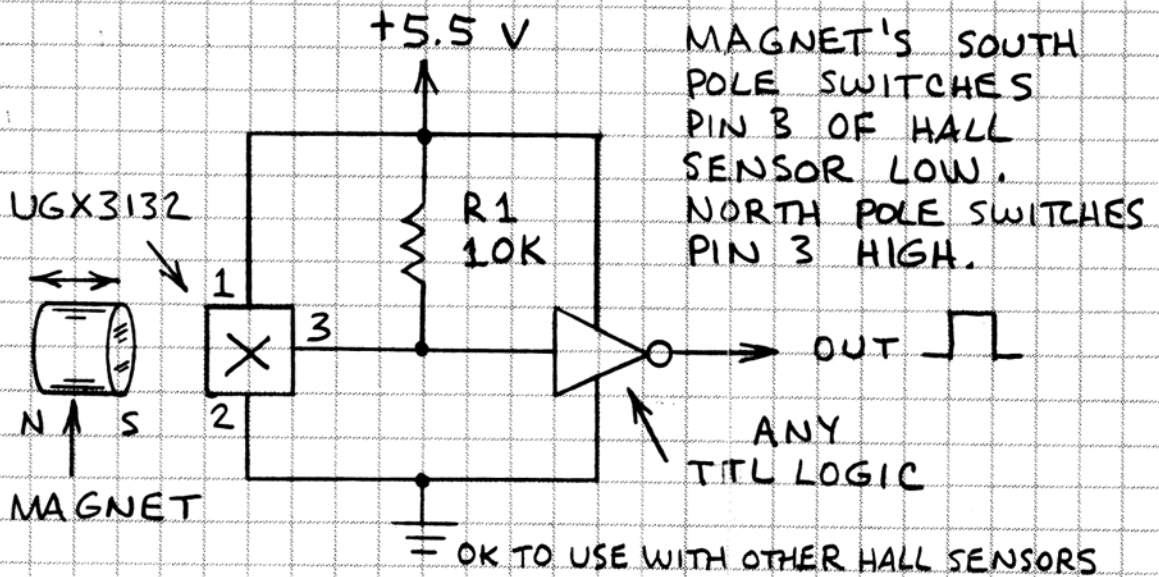

THIS CIRCUIT WORKS WITH OLDER TTL AND NEWER LOW-POWER TTL LOGIC. THE HALL SUPPLY VOLTAGE SHOULD MATCH THE TTL SUPPLY VOLTAGE.


CMOS LOGIC INTERFACE

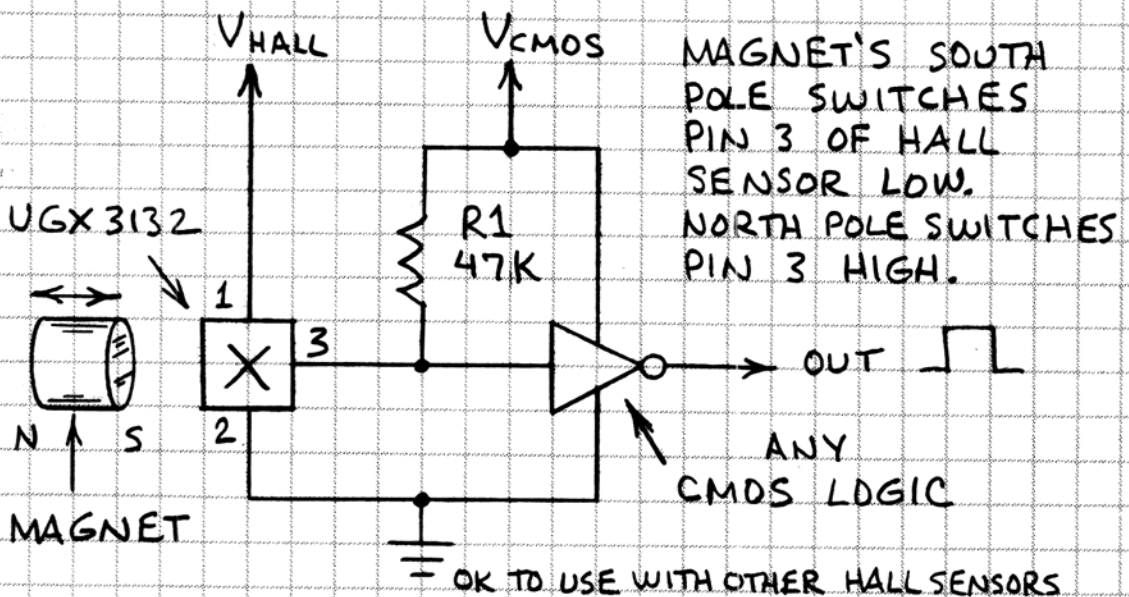

BEST TO POWER HALL SENSOR AND CMOS LOGIC FROM SAME SUPPLY WHEN POSSIBLE. IF NOT, KEEP HALL SUPPLY VOLTAGE AT OR BELOW CMOS SUPPLY VOLTAGE. BE SURE TO FOLLOW CMOS HANDLING PRECAUTIONS.



FERROUS METAL INDICATOR

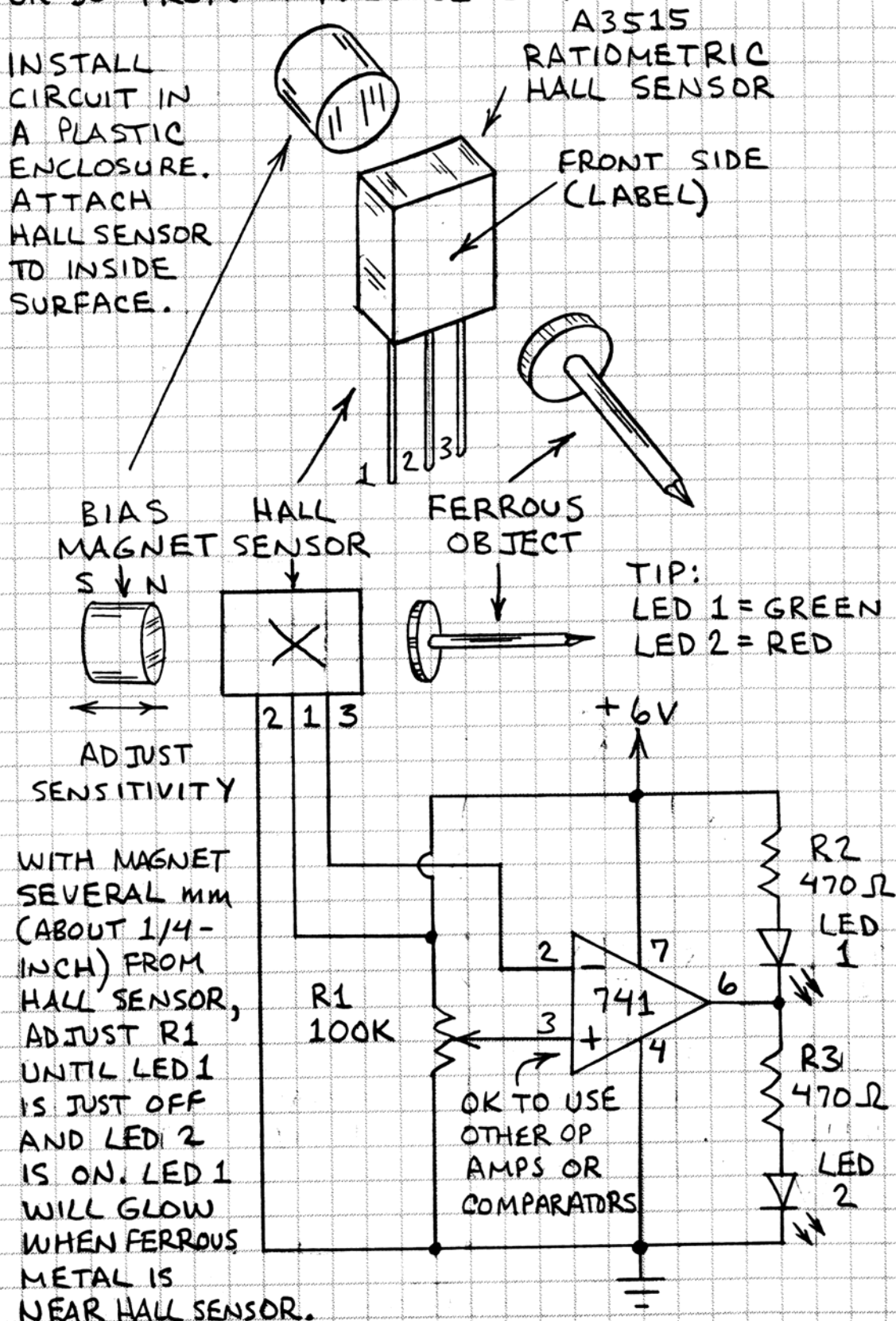THIS SIMPLE CIRCUIT INDICATES WHEN A FERROUS METAL OBJECT IS WITHIN 1 CM OR SO FROM A HALL SENSOR.



HALL SENSOR RELAY

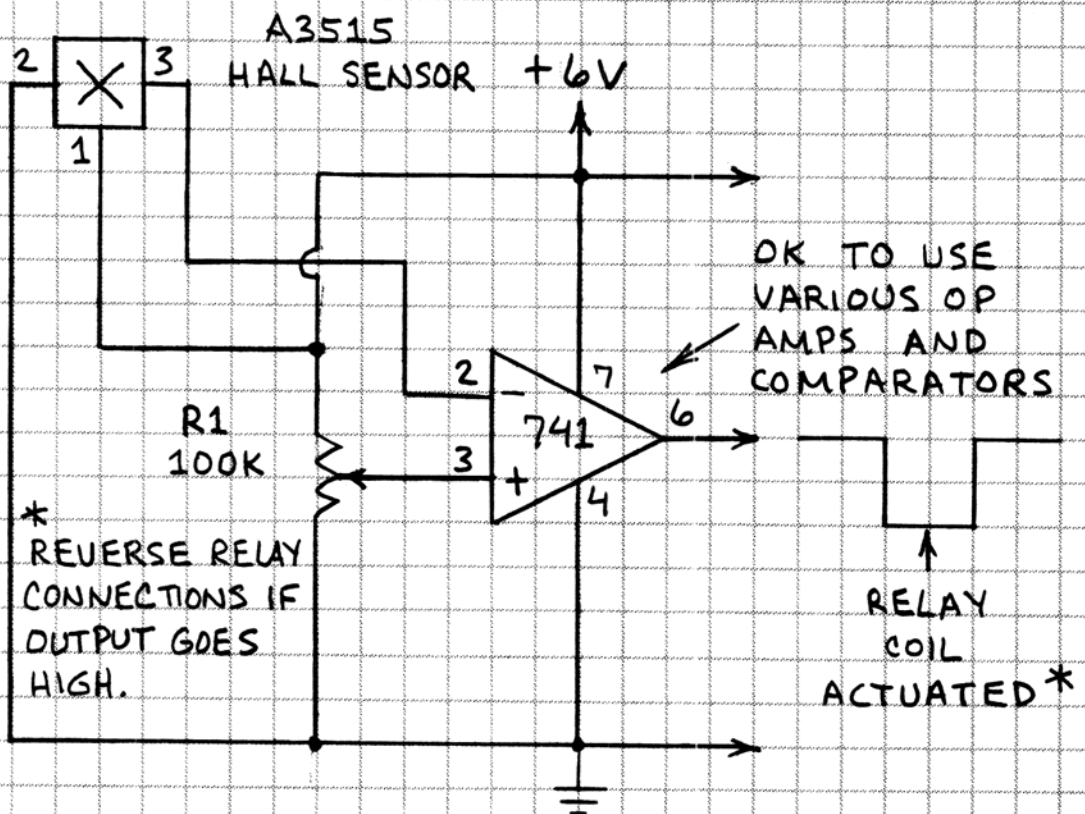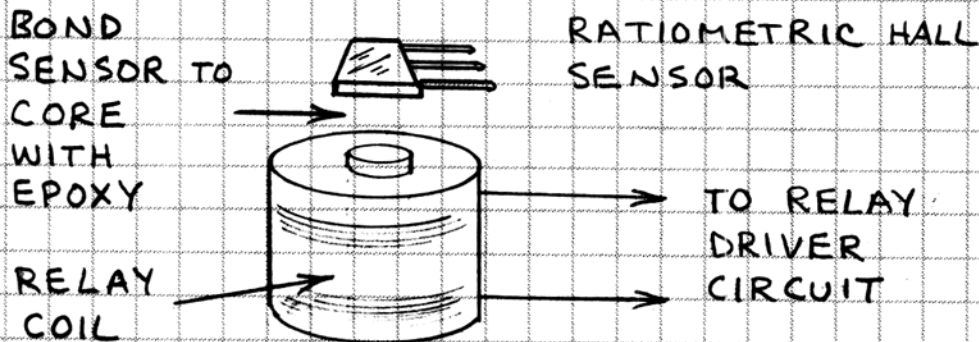
THE MOVING CONTACT OF AN ELECTROMAGNETIC RELAY PRODUCES A SOMETIMES UNWANTED CLICKING SOUND AND CAN EVENTUALLY WEAR OUT OR BE CONTAMINATED WITH GREASE OR DUST. A HALL SENSOR CAN REPLACE A RELAY'S CONTACTS IN SOME APPLICATIONS.




ADJUST R1 UNTIL PIN 6 JUST GOES HIGH. WHEN RELAY COIL IS ENERGIZED, PIN 6 WILL GO LOW. CHANGES IN RESIDUAL MAGNETISM OF THE RELAY'S STEEL CORE MAY NECESSITATE OCCASIONAL ADJUSTMENTS OF R1.

LEVEL INDICATOR

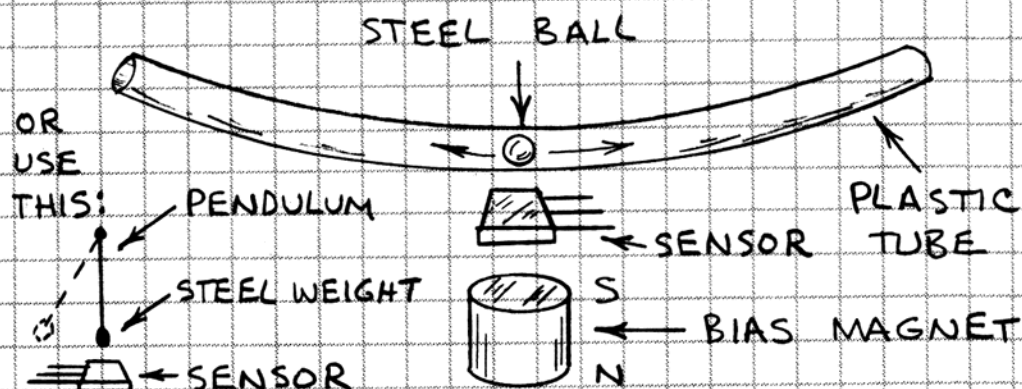THIS CIRCUIT IS AN ELECTRONIC LEVEL INDICATOR THAT SENSES WHEN A ROLLING STEEL BALL IS AT REST.




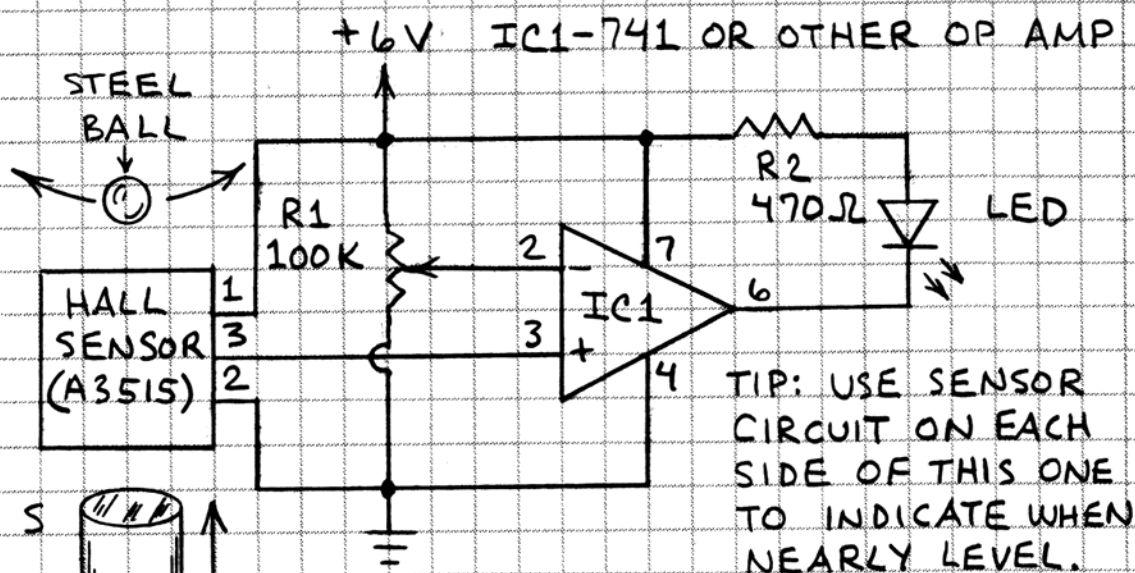
PROTOTYPE CIRCUIT USES A BB INSIDE A GENTLY BENT SODA STRAW. A SMALL BALL BEARING WILL WORK BETTER AS IT IS MORE SPHERICAL.



PLACE SOUTH POLE OF MAGNET ABOUT 1 CM (0.4 INCH) BEHIND HALL SENSOR. ADJUST R1 UNTIL LED JUST STOPS GLOWING. THE LED SHOULD NOW GLOW WHEN STEEL BALL APPROACHES THE HALL SENSOR. EXPERIMENT WITH POSITION OF MAGNET FOR BEST RESULTS.

MAGNET POSITION DETECTOR

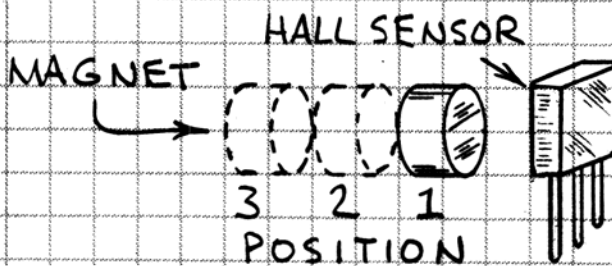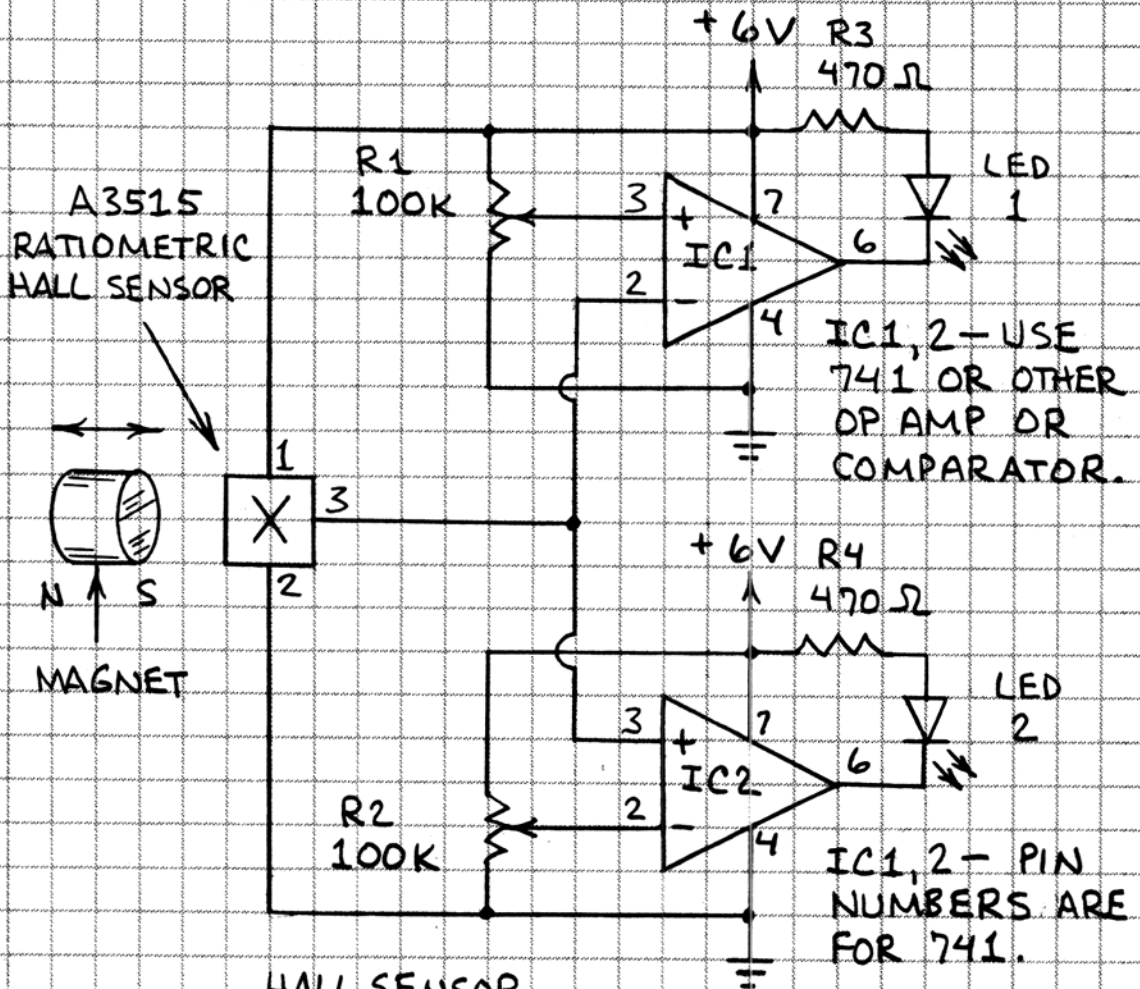THIS CIRCUIT INDICATES WHEN A MAGNET IS AT A PRESET, ADJUSTABLE DISTANCE FROM A RATIOMETRIC HALL SENSOR.





PLACE SOUTH POLE OF MAGNET UP TO 1-2 CM FROM SENSOR. ADJUST R1 AND R2 UNTIL LED1 AND LED2 JUST GLOW. WHEN MAGNET IS MOVED TOWARD SENSOR, LED2 SWITCHES OFF. WHEN MAGNET IS MOVED AWAY, LED1 SWITCHES OFF. USE NORTH POLE OF MAGNET TO REVERSE OPERATION.

POSITION	LED 1	LED 2
SOUTH 1	ON	OFF
SOUTH 2	ON	ON
SOUTH 3	OFF	ON
NORTH 1	OFF	ON
NORTH 2	ON	ON
NORTH 3	ON	OFF

DUAL-OUTPUT HALL SENSORS

A PAIR OF BACK-TO-BACK HALL SENSORS PROVIDES A DUAL-OUTPUT MAGNET SENSOR. THIS METHOD WORKS WITH BOTH DIGITAL HALL SWITCHES AND RATIO-METRIC HALL SENSORS. RATIO-METRIC HALL SENSORS PROVIDE HIGHER SENSITIVITY.

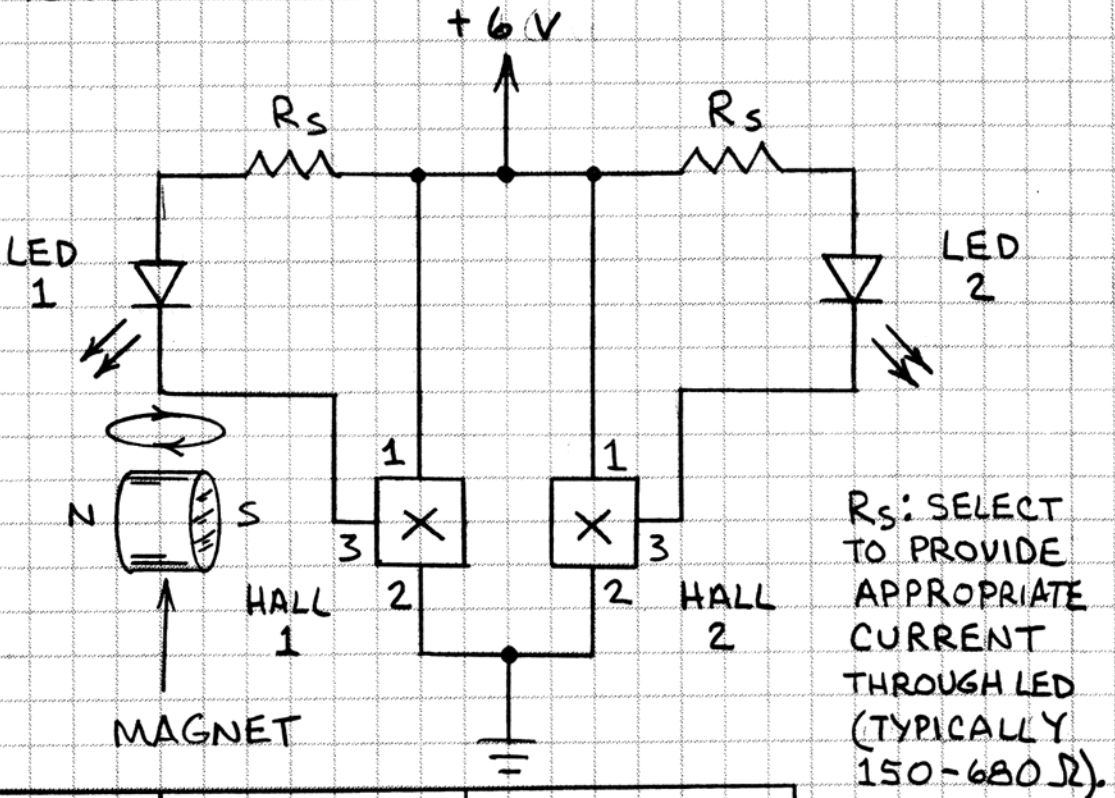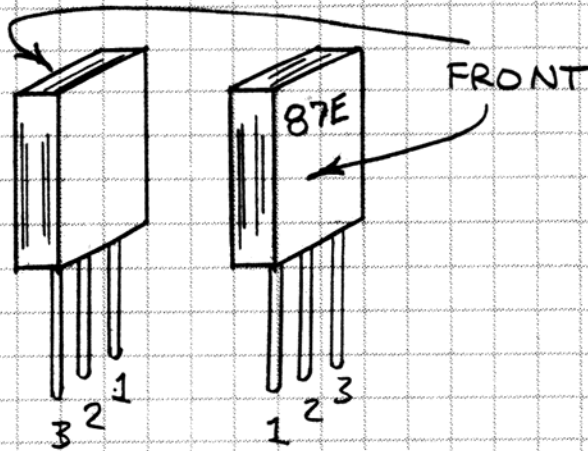MOUNT TWO SENSORS CLOSE TO ONE ANOTHER (TOUCHING) ON CIRCUIT BOARD AND/OR BOND TOGETHER WITH FILLED EPOXY.




POLE AT HALL 1	DIGITAL		RATIO-METRIC	
	LED 1	LED 2	LED 1	LED 2
N	OFF	ON	ON	OFF
S	ON	OFF	OFF	ON


HALL 1, 2:
A3141,
A3515

FIELD STRENGTH BARGRAPH

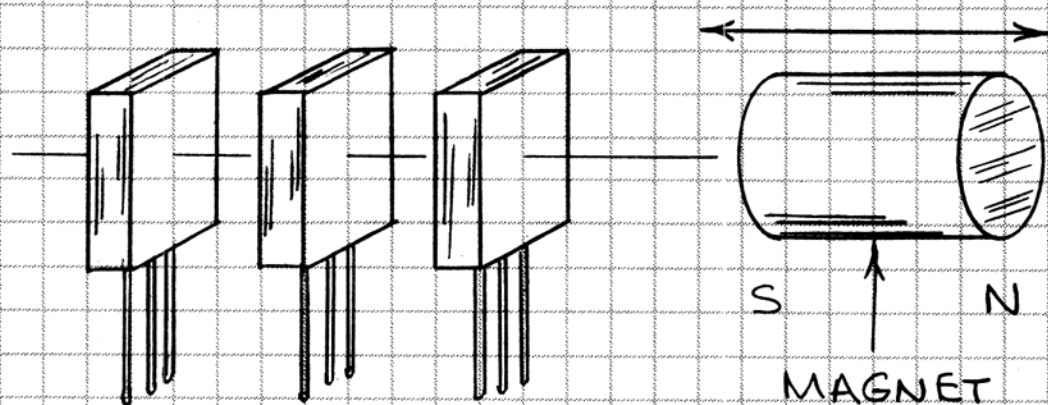A LINEAR OR RATIOMETRIC HALL SENSOR CAN MEASURE THE STRENGTH OF A MAGNETIC FIELD. THIS CIRCUIT SHOWS HOW TO USE A STACK OF DIGITAL HALL SENSORS (THREE OR MORE) TO DISPLAY MAGNETIC FIELD STRENGTH ON A BARGRAPH LED DISPLAY.



STACKED HALL SENSORS (A3141)


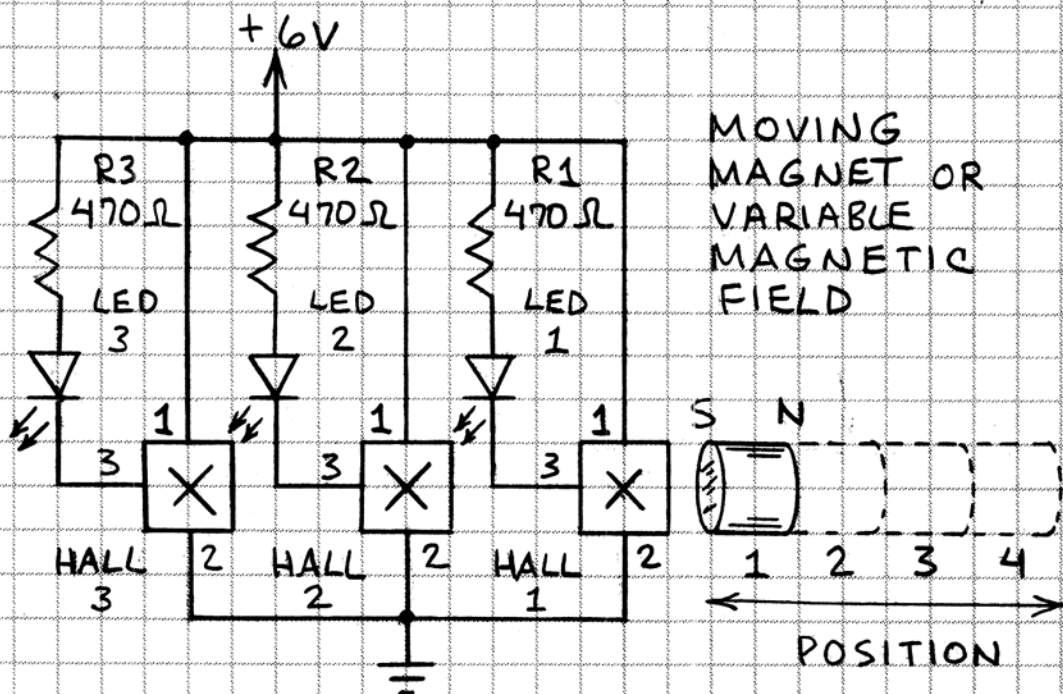


POSITION	LED 1	LED 2	LED 3
1	ON	ON	ON
2	ON	ON	OFF
3	ON	OFF	OFF
4	OFF	OFF	OFF

OK TO USE ANY COLOR LEDs. I USED RED, GREEN AND BLUE.

HALL SENSOR DIRECTION INDICATOR

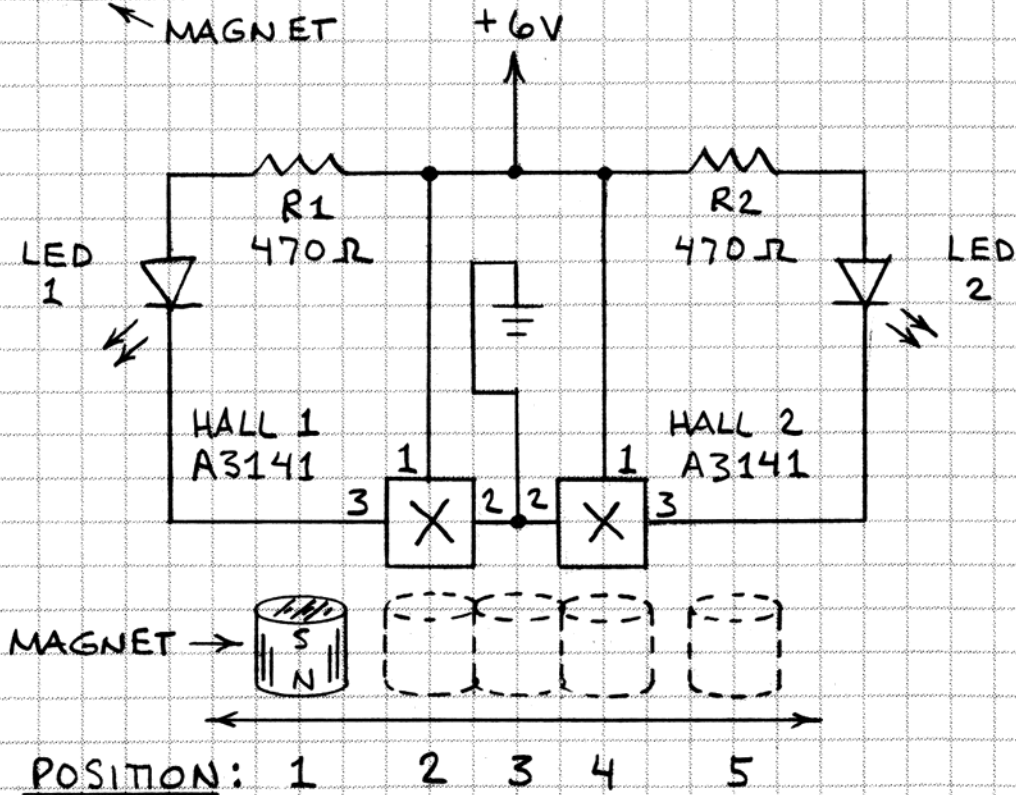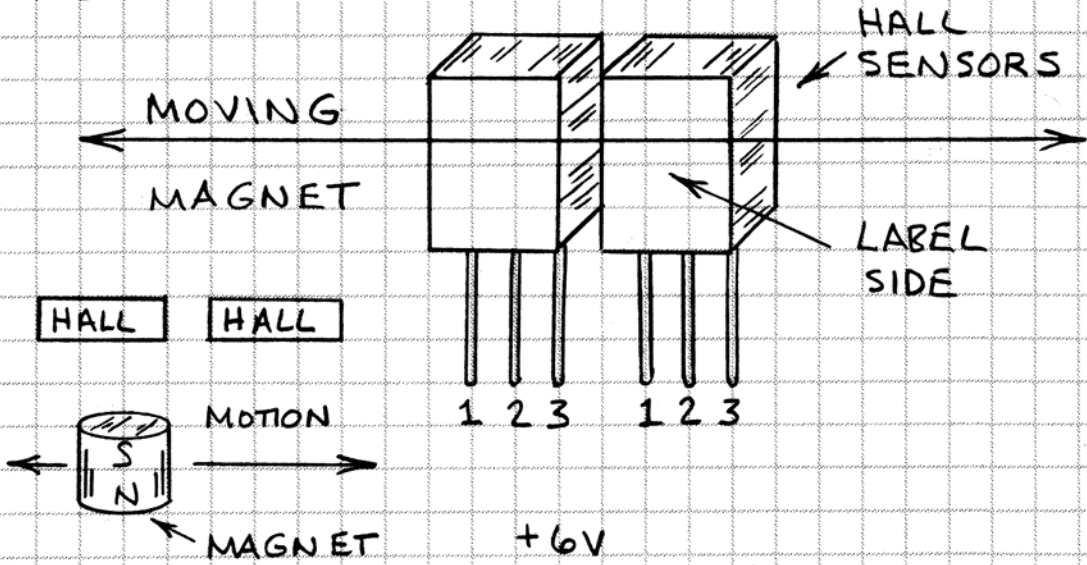TWO OR MORE HALL SENSORS ARRANGED SIDE-BY-SIDE CAN INDICATE THE DIRECTIONAL MOVEMENT OF A NEARBY MAGNET.




POSITION	LED 1	LED 2
1	OFF	OFF
2	ON	OFF
3	ON	ON
4	OFF	ON
5	OFF	OFF

THIS CIRCUIT DRIVES LEDs, BUT IT WILL ALSO DRIVE EXTERNAL LOGIC CIRCUITS.

ULTRA-SENSITIVE MAGNET SWITCH

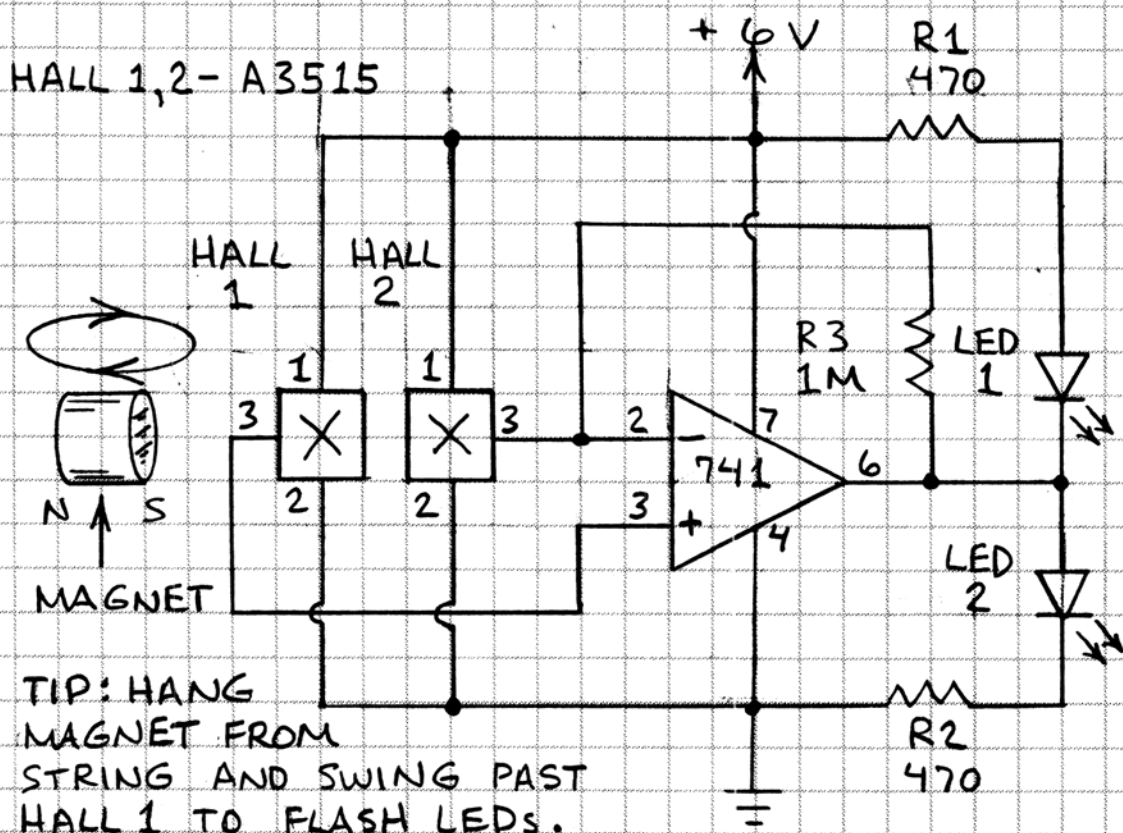A VERY SENSITIVE MAGNET SWITCH CAN BE MADE BY CONNECTING A PAIR OF BACK-TO-BACK HALL SENSORS TO AN OP AMP OR COMPARATOR.





THIS CIRCUIT WILL RESPOND TO A MAGNET 15 CM (ABOUT 6 INCHES) AWAY. WITH NO MAGNET OR WHEN SOUTH POLE OF MAGNET IS NEAR HALL SENSOR 1, LED 2 GLOWS. WHEN NORTH POLE OF MAGNET IS NEAR HALL SENSOR 1, LED 1 GLOWS. USE DIFFERENT COLOR LEDs FOR LEDs 1 AND 2, EITHER INDIVIDUAL LEDs OR A BICOLOR LED.

MOUNT HALL SENSORS BACK-TO-BACK WITH FRONT SIDE OF HALL SENSOR 1 (SIDE WITH NUMBERS) CLOSEST TO WHERE MAGNET WILL BE PLACED.


THOUGH THIS CIRCUIT DRIVES LEDs, IT CAN ALSO POWER MANY OTHER DEVICES. USE APPROPRIATE INTERFACE CIRCUITRY.

MAGNET MUSIC

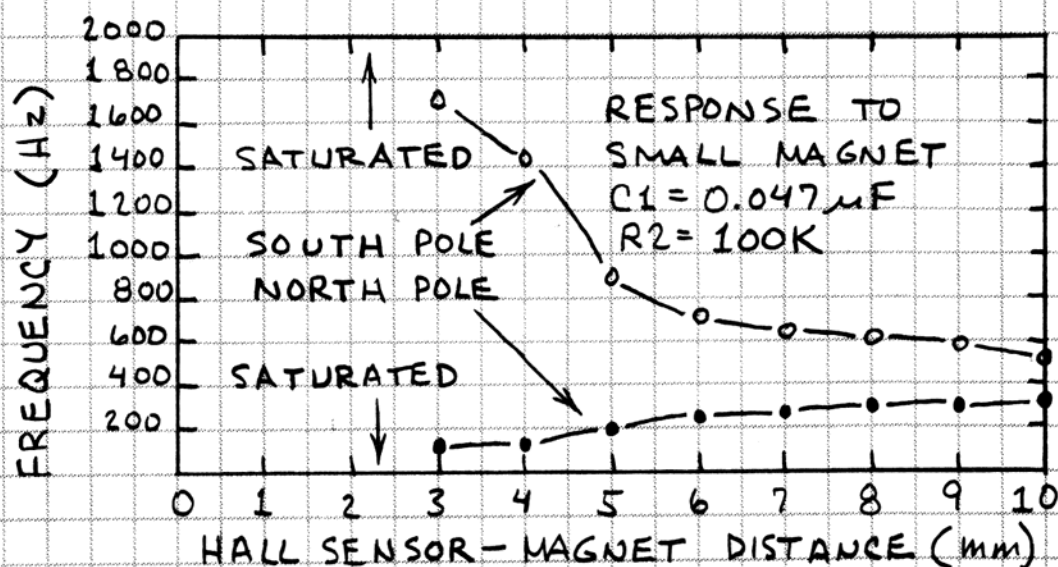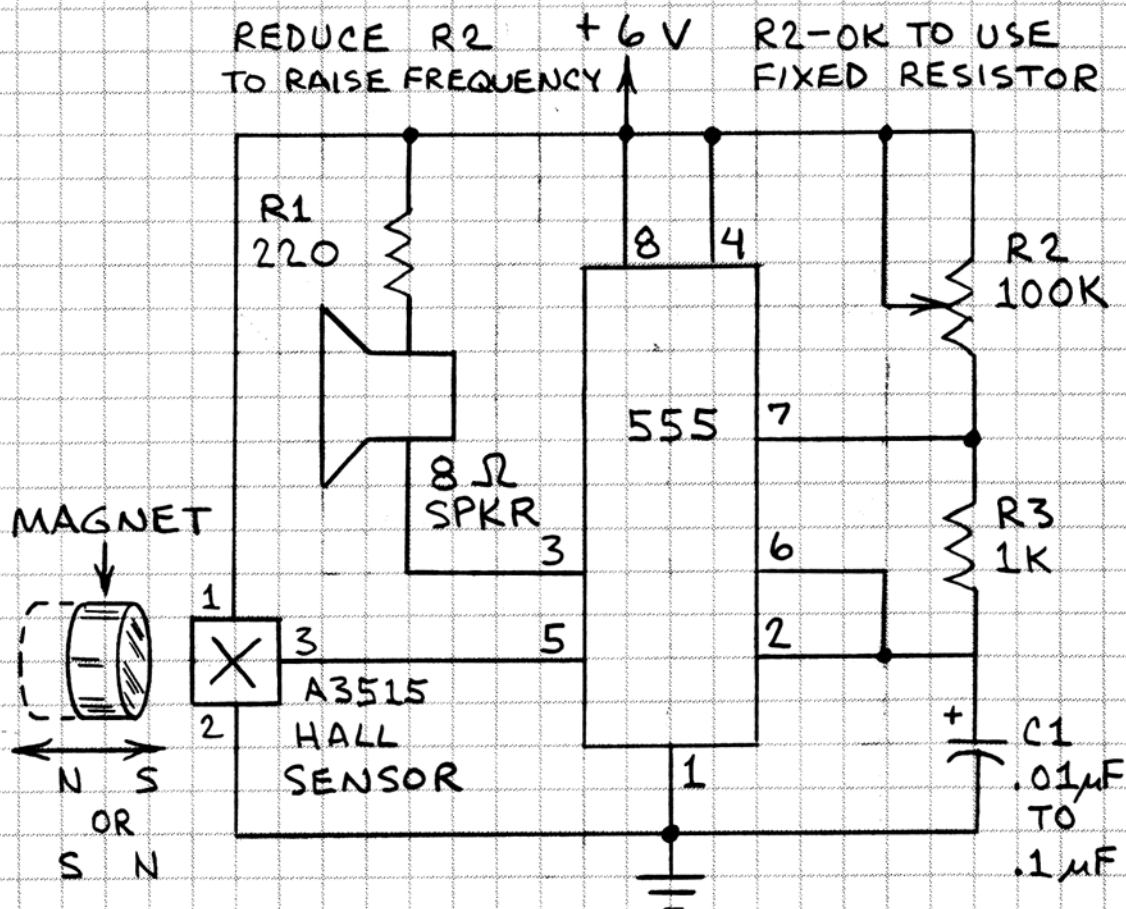
THE OUTPUT VOLTAGE FROM A RATIOMETRIC (LINEAR) HALL SENSOR CAN CONTROL A VOLTAGE-TO-FREQUENCY CONVERTER. THIS PROVIDES A MUSICAL TONE WHOSE FREQUENCY IS CONTROLLED BY A MAGNETIC FIELD.



MUSICAL PENDULUM

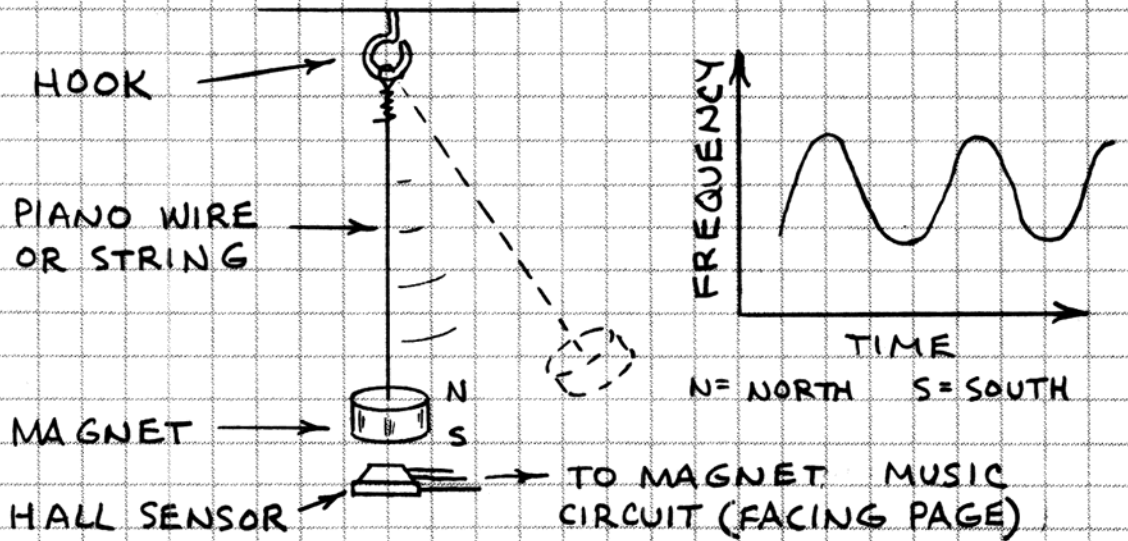


DAMPED OSCILLATING TONE

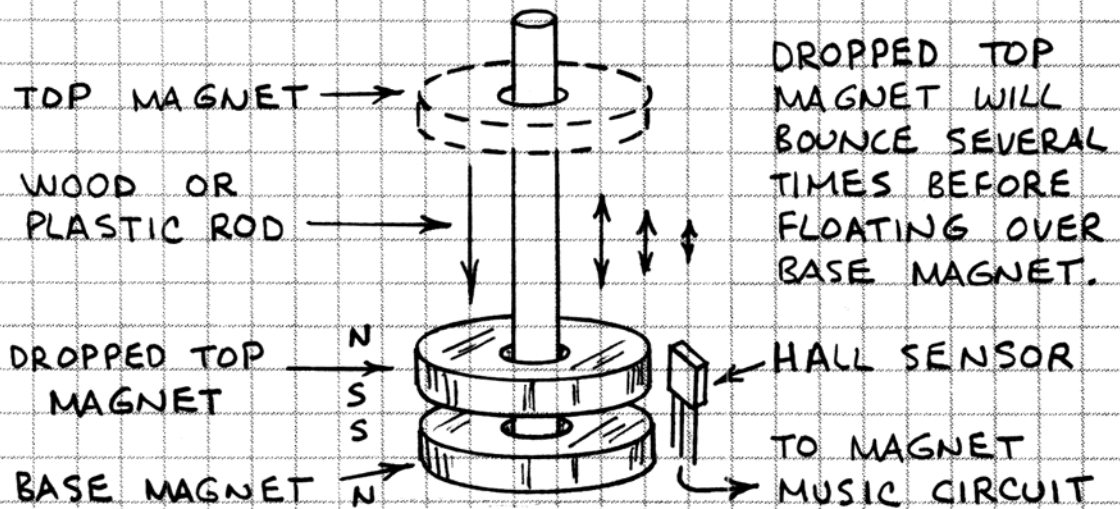

PRESSURE-SENSITIVE TONE

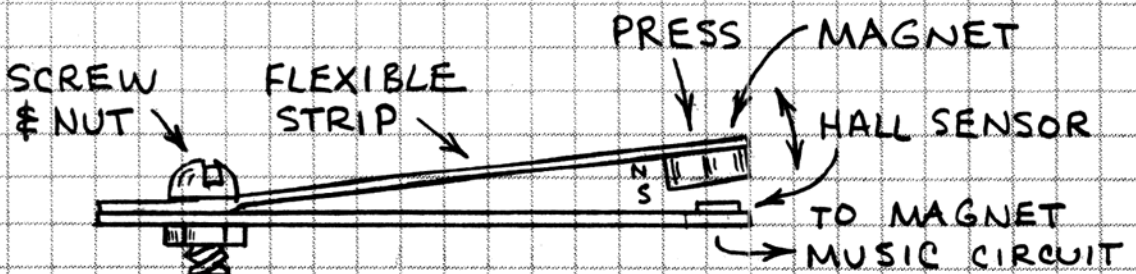PRESS AND RELEASE FLOATING MAGNET (SHOWN ABOVE) OR MOUNT A MAGNET ON A FLEXIBLE BEAM AS SHOWN HERE:




SUPER-SENSITIVE FIELD SENSOR

AN INEXPENSIVE COMPASS IS A MUCH MORE SENSITIVE DETECTOR OF MAGNETIC FIELDS THAN A HALL SENSOR. COMBINING A RATIO-METRIC HALL SENSOR WITH A COMPASS PROVIDES A SUPER-SENSITIVE MAGNETIC FIELD DETECTOR.

ATTACH HALL SENSOR TO SIDE OF COMPASS (TOP OR BOTTOM) CLOSEST TO NEEDLE. USE TAPE TO HOLD SENSOR IN PLACE.

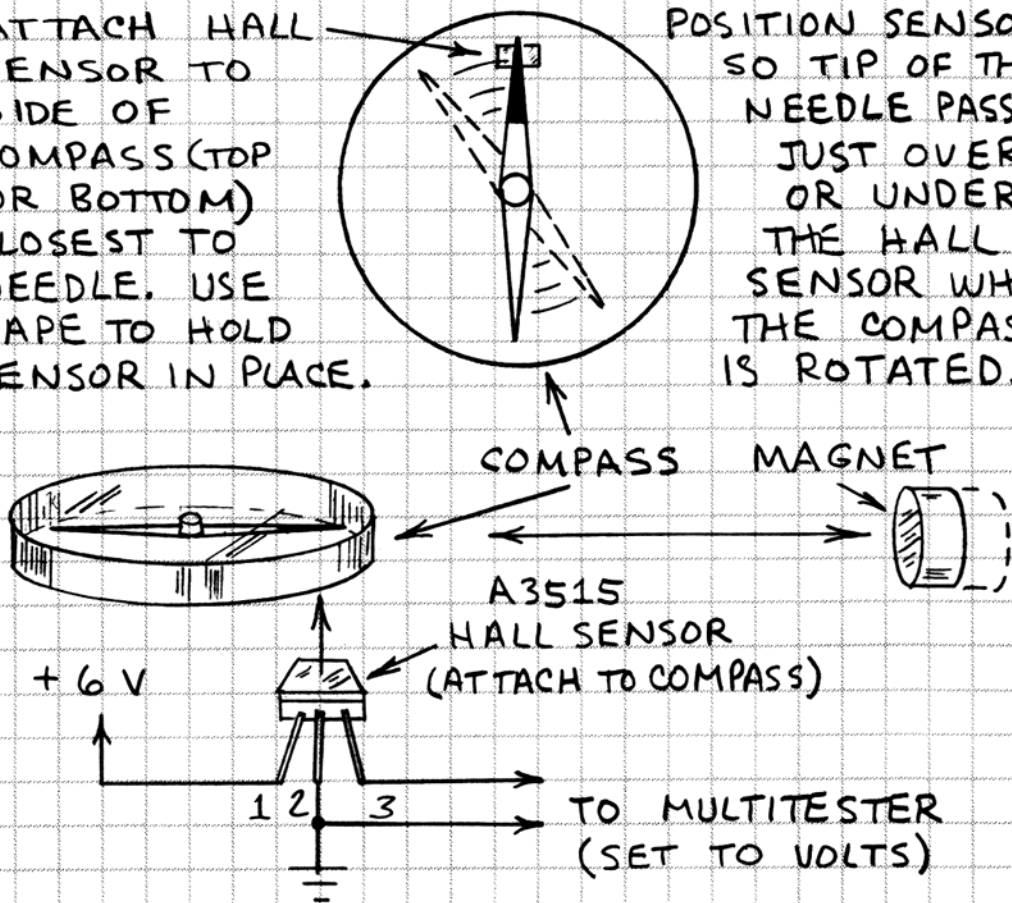POSITION SENSOR SO TIP OF THE NEEDLE PASSES JUST OVER OR UNDER THE HALL SENSOR WHEN THE COMPASS IS ROTATED.




THIS ARRANGEMENT WILL DETECT MOVEMENTS OF A STRONG MAGNET MORE THAN 1 METER (ABOUT 3 FEET) AWAY FROM COMPASS. THE VOLTAGE CHANGE MAY BE ONLY ABOUT 10 MILLIVOLTS (0.010 VOLT) OR SO. SO IT'S BEST TO USE A DIGITAL MULTITESTER.

USE THIS ARRANGEMENT WITH A VOLTAGE-TO-FREQUENCY CIRCUIT TO PROVIDE A TONE THAT CHANGES FREQUENCY WHEN THE COMPASS NEEDLE MOVES PAST THE HALL SENSOR. SEE THE "MAGNET MUSIC" PROJECT IN THIS MINI-NOTEBOOK FOR DETAILS (PAGE 90).

SUPER-SENSITIVE FIELD SWITCH

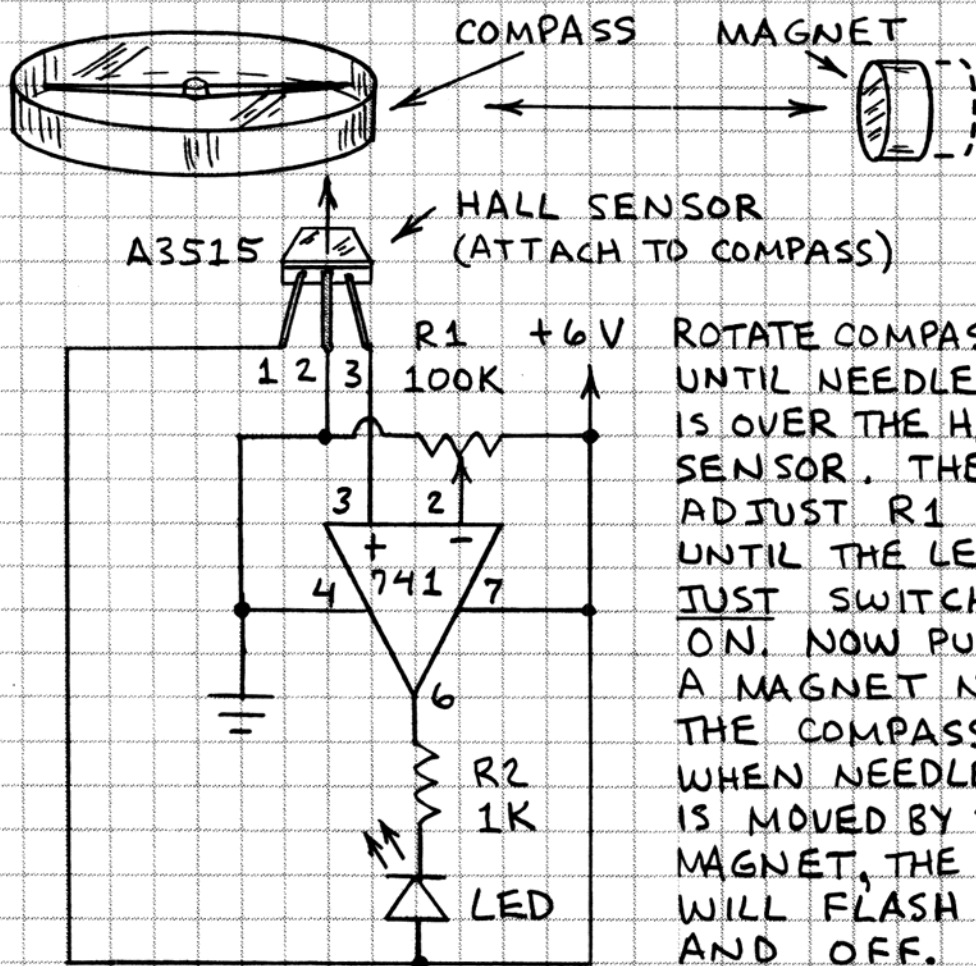THIS CIRCUIT WILL ACTIVATE AN LED WHEN A MAGNET IS PLACED UP TO 1 METER (ABOUT 3 FEET) AWAY.




ABOUT THIS CIRCUIT: THE 741 IS A LOW-COST OPERATIONAL AMPLIFIER (OP AMP) CONNECTED AS A COMPARATOR. THE OUTPUT OF A COMPARATOR IS EITHER LOW OR HIGH. IN THIS CIRCUIT, THE OUTPUT SWITCHES FROM LOW TO HIGH WHEN THE HALL SENSOR OUTPUT VOLTAGE IS ABOUT 0.01 VOLT HIGHER THAN THE VOLTAGE AT PIN 2 OF THE 741.

MANY DIFFERENT OP AMPS WILL WORK IN THIS CIRCUIT. JUST BE SURE TO CONNECT THE PROPER PINS. R2 CAN BE REDUCED TO 470 Ω . THE LED CAN BE REPLACED BY A LOW-VOLTAGE PIEZO TONE GENERATOR.

GIANT COMPASS MAGNETOMETER

GEOMAGNETIC STORMS CAUSED BY SOLAR ACTIVITY CAN CAUSE MAJOR POWER BLACKOUTS AND AURORAS. THEY ALTER EARTH'S MAGNETIC FIELD SO THAT COMPASS NEEDLES DEViate FROM MAGNETIC NORTH. THE GIANT COMPASS SHOWN HERE SHOULD INDICATE COMPASS DEFLECTIONS CAUSED BY GEOMAGNETIC STORMS. A SMALLER VERSION THAT INDICATES DEFLECTIONS WITH REFLECTED LIGHT WAS DESCRIBED BY RON J. LIVESey IN "SKY & TELESCOPE" (OCT. 1989, pp. 426-432).

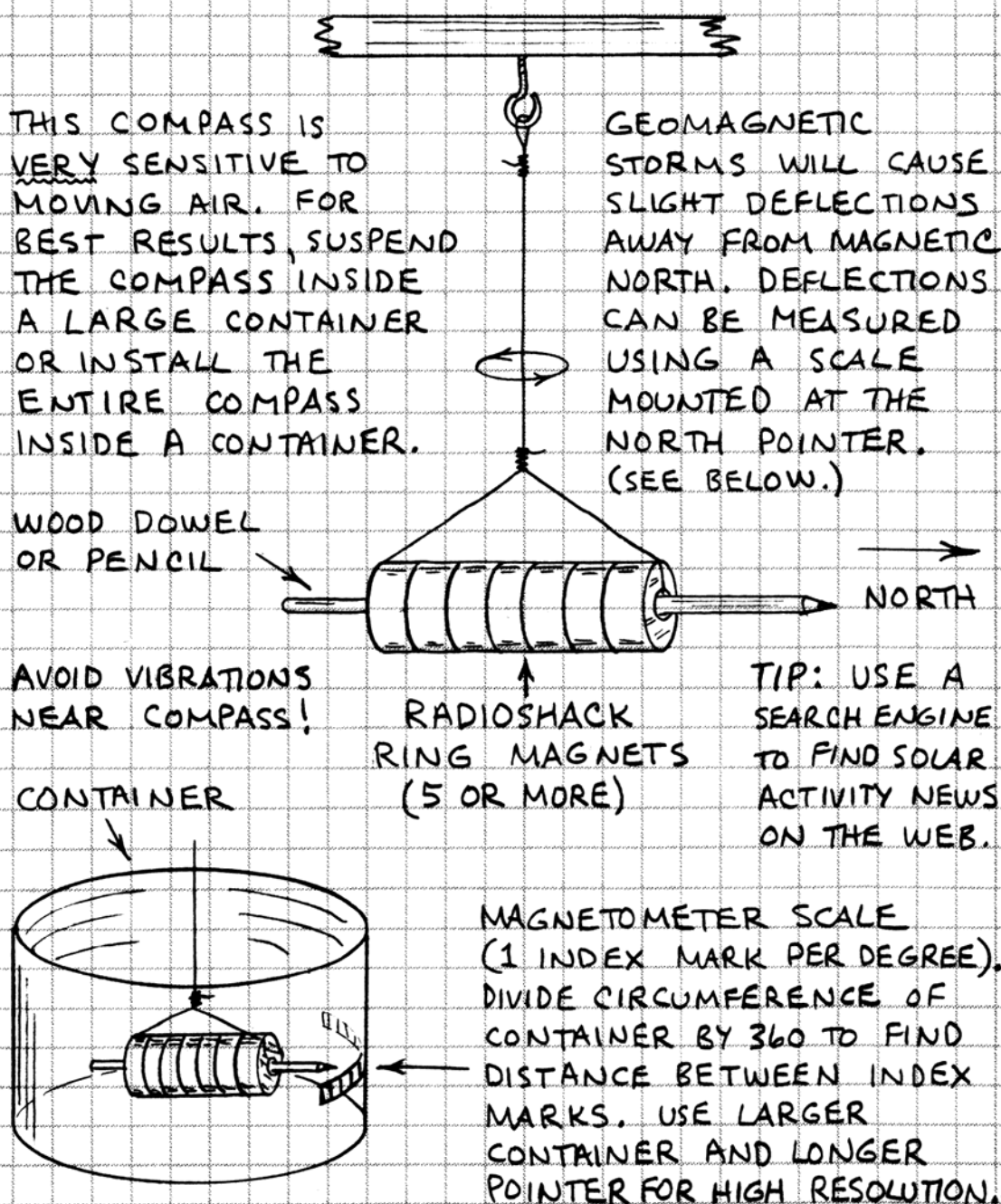


HALL SENSOR NORTH COMPASS

A RATIO-METRIC HALL SENSOR CAN DETECT MAGNETIC NORTH. AT MY LOCATION IN CENTRAL TEXAS THE OUTPUT FROM A RATIO-METRIC HALL SENSOR IS A FEW MILLIVOLTS HIGHER WHEN THE SENSOR POINTS NORTH THAN WHEN IT POINTS ELSEWHERE. THIS VOLTAGE IS ENOUGH TO TRIGGER THIS CIRCUIT.


ADJUST R1 UNTIL VOLTAGE AT PIN 6 OF IC1 IS SOMEWHERE BETWEEN LOWEST AND HIGHEST VALUE. GO OUTDOORS AWAY FROM POWER LINES AND LARGE METAL OBJECTS. ROTATE CIRCUIT UNTIL PRINTED FACE OF HALL SENSOR POINTS NORTH. ADJUST R4 UNTIL LED 1 JUST TURNS ON AND LED 2 JUST TURNS OFF. ROTATE CIRCUIT BOARD TOWARD EAST OR WEST AND LED 1 WILL TURN OFF AND LED 2 WILL TURN ON.

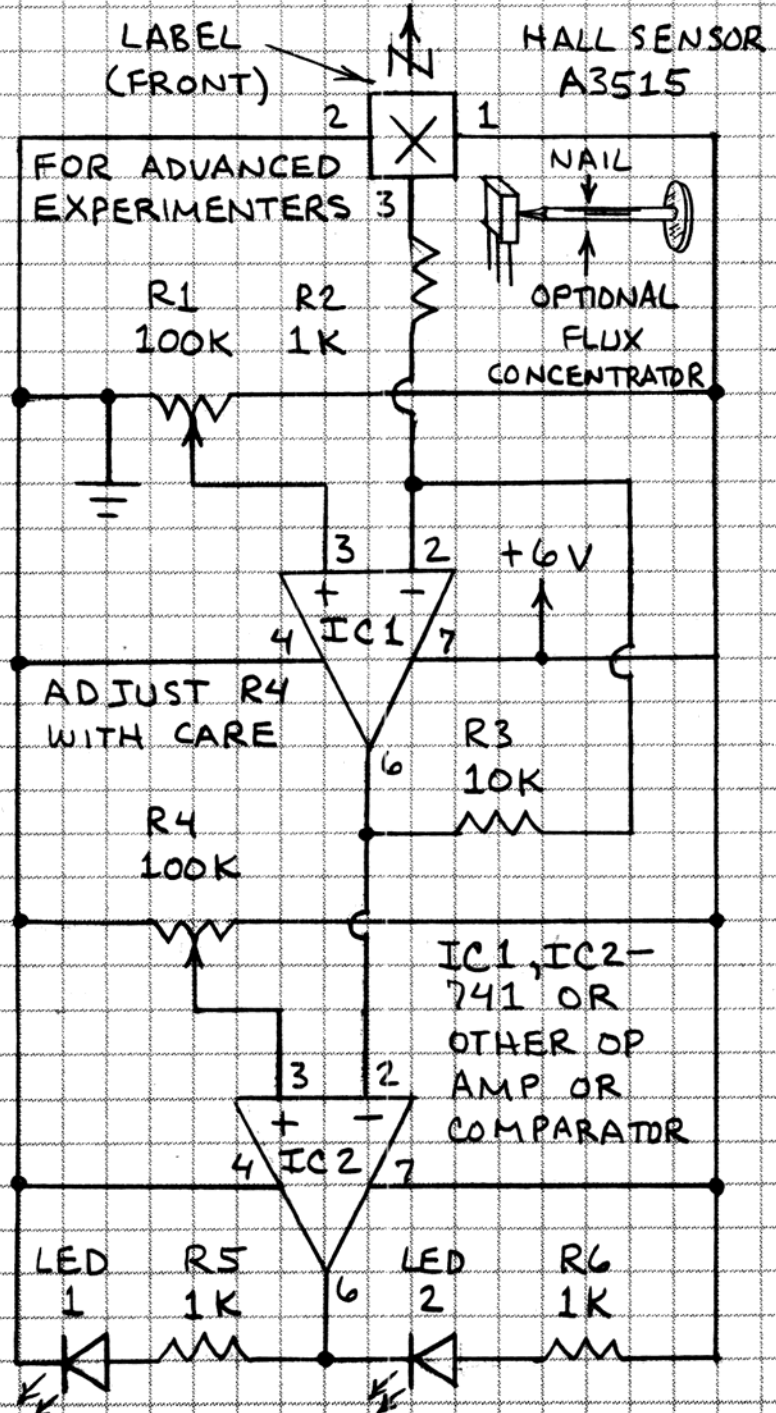TIP: INCREASE SENSITIVITY BY USING A NAIL AS A FLUX CONCENTRATOR (SEE ABOVE).



SPECIALIZED HALL SENSORS

A3422 DIRECTION SENSOR

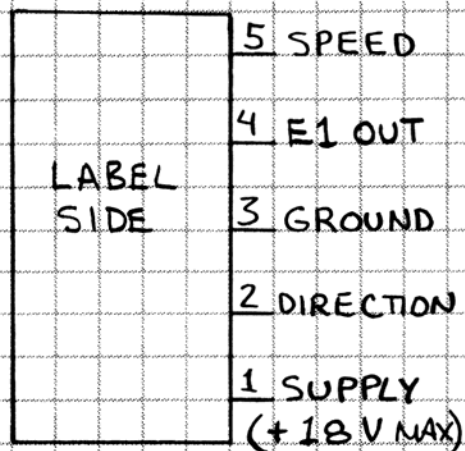


THIS DEVICE HAS TWO SIDE-BY-SIDE HALL SENSORS (E1 AND E2). IT IS DESIGNED TO DETECT ROTATIONAL DIRECTION AND SPEED OF A ROTATING RING MAGNET.


THE A3422 CAN BE USED AS A MAGNET POLE INDICATOR.

E1 IS OUTPUT FROM ONE OF THE TWO HALL SENSORS.

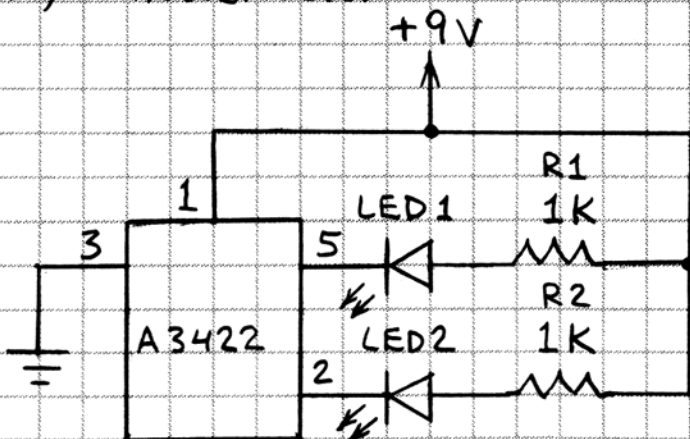LED 1 = NO MAGNET
LED 2 = SOUTH POLE OF MAGNET




ATS610 GEAR SENSOR

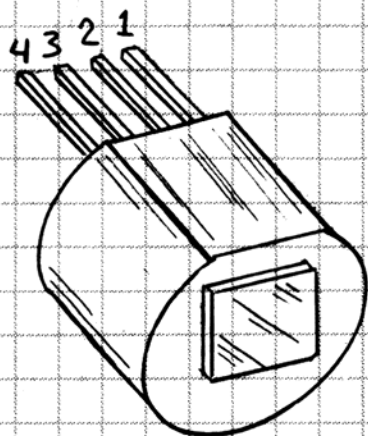

THIS SENSOR INCLUDES A BUILT-IN BIAS MAGNET BEHIND TWO HALL SENSORS. THIS SENSOR IS DESIGNED TO DETECT SMALL TEETH ON A GEAR. IT ALSO WORKS WELL AS A FERROUS METAL DETECTOR.

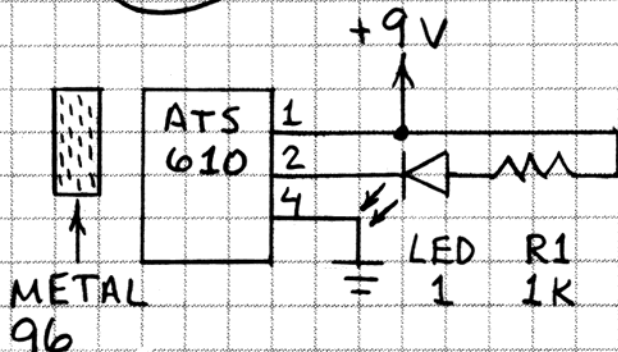PIN 1 - SUPPLY (+16V)
PIN 2 - OUTPUT
PIN 3 - CAPACITOR
PIN 4 - GROUND



LED 1 STOPS GLOWING WHEN FERROUS METAL IS CLOSE TO SENSOR.


III. SOLAR CELL PROJECTS

OVERVIEW

SOLAR CELLS MADE FROM THIN WAFERS OF SILICON CONVERT LIGHT DIRECTLY INTO ELECTRICITY.

POWER GENERATION IS BY FAR THE MOST IMPORTANT APPLICATION FOR SOLAR CELLS AND ARRAYS. THEREFORE THIS SECTION INCLUDES BASIC INFORMATION ABOUT THE SUN AND SOLAR ENERGY. HOW SOLAR CELLS AND SOLAR CELL ARRAYS ARE USED TO CHARGE STORAGE BATTERIES AND TO DIRECTLY POWER SOME CIRCUITS IS ALSO COVERED.

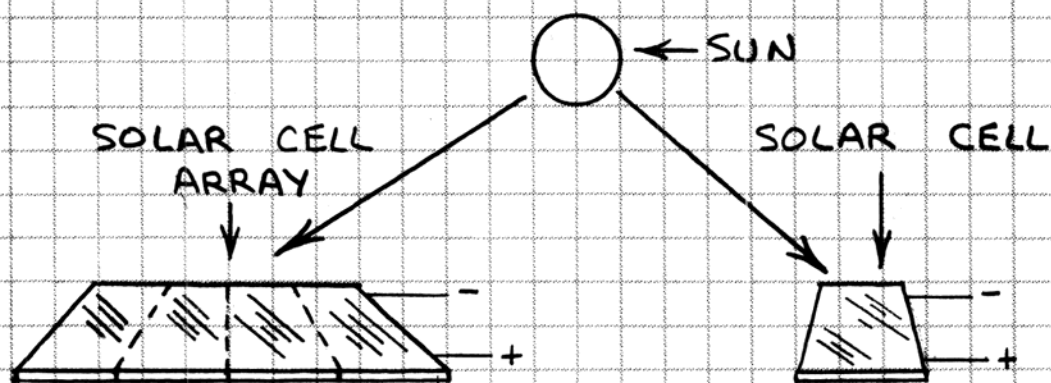IT'S IMPORTANT TO KNOW THAT SOLAR CELLS HAVE MANY APPLICATIONS UNRELATED TO SOLAR POWER. THIS IS BECAUSE SOLAR CELLS WORK VERY WELL AS RELATIVELY INEXPENSIVE AND SENSITIVE LIGHT SENSORS. THIS MINI-NOTEBOOK DESCRIBES MANY USES FOR SOLAR CELLS AS LIGHT SENSORS. VARIOUS CIRCUITS THAT USE SOLAR CELLS AS LIGHT SENSORS ARE ALSO GIVEN.



POWER SYSTEMS

1. CHARGE STORAGE BATTERIES.
2. POWER CIRCUITS DIRECTLY.

SENSING SYSTEMS

1. DETECT SUNLIGHT.
2. DETECT LIGHT FROM LEDs, LAMPS AND OTHER SOURCES.

SOLAR ENERGY MILESTONES

FOR THOUSANDS OF YEARS PEOPLE HAVE USED SUNLIGHT TO WARM THEIR HOMES. SOCRATES (470-399 B.C.) TAUGHT THE IMPORTANCE OF PLACING HOMES SO THE SUN'S WARMING RAYS COULD WARM THE INTERIOR ROOMS DURING WINTER.

HERE ARE JUST A FEW HIGHLIGHTS OF HISTORIC SOLAR ENERGY DEVELOPMENTS:

DESTRUCTION OF ROMAN FLEET (212 B.C.) - ARCHIMEDES IS REPORTED TO HAVE IGNITED INVADING ROMAN SHIPS BY MEANS OF REFLECTED SUNLIGHT.

DIAMOND MELTED (1695) - TWO ITALIAN EXPERIMENTERS SUCCEEDED IN MELTING A DIAMOND USING FOCUSED SUNLIGHT.

SOLAR FURNACE (1774) - THE FRENCH CHEMIST ANTOINE-LAURENT LAVOISIER MADE A SOLAR FURNACE THAT MELTED PLATINUM.

SOLAR-POWERED PRINTING PRESS (1878) - A LARGE PARABOLIC REFLECTOR COLLECTED ENOUGH SUNLIGHT TO POWER A PRINTING PRESS.

SOLAR STEAM ENGINE (1901) - A. G. ENEAS DESIGNED A SOLAR STEAM ENGINE THAT PUMPED IRRIGATION WATER IN ARIZONA. SUNLIGHT WAS COLLECTED BY 1,788 MIRRORS INSTALLED IN A FIXTURE THAT RESEMBLED A GIANT UMBRELLA 33.5 FEET (ABOUT 10 METERS) IN DIAMETER.

SOLAR ENGINE (1908) - JOHN BOYLES AND H. E. WILLSIE DEMONSTRATED A 15-HORSE-POWER ENGINE POWERED BY POOLS OF WATER THAT CAPTURED AND STORED THE HEAT FROM SUNLIGHT.

SOLAR ELECTRICAL PLANT (1913) - FRANK SHUMAN AND C.V. BOYS BUILT THE WORLD'S FIRST SOLAR-POWERED ELECTRICAL PLANT NEAR CAIRO, EGYPT. THE HUGE FACILITY USED SEVEN SOLAR COLLECTORS, EACH 204 FEET (ABOUT 62 METERS) LONG. THE COLLECTORS HAD A TOTAL AREA OF 13,000 SQUARE FEET (ABOUT 1,208 SQUARE METERS). THEY AUTOMATICALLY TRACKED THE SUN.

SOLAR OVEN (1925) - C. G. ABBOT OF THE SMITHSONIAN INSTITUTION COOKED MEALS USING A SOLAR-POWERED OVEN AT HIS SUN OBSERVATORY ON MOUNT WILSON, CALIFORNIA.

SOLAR FURNACE (1950's) - FRENCH SCIENTIST FELIX TROMBE DESIGNED THE WORLD'S LARGEST SOLAR FURNACE. THIS FACILITY, WHOSE 9,000 MIRRORS ARE INSTALLED ON THE SIDE OF A BUILDING, CAN REACH THE TEMPERATURE OF THE SUN'S SURFACE, $10,000^{\circ}$ FAHRENHEIT (ABOUT $5,538^{\circ}$ CELSIUS).

SILICON SOLAR CELL (1954) - GERALD PEARSON, DARYL CHAPIN AND CALVIN FULLER OF BELL LABORATORIES DEVELOPED THE FIRST SUCCESSFUL SILICON SOLAR CELL. THIS DEVELOPMENT LED TO THE MODERN ERA OF PHOTOVOLTAIC SOLAR POWER CONVERSION.

MID-EAST OIL CRISIS (1970's) - THE OIL CRISIS OF THE 1970'S STIMULATED SIGNIFICANT NEW RESEARCH IN SOLAR ENERGY. OLD KINDS OF SOLAR ENERGY SYSTEMS WERE IMPROVED AND NEW KINDS WERE DEVELOPED.


THIN-FILM SOLAR CELL (1980's) - MANY KINDS OF SOLAR CELLS HAVE BEEN DEVELOPED, BUT THIN-FILM CELLS OF SILICON AND OTHER SEMICONDUCTORS ARE AMONG THE MOST IMPORTANT. THEY CAN BE MADE AS FLEXIBLE SHEETS MUCH LARGER THAN STANDARD SILICON SOLAR CELLS.

ENERGY FROM THE SUN


THE SUN EMITS AN INCREDIBLE AMOUNT OF ELECTROMAGNETIC RADIATION. THE TOTAL RADIATED POWER IS 3.83×10^{23} KILOWATTS (KW) OR 383,000,000,000,000,000,000,000,000 WATTS. MOST OF THIS RADIATION IS LOST TO SPACE. ONLY A TINY FRACTION IS INTERCEPTED BY EARTH AND THE OTHER PLANETS. ACCORDING TO THE SOLAR ENERGY INDUSTRIES ASSOCIATION (SEIA), ALL THE ELECTRICITY CONSUMED IN THE UNITED STATES COULD BE PROVIDED BY PHOTOVOLTAIC SOLAR CELL MODULES COVERING 0.3 % OF THE LAND AREA OF THE U.S.

THE SOLAR CONSTANT

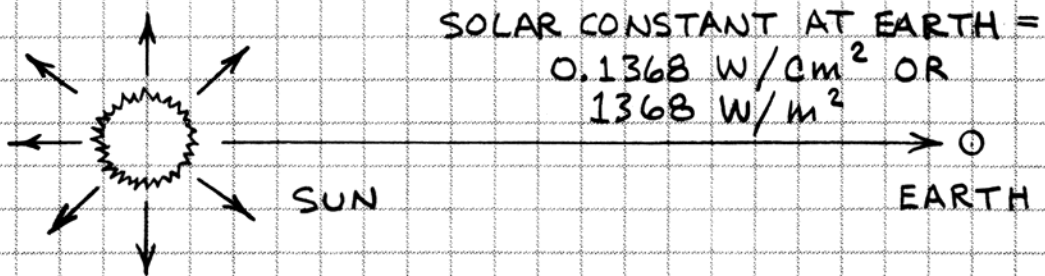THE MEAN AMOUNT OF SUNLIGHT AT THE TOP OF EARTH'S ATMOSPHERE IS CALLED THE SOLAR CONSTANT. MEASUREMENTS MADE BY SEVERAL SATELLITES SHOW THAT THE SOLAR CONSTANT IS 136.8 WATTS PER SQUARE CENTIMETER.



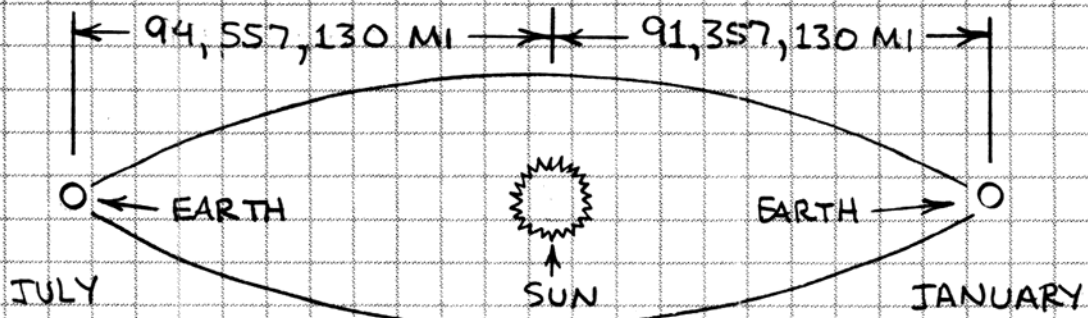THE SUNLIGHT INTENSITY AT EARTH VARIES BECAUSE EARTH'S ORBIT AROUND THE SUN IS SLIGHTLY ELLIPTICAL. THE MEAN DISTANCE OF EARTH FROM THE SUN IS 92,957,130 MILES (149,600,000 KILOMETERS). IN EARLY JANUARY EARTH IS ABOUT 1,600,000 MILES (2,575,000 KM) CLOSER TO THE SUN. IN EARLY JULY EARTH IS ABOUT 1,600,000 MILES (2,575,000 KM) FARTHER FROM THE SUN. (SEE DRAWING ON FACING PAGE.)



THE DIFFERENCE IN THE INTENSITY OF SUNLIGHT BETWEEN PERIHELION (CLOSEST POINT) AND APHELION (FARTHEST POINT) IS ABOUT 6.7%. USE THE SOLAR CONSTANT TABLE TO FIND THE SOLAR CONSTANT FOR THE FIRST DAY OF ANY MONTH.

SOLAR CONSTANT TABLE

MULTIPLY THE MEAN SOLAR CONSTANT (1,368 WATTS PER SQUARE METER OR 136.8 MILLIWATTS PER SQUARE CENTIMETER) BY THE CORRECTION NUMBERS IN THIS TABLE TO FIND THE ACTUAL SOLAR IRRADIANCE ON THE GIVEN DATES.

JANUARY	1.0335	JULY	0.9666
FEBRUARY	1.0288	AUGUST	0.9709
MARCH	1.0173	SEPTEMBER	0.9828
APRIL	1.0009	OCTOBER	0.9995
MAY	0.9841	NOVEMBER	1.0164
JUNE	0.9741	DECEMBER	1.0288

FROM KINSELL L. COULSON, "SOLAR AND TERRESTRIAL RADIATION," ACADEMIC PRESS, 1975.


EXAMPLE: WHAT IS THE SUN'S IRRADIANCE AT THE TOP OF THE ATMOSPHERE ON MAY 1? THE IRRADIANCE ON MAY 1 IS 0.9841 OF THE MEAN SOLAR CONSTANT OF 136.8 MILLIWATTS PER SQUARE CENTIMETER. 0.9841×136.8 IS 134.625 MILLIWATTS PER SQUARE CENTIMETER.

SUNLIGHT AND THE ATMOSPHERE


A SOLAR CELL ON A SATELLITE RECEIVES AT LEAST 15% MORE SOLAR ENERGY THAN AN IDENTICAL SOLAR CELL ON EARTH. FOR EXAMPLE, AT NOON ON JULY 1 THE SOLAR IRRADIANCE AT ALBUQUERQUE, NEW MEXICO, IS ABOUT 100 MILLIWATTS PER SQUARE CM (100 mW/cm^2) IF THE SUN IS NOT BLOCKED BY A CLOUD. FROM THE SOLAR CONSTANT TABLE (P.9) THE IRRADIANCE AT THE TOP OF THE ATMOSPHERE ON JULY 1 IS $0.9666 \times 136.8 \text{ mW/cm}^2$ OR 132.2 mW/cm^2 . THUS ONLY 75.6% OF THE INTENSITY OF THE SUNLIGHT AT THE TOP OF THE ATMOSPHERE REACHES ALBUQUERQUE ON JULY 1. ALBUQUERQUE IS ABOUT 1 MILE (1.6 KILOMETERS) ABOVE SEA LEVEL AND THE AIR IS OFTEN DRY. LESS SUNLIGHT REACHES REGIONS NEARER SEA LEVEL, ESPECIALLY WHEN THE AIR IS MOIST. MUCH LESS SUNLIGHT IS RECEIVED EVERYWHERE DURING WINTER AND WHEN CLOUDS BLOCK THE SKY.

HERE ARE SOME OF THE CHIEF FACTORS THAT AFFECT SUNLIGHT:

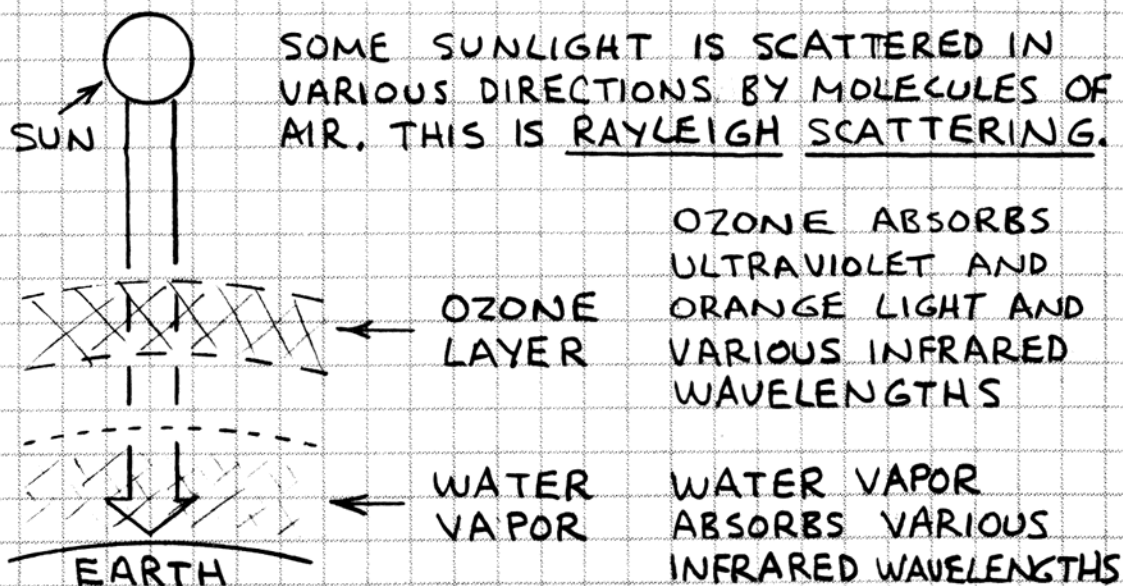
1. WATER VAPOR, OZONE AND OTHER GASES IN THE ATMOSPHERE ABSORB SUNLIGHT.



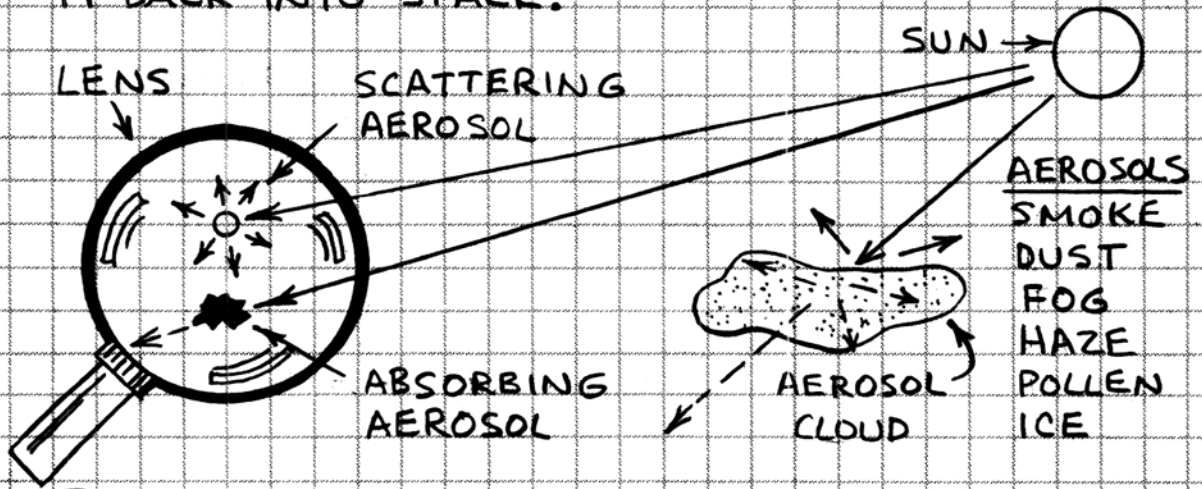
2. AEROSOLS ARE TINY PARTICLES AND DROPLETS IN THE ATMOSPHERE THAT CAN ABSORB CONSIDERABLE SUNLIGHT OR SCATTER IT BACK INTO SPACE.



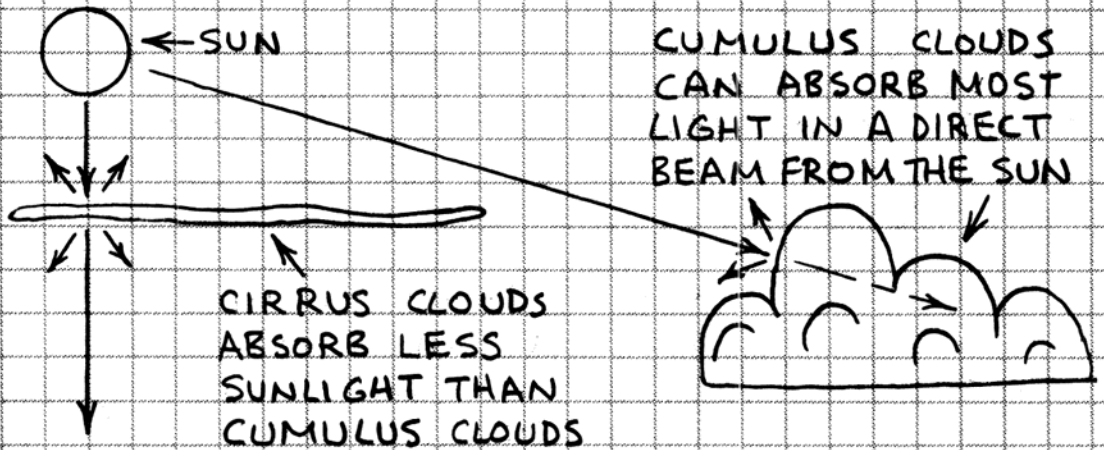3. CLOUDS ARE FORMED FROM ENORMOUS NUMBERS OF TINY WATER DROPLETS OR ICE CRYSTALS. CLOUDS ABSORB AND SCATTER LIGHT.



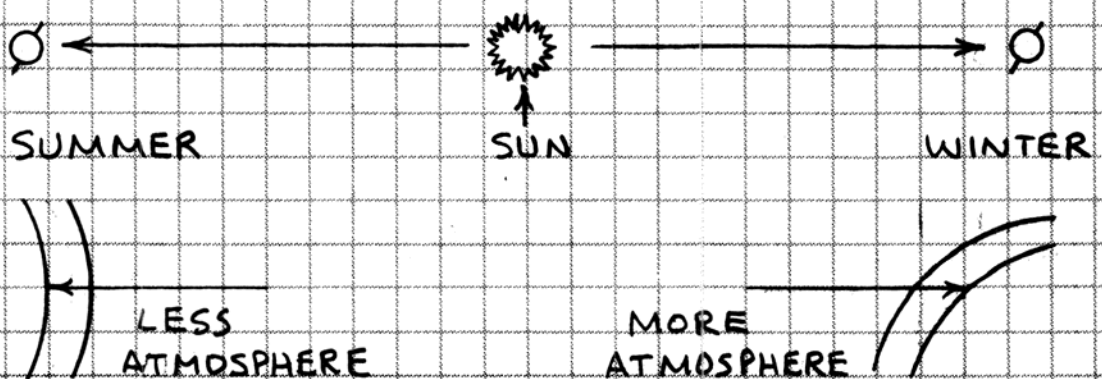4. THE TILT OF THE EARTH CAUSES SUNLIGHT TO PASS THROUGH MORE ATMOSPHERE DURING FALL, WINTER AND SPRING.




SOLAR CELLS



MANY SEMICONDUCTORS WILL GENERATE ELECTRICITY FROM SUNLIGHT. THE MOST COMMON AND BEST DEVELOPED SOLAR CELLS ARE MADE FROM SILICON. SINCE SILICON FORMS 27.7% OF EARTH'S CRUST, SILICON SOLAR CELLS ARE POTENTIALLY INEXPENSIVE. BUT TRANSFORMING SILICON INTO SOLAR CELLS IS AN EXPENSIVE PROCESS THAT REQUIRES CONSIDERABLE ELECTRICITY.



HOW SOLAR CELLS WORK

LIGHT CONSISTS OF PACKETS OF ENERGY CALLED PHOTONS THAT TRAVEL IN A WAVE-LIKE FASHION. WHEN PHOTONS STRIKE SILICON ATOMS THEY DISLODGE ELECTRONS. THE MISSING ELECTRONS LEAVE BEHIND POSITIVELY CHARGED ATOMS. THESE ATOMS ATTRACT FREE ELECTRONS IN THE SILICON. THIS RANDOM MOVEMENT OF ELECTRONS CAN BE CONVERTED INTO A FLOW OF ELECTRONS IF A PN JUNCTION IS FORMED IN THE SILICON. ELECTRONS DISLODGED BY PHOTONS NEAR THE PN JUNCTION ARE ATTRACTED TO THE P SIDE OF THE JUNCTION. THE RESULT IS A FLOW OF ELECTRICAL CURRENT WHEN LIGHT IS PRESENT. THE LEVEL OF CURRENT IN AMPERES IS DIRECTLY PROPORTIONAL TO THE LIGHT INTENSITY. THE POTENTIAL OF THE CURRENT IN VOLTS IS UNRELATED TO THE LIGHT INTENSITY. A TYPICAL SILICON SOLAR CELL GENERATES 0.45 TO 0.55 VOLT IN DIRECT SUNLIGHT.

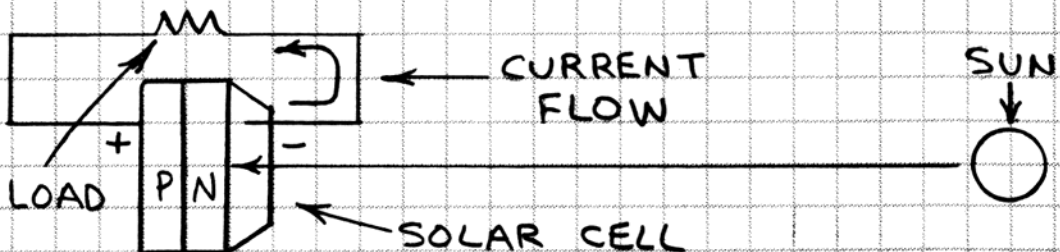

SOLAR CELL EFFICIENCY

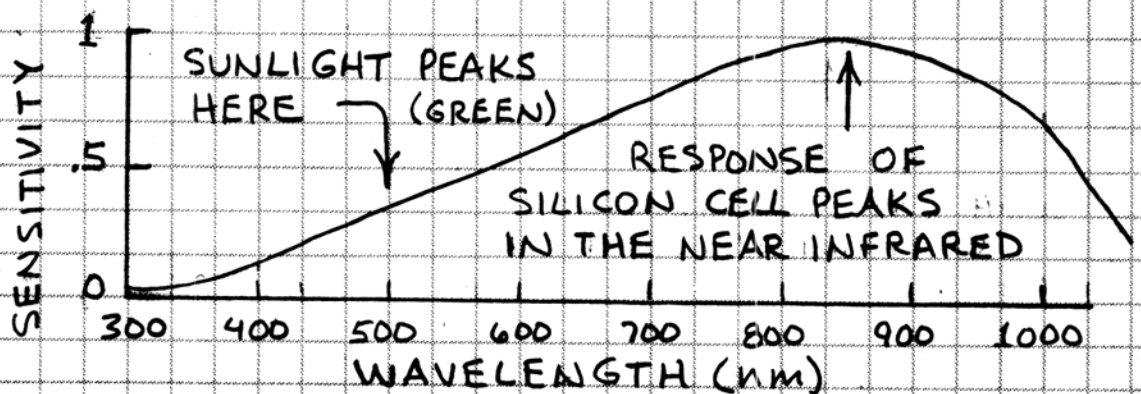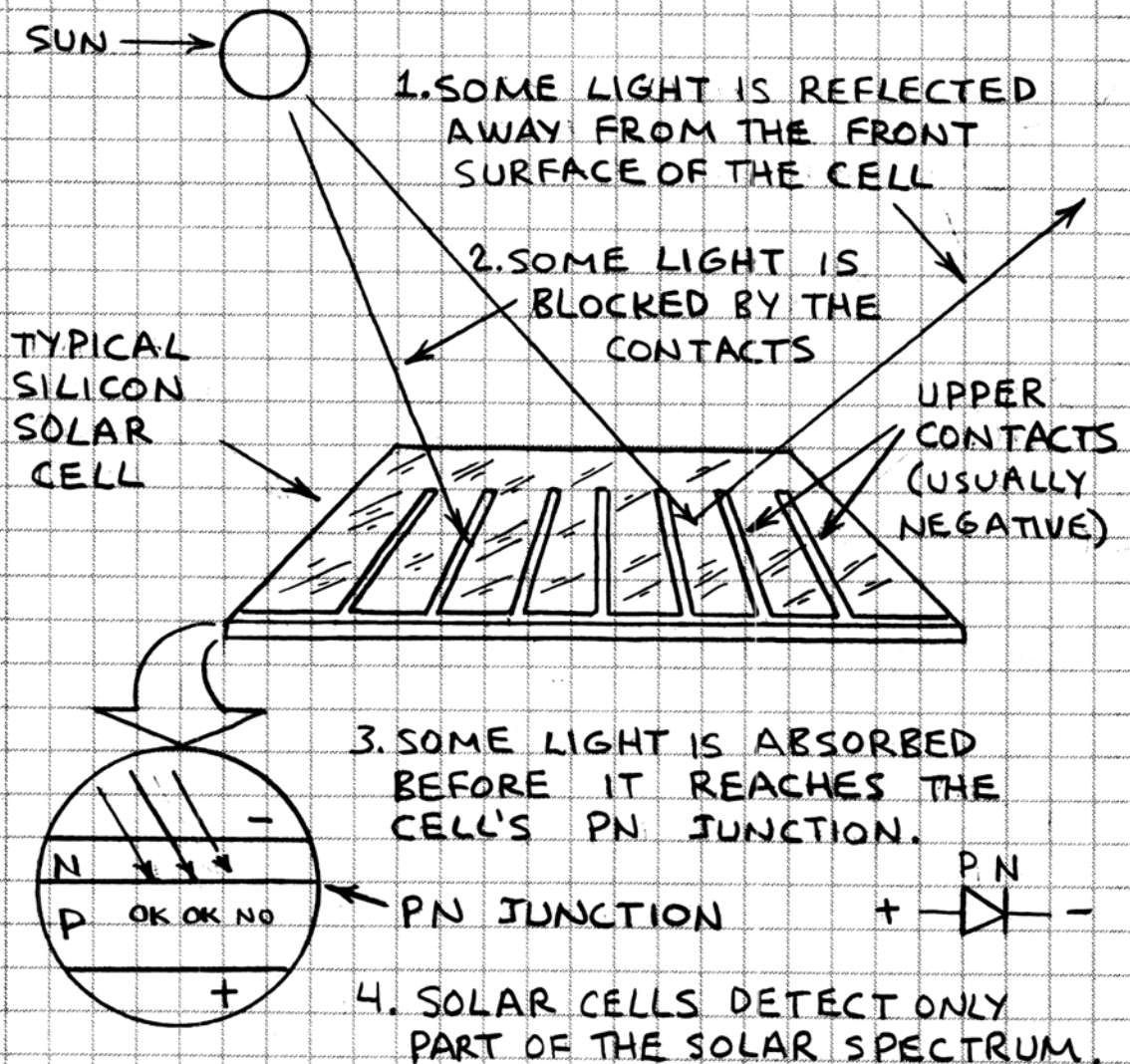
IF EVERY PHOTON STRIKING A SOLAR CELL DISLODGES AN ELECTRON, THE CELL WILL TRANSFORM NEARLY 100 % OF THE LIGHT THAT STRIKES IT INTO ELECTRICITY. THE ACTUAL EFFICIENCY OF REAL SOLAR CELLS IS FROM ABOUT 5 % TO 20 %. THERE ARE SEVERAL REASONS FOR REDUCED EFFICIENCY:



SILICON SOLAR CELL RATINGS


IT IS IMPORTANT TO READ AND UNDERSTAND SOLAR CELL RATINGS, ESPECIALLY WHEN THE CELLS ARE TO BE USED TO CHARGE A STORAGE CELL OR BATTERY.

SILICON SOLAR CELL VOLTAGE

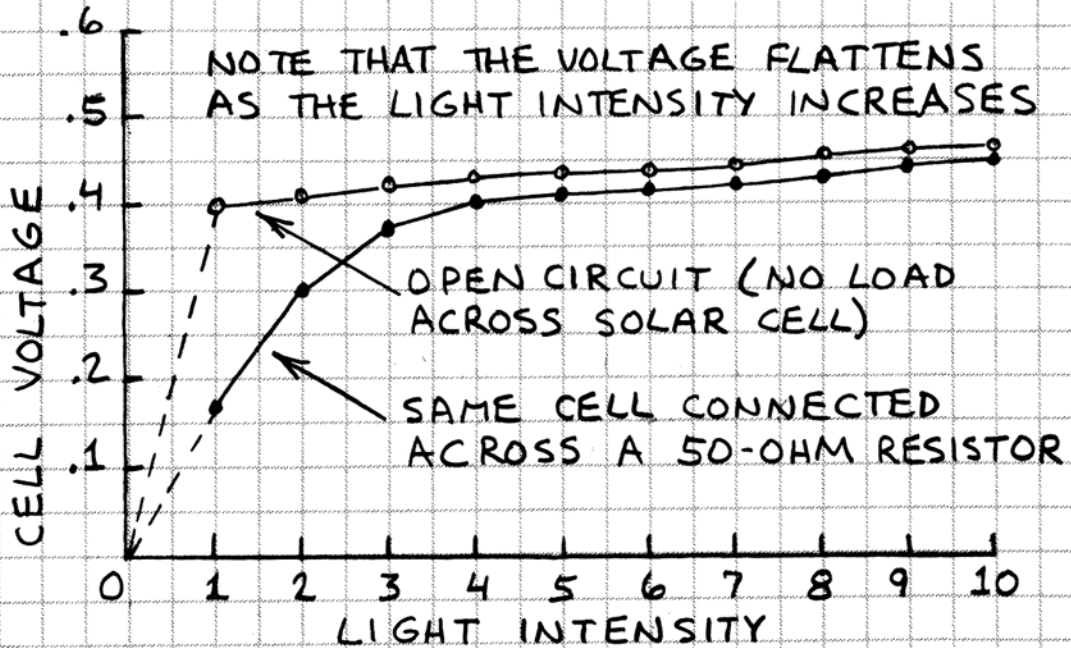


INCREASING SOLAR CELL VOLTAGE

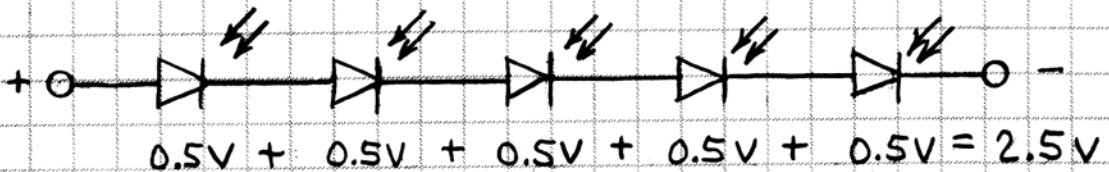WHEN SOLAR CELLS ARE USED TO CHARGE STORAGE CELLS OR BATTERIES, SEVERAL CELLS MUST BE CONNECTED IN SERIES TO OBTAIN A SUFFICIENTLY HIGH VOLTAGE.




TYPICAL SERIES ARRAY:

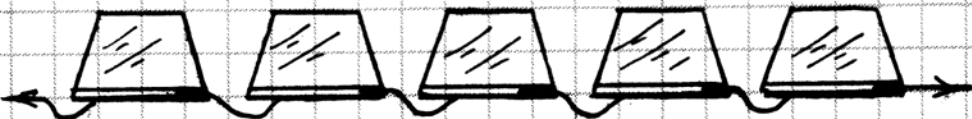


A STRING OF SOLAR CELLS CONNECTED IN SERIES OR IN PARALLEL (SEE BELOW) IS CALLED AN ARRAY. ALL THE CELLS IN AN ARRAY SHOULD BE EQUALLY ILLUMINATED. SHADING ONE CELL IN A 6.5-VOLT ARRAY DROPPED THE OUTPUT TO 6.2 VOLTS.

SILICON SOLAR CELL CURRENT

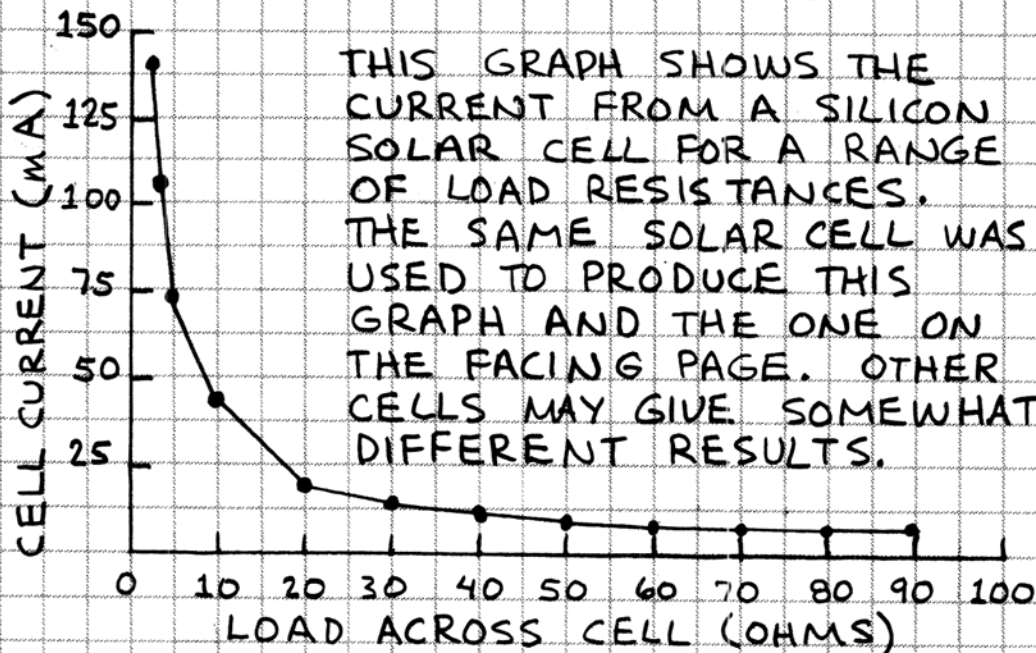


INCREASING SOLAR CELL CURRENT

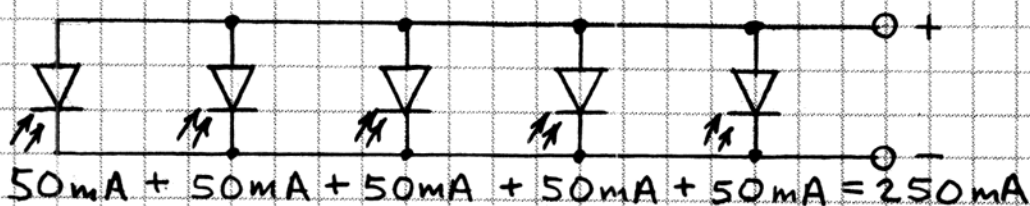CONNECTING SOLAR CELLS IN PARALLEL INCREASES THE OUTPUT CURRENT. THIS IS ESPECIALLY USEFUL WHEN CHARGING LARGE STORAGE BATTERIES.



TYPICAL PARALLEL ARRAY:

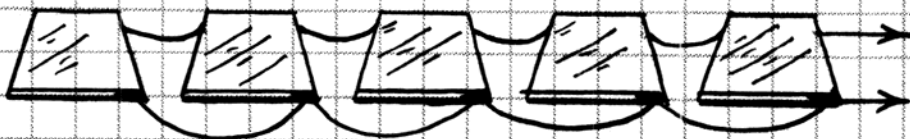

SOLDERING LEADS TO SOLAR CELLS

SOLAR CELLS OR SOLD WITH OR WITHOUT LEADS. SOLDERING LEADS TO SOLAR CELLS IS TRICKY, BUT YOU CAN SAVE MONEY IF YOU ARE WILLING TO SOLDER THE LEADS YOURSELF USING THE REFLOW SOLDERING METHOD DESCRIBED HERE. SOLAR CELLS ARE FRAGILE, SO USE CARE.

SUITABLE SOLDERING IRONS AND SOLDER ARE AVAILABLE FROM RADIOSHACK. SELECT A LOW-WATTAGE IRON OF ABOUT 15 TO 30 WATTS. USE 0.032-INCH OR SMALLER ROSIN CORE SOLDER. DO NOT USE ACID-CORE SOLDER.


BE SURE TO TIN THE TIP OF THE SOLDERING IRON. FIRST, ALLOW THE IRON TO BECOME HOT ENOUGH TO MELT SOLDER. THEN MELT SOLDER OVER THE TIP OF THE SOLDERING IRON. CAREFULLY BRUSH OFF THE EXCESS SOLDER WITH A SOFT CLOTH. AVOID SPLASHING SOLDER ON YOURSELF OR OTHERS. A PROPERLY TINNED TIP WILL APPEAR SMOOTH AND SHINY.

FOLLOW THESE STEPS TO SOLDER LEADS TO A SOLAR CELL:

1. FIND A SAFE PLACE TO WORK. IT IS ESPECIALLY IMPORTANT THAT THE SOLDERING IRON'S POWER CORD BE SAFELY PLACED. SO BE SURE AN ELECTRICAL OUTLET IS NEARBY. CAUTION: A HOT SOLDERING IRON CAN BURN SKIN OR CLOTHING!


2. SILICON SOLAR CELLS HAVE ELECTRODES ON BOTH SIDES. THE ELECTRODE ON THE LIGHT-SENSITIVE, UPPER SURFACE IS A THIN STRIP OF METAL ALONG ONE EDGE OF THE CELL. PLACE THE CELL WITH THE TOP SIDE UP ON YOUR WORK SURFACE (A PIECE OF SCRAP WOOD IS BEST) AND USE A PIECE OF MASKING TAPE TO HOLD IT IN PLACE WHILE YOU SOLDER.

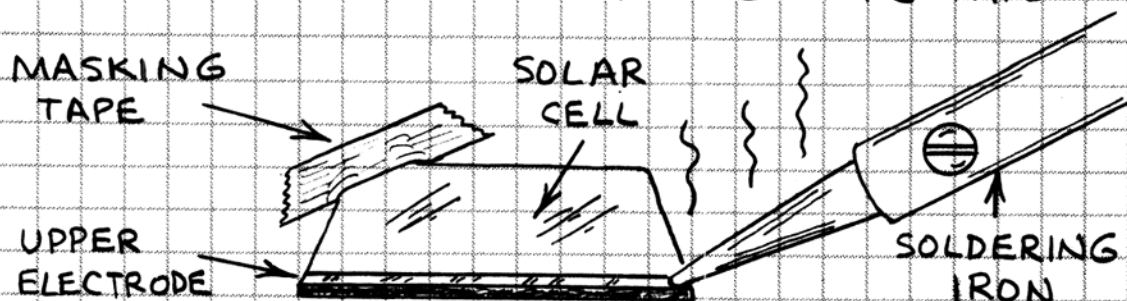3. WHEN THE SOLDERING IRON IS HOT, GENTLY TOUCH THE EDGE OF THE TIP TO ONE END OF THE UPPER ELECTRODE. LIKE THIS:



4. AFTER A SECOND OR SO, TOUCH THE END OF A LENGTH OF SOLDER TO WHERE THE SOLDERING IRON TOUCHES THE ELECTRODE. ALLOW SOME SOLDER TO MELT ONTO THE ELECTRODE AND REMOVE THE IRON.

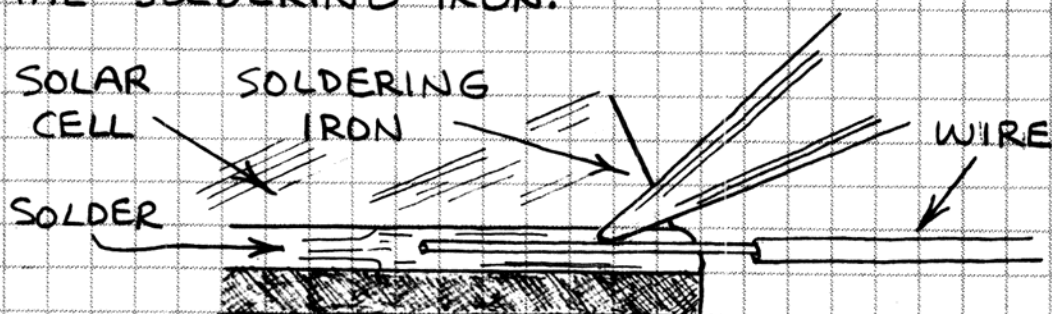5. REMOVE ABOUT 0.2 INCH (5 mm) OF THE INSULATION FROM THE END OF SOME WRAPPING WIRE. PLACE THE EXPOSED END OF THE WIRE ALONG THE TOP OF THE SOLDER THAT YOU MELTED ONTO THE ELECTRODE AND THEN GENTLY PRESS THE SOLDERING IRON AGAINST THE WIRE AND REMELT THE SOLDER. WHEN THE WIRE PUSHES INTO THE MOLTEN SOLDER, HOLD THE WIRE VERY STILL AND REMOVE THE SOLDERING IRON.



6. AFTER THE SOLAR CELL COOLS, GENTLY REMOVE THE TAPE, FLIP THE CELL OVER AND TAPE IT IN PLACE AGAIN. FOLLOW STEPS 3-5 ABOVE TO SOLDER A LENGTH OF WRAPPING WIRE TO THE BACK ELECTRODE. AFTER THE WIRE SINKS INTO THE MOLTEN SOLDER, BE SURE TO KEEP THE WIRE VERY STILL WHILE THE SOLDER COOLS.

MOUNTING SOLAR CELLS


SOLAR CELLS ARE AVAILABLE UNMOUNTED OR INSTALLED IN VARIOUS KINDS OF PROTECTIVE ENCLOSURES. IT'S BEST TO INSTALL UNMOUNTED CELLS IN AN ENCLOSURE OR TO MOUNT THEM ON A PROTECTIVE PANEL. TWO METHODS THAT I HAVE USED ARE DESCRIBED HERE.

ADVANTAGES OF MOUNTED CELLS

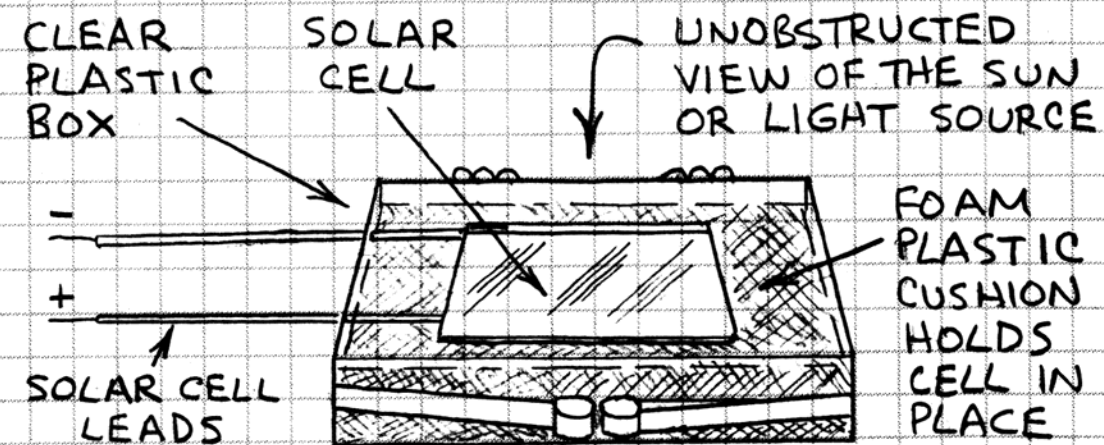1. SOLAR CELLS ARE BRITTLE AND EASILY BROKEN. MOUNTING THEM GREATLY REDUCES THE RISK OF BREAKAGE.
2. WIRE LEADS SOLDERED TO A SOLAR CELL ARE EASILY PULLED AWAY. MOUNTING THE CELL WILL PROTECT THE LEADS.
3. AN ENCLOSURE OR PANEL CAN BE MOUNTED ON THE CIRCUIT IT IS DESIGNED TO POWER.
4. AN ENCLOSURE OR PANEL PROTECTS THE SOLAR CELL(S) FROM MOISTURE AND DUST.

INSTALLING CELLS IN AN ENCLOSURE

ONE OR MORE SOLAR CELLS CAN BE EASILY INSTALLED IN A TRANSPARENT BOX.




THE DRAWING ON THE FACING PAGE SHOWS A SOLAR CELL SANDWICHED BETWEEN A FOAM PLASTIC CUSHION AND THE LID OF A CLEAR PLASTIC BOX. YOU CAN ALSO SANDWICH THE CELL(S) BETWEEN THE LID AND A PLASTIC OR CARDBOARD LINER INSERTED IN THE LID AND CEMENTED IN PLACE.

I HAVE USED INDIVIDUAL RADIOSHACK SOLAR CELLS INSTALLED IN PLASTIC BOXES AS LIGHT SENSORS WITHOUT EVER DAMAGING A CELL OR BREAKING ITS LEADS. SERIES OR PARALLEL ARRAYS OF CELLS CAN BE INSTALLED IN LARGER PLASTIC BOXES. SOLDER THE CELLS TO ONE ANOTHER WITH SHORT LENGTHS OF WRAPPING WIRE. SECURE THE CELLS IN PLACE AS SHOWN ON THE FACING PAGE OR USE A LINER AS DESCRIBED ABOVE. BE SURE THE CONNECTION WIRES DO NOT BLOCK ANY OF THE CELLS.

MOUNTING SOLAR CELLS ON A PANEL

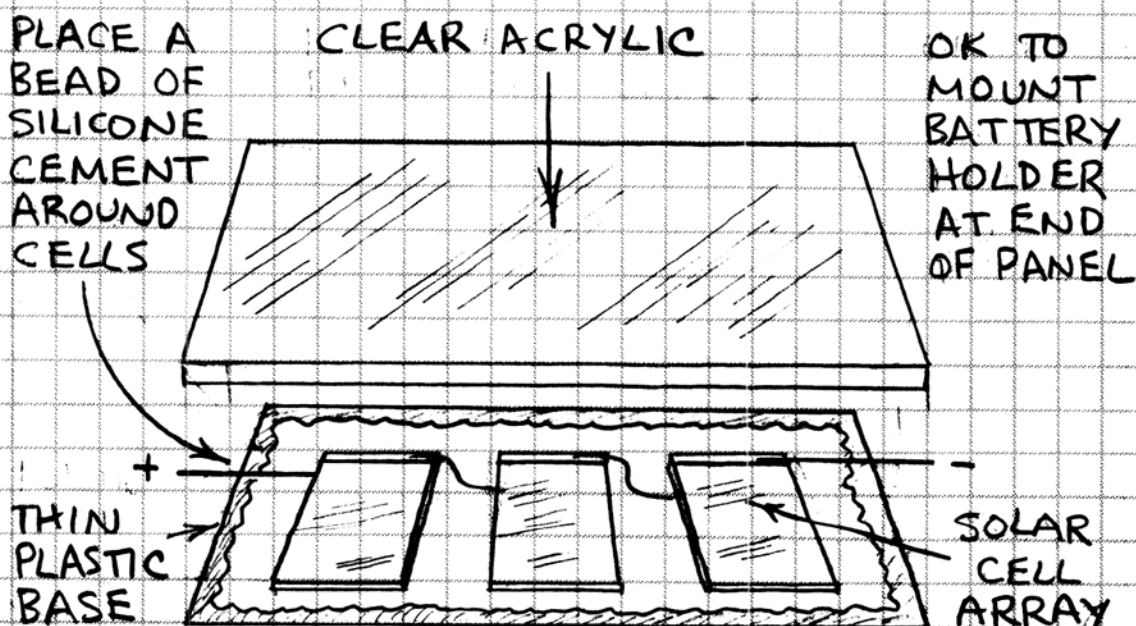FOR MANY YEARS I HAVE USED HOMEMADE SOLAR CELL PANELS TO CHARGE FLASHLIGHT CELLS ON BICYCLE TRIPS. HERE'S HOW THEY ARE MADE:



SOLAR CELL BATTERY CHARGERS


LEAD-ACID AND NICKEL CADMIUM (NiCd) ARE THE MOST COMMON STORAGE BATTERIES. CERTAIN ALKALINE, LITHIUM AND OTHER TYPES CAN ALSO BE USED AS RECHARGEABLE STORAGE BATTERIES. WHEN CHARGING A STORAGE BATTERY YOU MUST OBSERVE SEVERAL PRECAUTIONS TO AVOID DAMAGE TO THE BATTERY OR ONE OF ITS CELLS. THESE PRECAUTIONS WILL ALSO GREATLY REDUCE THE POSSIBILITY OF FIRE OR EVEN EXPLOSION, WHICH CAN OCCUR WHEN A STORAGE BATTERY IS IMPROPERLY CHARGED.

STORAGE BATTERY PRECAUTIONS

1. CHARGE ONLY CELLS AND BATTERIES DESIGNED TO BE RECHARGED. CAUTION: NEVER ATTEMPT TO CHARGE OTHER KINDS OF BATTERIES! THEY MAY OVERHEAT, SWELL AND POSSIBLY EXPLODE.

2. NEVER EXCEED THE MAXIMUM ALLOWED CHARGING CURRENT FOR A STORAGE CELL OR BATTERY. INSTEAD OF REDUCING THE CHARGING TIME, THE CELL OR THE BATTERY MAY BE RUINED.


3. CHARGE MULTIPLE STORAGE CELLS IN SERIES INSTEAD OF IN PARALLEL.

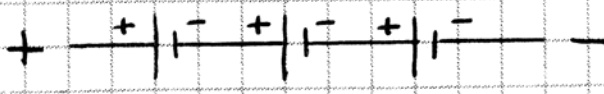CELLS IN SERIES: 

4. KEEP BATTERIES AWAY FROM DIRECT SUNLIGHT WHILE BEING CHARGED.

5. IF A BATTERY BECOMES ^{SSS}HOT WHILE BEING CHARGED, IMMEDIATELY DISCONNECT IT OR REMOVE IT FROM THE SOLAR CHARGER. ALLOW IT TO COOL BEFORE USING IT.

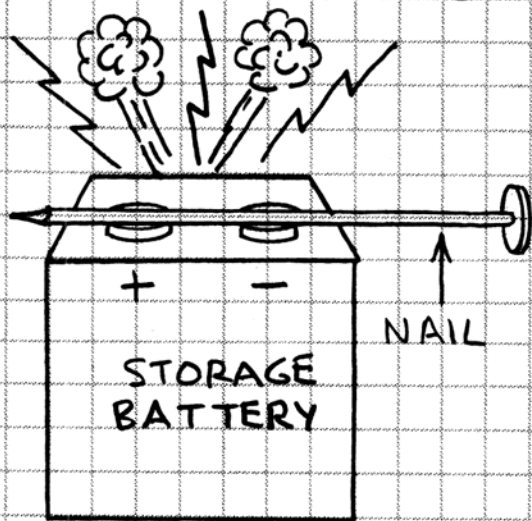6. NEVER SHORT THE TERMINALS OF A STORAGE CELL OR BATTERY! STORAGE CELLS HAVE A VERY LOW INTERNAL RESISTANCE. THIS MEANS THEY CAN PRODUCE A VERY HIGH CURRENT IF THEIR TERMINALS ARE SHORTED.



CAUTION!

DO NOT SHORT THE TERMINALS OF A STORAGE CELL OR BATTERY WITH A NAIL, COIN, METAL FOIL OR OTHER CONDUCTOR.

7. USE TAPE TO INSULATE THE EXPOSED TERMINALS OF STORAGE CELLS AND BATTERIES. OTHERWISE THE TERMINALS MIGHT BECOME ACCIDENTALLY SHORTED TOGETHER. WHEN POSSIBLE, USE AN INSULATED BATTERY HOLDER OR CONNECTION CLIPS WITH INSULATED LEADS.

8. IT'S BEST TO CHARGE NICKEL CADMIUM STORAGE CELLS AND BATTERIES WHEN THEY ARE FULLY DISCHARGED. THIS INCREASES THE TIME THESE CELLS WILL FUNCTION BETWEEN CHARGES.

9. NEVER GUESS ABOUT THE SPECIFICATIONS OF AN UNKNOWN OR UNMARKED BATTERY. THE SPECIFICATIONS OF BATTERIES SOLD BY RADIOSHACK ARE LISTED IN THE RADIOSHACK CATALOG. YOU CAN FIND THE SPECIFICATIONS OF BATTERIES VIA THE WORLD WIDE WEB. BEGIN YOUR SEARCH BY SELECTING ONE OF THE WEB SEARCH ENGINES. TYPE IN THE MANUFACTURER'S NAME AND THE WORD "BATTERY" OR "CELL" TO NARROW YOUR SEARCH.

SOLAR CELL BATTERY CHARGERS

SERIES ARRAYS OF SOLAR CELLS ARE USED TO CHARGE STORAGE CELLS AND BATTERIES. THE ARRAY MUST GENERATE A SLIGHTLY HIGHER VOLTAGE THAN THAT OF THE BATTERY BEING CHARGED. HERE ARE THE NUMBER OF SERIES-CONNECTED CELLS COMMONLY USED TO CHARGE SOME POPULAR BATTERY CONFIGURATIONS:


1 1.2-VOLT NiCd CELL - 4 SOLAR CELLS

2 1.2-VOLT NiCd CELLS IN SERIES - 9 SOLAR CELLS

4 1.2-VOLT NiCd CELLS IN SERIES - 18 SOLAR CELLS

1 12-VOLT LEAD-ACID BATTERY - 36 SOLAR CELLS

SOLAR 2xAA CHARGER

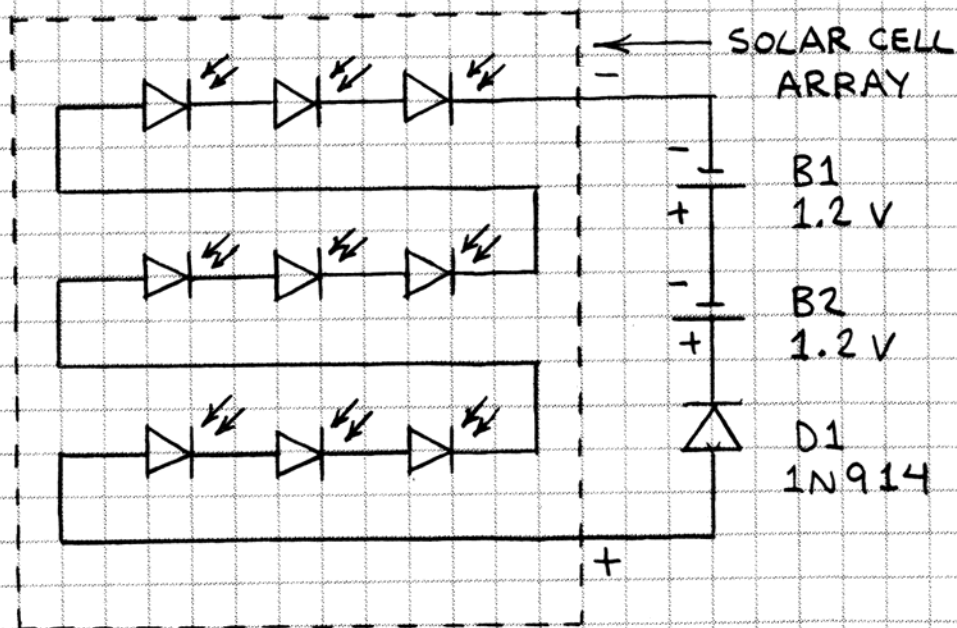

THIS CIRCUIT WILL CHARGE 2 AA NiCd CELLS. IF THE CELLS ARE FULLY DISCHARGED, SOLAR CELLS THAT GENERATE 50 TO 100 mA WILL CHARGE THE CELLS IN ABOUT 5 TO 8 HOURS.

D1 PREVENTS THE NiCd CELLS FROM DISCHARGING THROUGH THE SOLAR CELLS.

SOLAR BATTERY CHARGER TIPS

1. NEVER EXCEED THE RECOMMENDED CHARGE RATE FOR A STORAGE CELL.
2. INCREASED CURRENT REDUCES CHARGING TIME. CHECK THE BATTERY'S SPECIFICATIONS TO FIND THE MAXIMUM ALLOWABLE CURRENT.
3. DO NOT USE A SOLAR ARRAY THAT DELIVERS TOO MUCH CURRENT TO THE CELLS BEING CHARGED.
4. SEVERAL TIMES A DAY REORIENT A SOLAR PANEL SO IT FACES THE SUN.
5. SOLAR CELLS WORK BEST WHEN COOL. AVOID PLACING A SOLAR PANEL ON SURFACES THAT BECOME HOT IN SUNLIGHT, SUCH AS PAVEMENT OR DARK PAINTED METAL.
6. STORAGE BATTERIES CAN BE MOUNTED ON THE BACK SIDE OF A SOLAR PANEL. BUT THEY WORK BEST WHEN KEPT IN A COOLER LOCATION WHILE BEING CHARGED.

MONITORING A SOLAR CHARGER

YOU CAN MEASURE THE CURRENT FROM A SOLAR PANEL WITH A MULTIMETER.

1. CONNECT A MULTIMETER SET TO MEASURE CURRENT BETWEEN THE BLOCKING DIODE AND THE BATTERY BEING CHARGED. BE SURE TO OBSERVE POLARITY, OR...
2. CONNECT A 1-OHM POWER RESISTOR BETWEEN THE BLOCKING DIODE AND THE BATTERY BEING CHARGED. USE A MULTIMETER TO MEASURE THE VOLTAGE (V) ACROSS THE RESISTOR (R). FROM OHM'S LAW, CURRENT EQUALS V/R OR, IN THIS CASE, V .

TAKE A SOLAR CELL INTO SPACE


SOLAR CELLS ARE SENSITIVE TO ONLY PART OF THE SOLAR SPECTRUM. THEREFORE A SOLAR CELL CAN NOT MEASURE THE POWER OF THE TOTAL AMOUNT OF SUNLIGHT AT THE TOP OF THE ATMOSPHERE (THE SOLAR CONSTANT), EVEN IF YOU COULD TAKE ONE THERE.

ACCORDING TO SOLAREX, A MAJOR SOLAR CELL MANUFACTURER, A SOLAR CELL PRODUCES ABOUT +14.6% MORE POWER IN SPACE THAN THE SAME CELL PRODUCES ON EARTH. LET'S CALL THIS PERFORMANCE INCREASE A SOLAR CELL'S SPACE EFFICIENCY.

YOU DON'T NEED TO BECOME AN ASTRONAUT TO DETERMINE HOW MUCH MORE POWER A SOLAR CELL WILL PRODUCE IN SPACE. THE METHOD DESCRIBED HERE WILL REVEAL A SOLAR CELL'S SPACE EFFICIENCY FROM EARTH.

- FOLLOW THESE STEPS:

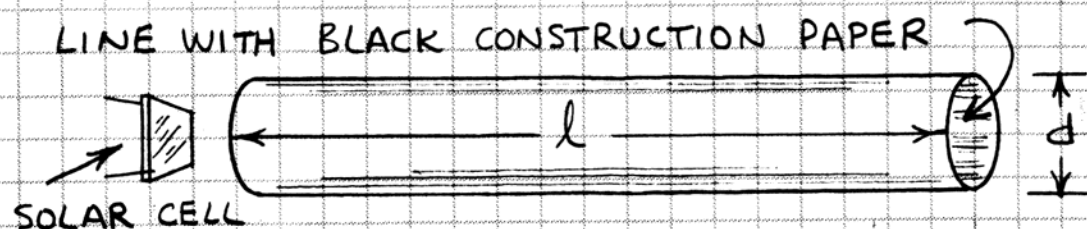1. MOUNT A SOLAR CELL AT THE END OF A PVC OR CARDBOARD TUBE:




l SHOULD BE AT LEAST 5 TIMES d .

USE DOUBLE SIDED TAPE TO ATTACH A BARE SOLAR CELL TO A THIN CARDBOARD DISK. USE DARK TAPE TO ATTACH THE CELL AND DISK TO THE END OF THE TUBE. ALTERNATIVELY, INSTALL THE SOLAR CELL IN A THIN, CLEAR PLASTIC BOX AND TAPE THE BOX TO THE END OF THE TUBE. IF THE SOLAR CELL IS LARGER THAN d , THE EXPOSED PORTION OF THE CELL MUST BE SHIELDED FROM LIGHT.

ONE WAY IS TO WRAP THE SOLAR CELL END OF THE TUBE WITH ALUMINUM FOIL. TAPE THE FOIL TO THE SIDE OF THE TUBE. BE SURE IT DOES NOT CONNECT TOGETHER OR SHORT THE SOLAR CELL LEADS.

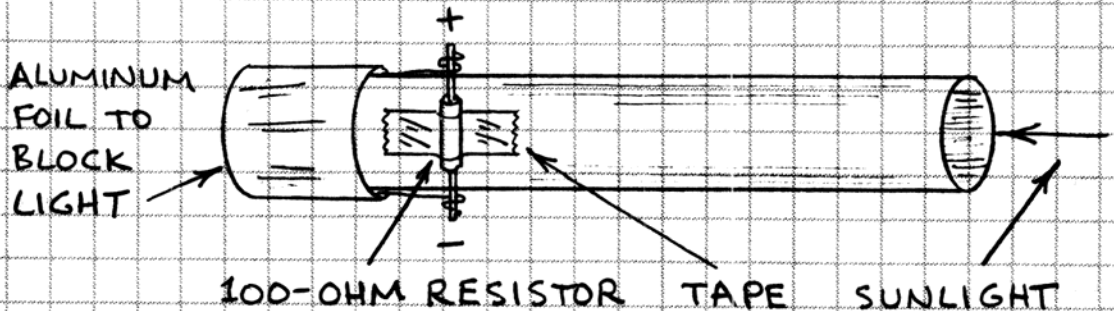2. CONNECT THE SOLAR CELL LEADS ACROSS A 100-OHM RESISTOR. TAPE THE RESISTOR TO THE SIDE OF THE TUBE AS SHOWN:



3. ON A CLEAR DAY MEASURE THE VOLTAGE ACROSS THE 100-OHM RESISTOR WHEN THE TUBE IS POINTED DIRECTLY AT THE SUN. THE TUBE IS PROPERLY POINTED WHEN ITS SHADOW DISAPPEARS AND WHEN THE VOLTAGE ACROSS THE 100-OHM RESISTOR REACHES A PEAK.

MAKE MEASUREMENTS FROM EARLY MORNING TO NOON OR FROM NOON TO LATE AFTERNOON. IF YOU DO NOT HAVE INTERNET ACCESS YOU WILL NEED TO MEASURE THE ANGLE OF THE SUN OVER THE HORIZON AT EACH MEASUREMENT. RECORD YOUR DATA IN A NOTEBOOK UNDER THESE HEADINGS:


DATE:				
LOCATION: (TOWN AND COORDINATES)				
SKY CONDITION: (CLEAR? BLUE?)				
OBSERVER: (YOUR NAME)				
TIME	SIGNAL (VOLTS)	SIGNAL (LN)	SUN ANGLE	AIR MASS

4. AIR MASS (m) IS THE THICKNESS OF THE ATMOSPHERE BETWEEN YOU AND THE SUN. $m = 1 / \sin \theta$, WHERE θ IS THE ANGLE OF THE SUN ABOVE THE HORIZON. FIND m FOR EACH TIME YOU MADE A MEASUREMENT. USE THE SUN ANGLES YOU MEASURED. OR VISIT A SEARCH ENGINE ON THE WORLD WIDE WEB AND ENTER "SUN ANGLE CALCULATOR." CHECK THE WEB SITES AND SELECT A CALCULATOR YOU LIKE. FOLLOW THE INSTRUCTIONS TO FIND THE SUN ANGLE FOR EACH TIME. CALCULATE m FOR EACH ANGLE AND ENTER THE RESULTS IN YOUR NOTEBOOK.


5. USE THE LN KEY ON A SCIENTIFIC CALCULATOR TO CONVERT THE SIGNALS YOU MEASURED TO THEIR NATURAL LOGARITHMS. ENTER THE RESULTS IN YOUR NOTEBOOK, HERE ARE SOME OF MY RESULTS:

DATE: FEBRUARY 21, 1999				
LOCATION: GERONIMO CREEK, TEXAS				
SKY CONDITION: CLEAR AND BLUE				
OBSERVER: FORREST M. MIMS III				
TIME	SIGNAL (VOLTS)	SIGNAL (LN)	SUN ANGLE	AIR MASS
1550:20	4.60	1.5261	30.09°	1.99
1616:00	4.44	1.4907	25.39°	2.33

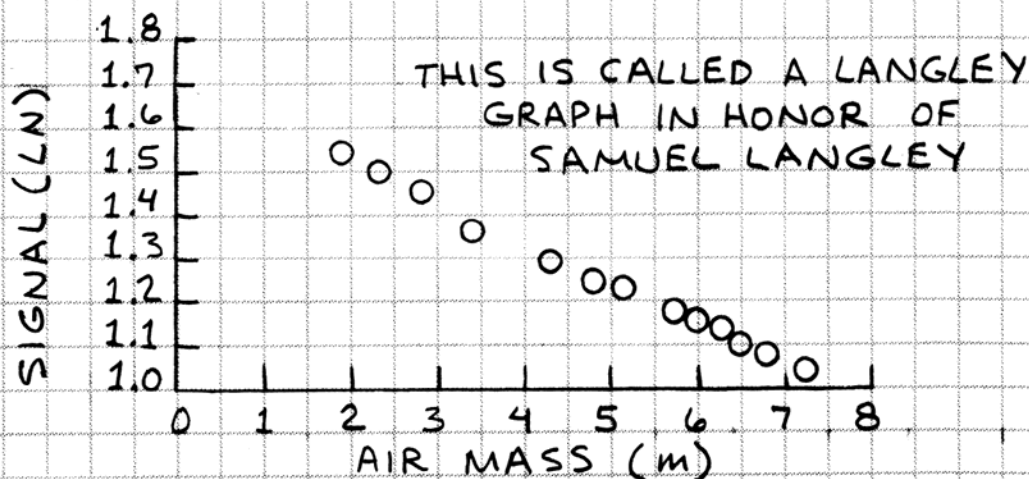6. GRAPH THE LN OF THE SIGNALS AND THEIR AIR MASSES. HERE'S MY GRAPH:



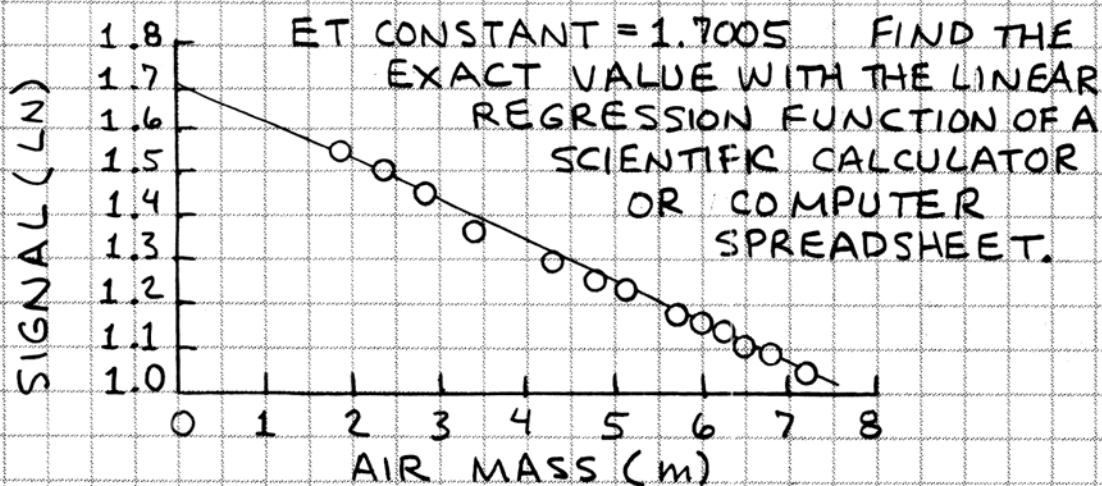IF THE SKY WAS CLEAR, THE POINTS BETWEEN AN AIR MASS OF ABOUT 2 TO 6 SHOULD FORM A STRAIGHT LINE. DRAW A LINE THROUGH THESE POINTS AND EXTEND IT TO THE Y (VERTICAL) AXIS OF THE GRAPH (AIR MASS = 0). THE LN OF THE SIGNAL THE SOLAR CELL WILL PRODUCE ABOVE THE ATMOSPHERE, THE CELL'S EXTRATERRESTRIAL (ET) CONSTANT, IS WHERE THE LINE CROSSES THE Y AXIS.




7. USE THE e^x KEY OF YOUR CALCULATOR TO CONVERT THE LN OF THE HIGHEST SIGNAL AT OR NEAR NOON AND THE ET CONSTANT TO THEIR ANTILOGS. DIVIDE THE ET CONSTANT BY THE NOON SIGNAL, SUBTRACT 1 AND ADD A % SIGN. THIS IS THE SOLAR CELL'S SPACE EFFICIENCY, THE INCREASE IN PERFORMANCE THE CELL WILL PROVIDE IN SPACE. THE SOLAR CELL I MEASURED HAS A SPACE EFFICIENCY OF +10.9%. THIS IS REASONABLY CLOSE TO THE +14.6% GIVEN BY SOLAREX. SOME OF THE DIFFERENCE IS BECAUSE THE LANGLEY METHOD WORKS BEST WITH A NARROW BAND OF WAVELENGTHS AND A SOLAR CELL DETECTS FROM ABOUT 400 TO 1100 NANOMETERS. DIFFERENCES ARE ALSO CAUSED BY DIFFERING AMOUNTS OF WATER VAPOR AND HAZE WHEN THE TESTS WERE CONDUCTED. WATER VAPOR IS ESPECIALLY IMPORTANT SINCE IT ABSORBS SOME NEAR INFRARED TO WHICH SOLAR CELLS ARE VERY SENSITIVE.

SOLAR POWERED MOTORS

SMALL DC MOTORS CAN BE POWERED BY SOLAR CELLS. SOME MOTORS REQUIRE ONLY A SINGLE CELL AND BRIGHT SUNLIGHT. MOST REQUIRE AN ARRAY OF SOLAR CELLS.


BASIC SOLAR POWERED MOTOR

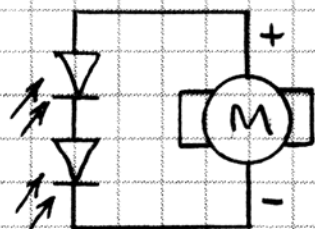

A SINGLE SOLAR CELL GENERATES ENOUGH CURRENT TO POWER MOST SMALL DC MOTORS. ADD CELLS IN SERIES IF MORE VOLTAGE IS REQUIRED.


HIGHER POWER SOLAR MOTOR

A SOLAR CELL ARRAY THAT POWERS A MOTOR ON A BRIGHT SUMMER DAY MAY NOT PROVIDE ADEQUATE POWER DURING WINTER. THIS CIRCUIT FEATURES TWO SERIES ARRAYS CONNECTED IN PARALLEL TO PROVIDE DOUBLE THE CURRENT PRODUCED BY A SINGLE ARRAY. IF IDENTICAL 0.5 VOLT CELLS ARE USED AND IF EACH PRODUCES 50 mA IN BRIGHT SUNLIGHT, THEN THIS ARRAY WILL PROVIDE 6 VOLTS ($12 \text{ CELLS} \times 0.5 \text{ VOLT}$) AND 100 mA.

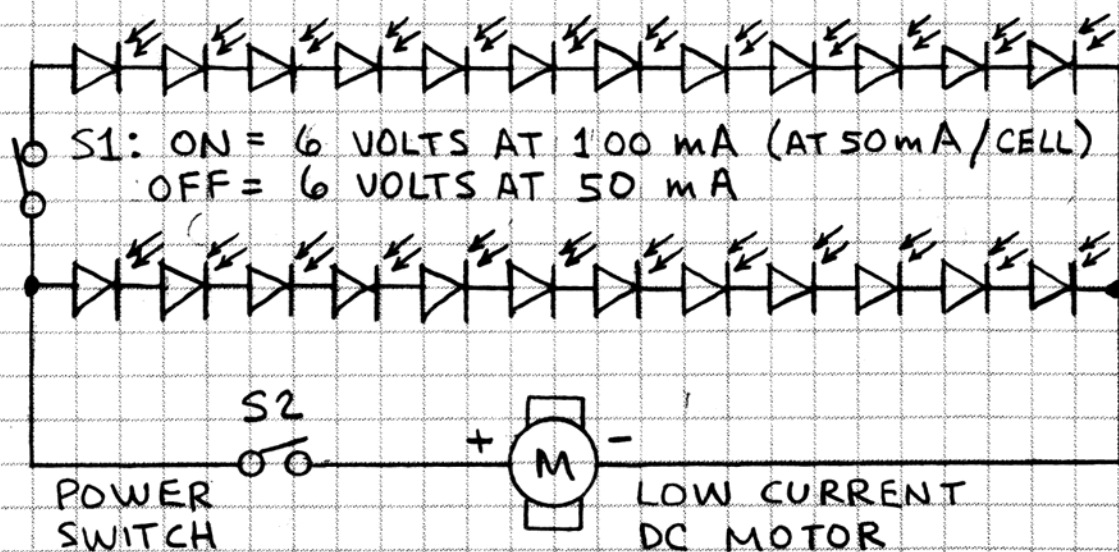

REVERSIBLE SOLAR MOTOR

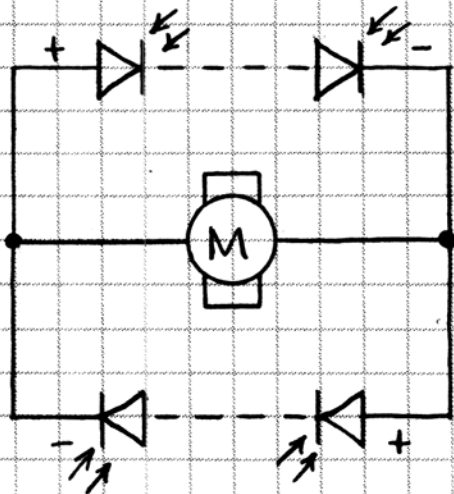A REVERSIBLE SOLAR POWERED MOTOR HAS APPLICATIONS IN ROBOTICS AND TRACKING THE SUN. THE ROTATION OF THE MOTOR BELOW IS CONTROLLED BY WHICH OF TWO SOLAR ARRAYS IS ILLUMINATED. WHEN BOTH ARRAYS ARE EQUALLY ILLUMINATED, THE MOTOR DOES NOT ROTATE.




IF ILLUMINATING THIS ARRAY CAUSES THE MOTOR TO ROTATE CLOCKWISE...

...ILLUMINATING THIS ARRAY CAUSES THE MOTOR TO ROTATE COUNTER CLOCKWISE.

SOLAR MOTOR WITH BATTERY BACKUP

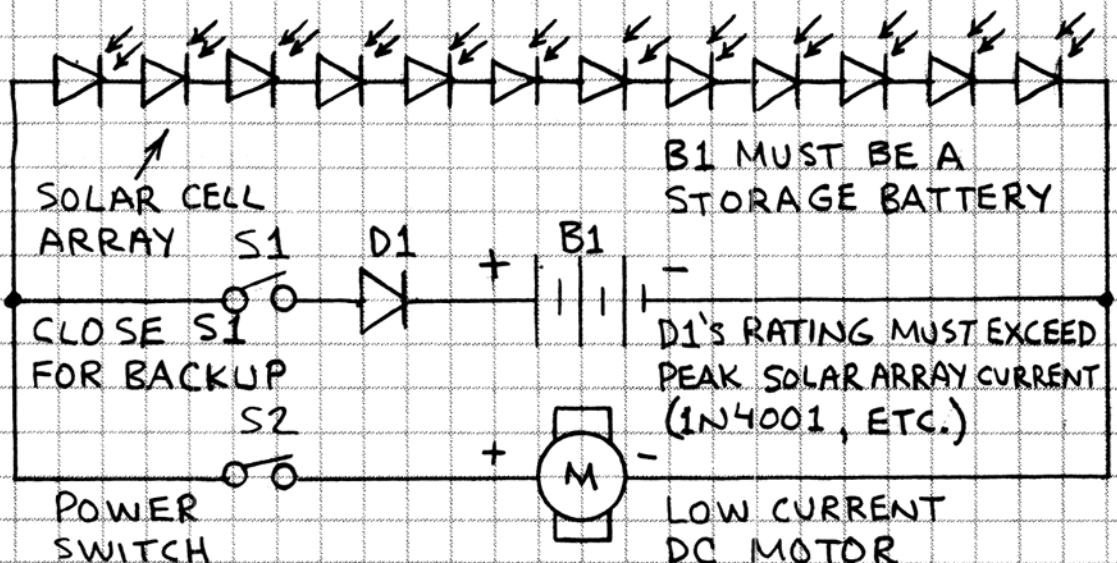
EVEN A BRIEF INTERRUPTION OF DIRECT SUNLIGHT WILL SLOW OR EVEN STOP A SOLAR POWERED MOTOR. A STORAGE BATTERY CONNECTED ACROSS THE MOTOR'S SOLAR CELL ARRAY WILL PROVIDE BACKUP POWER.



SOLAR ACTUATED MOTORS


SOLAR CELLS HAVE MANY APPLICATIONS IN ROBOTICS AND CONTROL. THE CIRCUITS SHOWN HERE SWITCH SMALL DC MOTORS ON OR OFF WITH SUNLIGHT. SOME ARE SO SENSITIVE THEY CAN BE TRIGGERED WITH A SMALL FLASHLIGHT OR LASER POINTER.

POWER FET ACTUATOR (1)

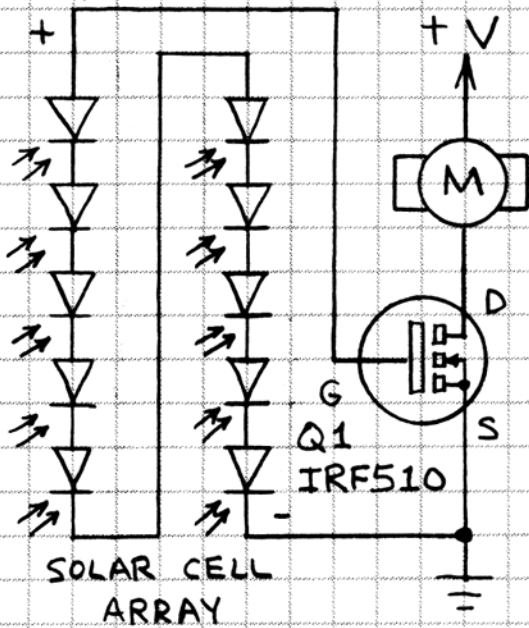

THIS CIRCUIT WILL DRIVE A SMALL DC MOTOR WHEN THE IRF510 POWER MOSFET IS SWITCHED ON WITH ABOUT 4 VOLTS FROM A SOLAR CELL ARRAY. THE IRF510 CAN DRIVE A MOTOR THAT CONSUMES UP TO 2 AMPS. +V SHOULD NOT EXCEED THE MOTOR'S RATING.


TRANSISTOR ACTUATOR

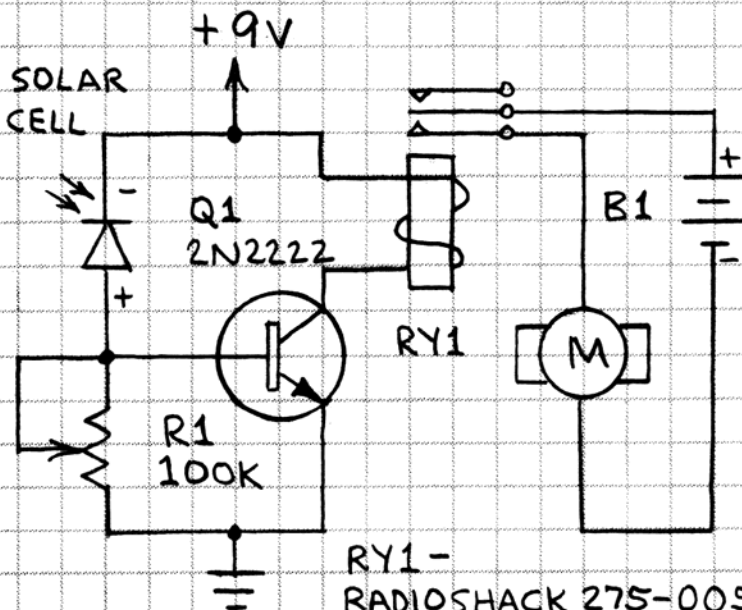

THIS CIRCUIT USES A REVERSE BIASED SOLAR CELL TO SENSE LIGHT. R1 CONTROLS THE SENSITIVITY. USE CIRCUIT TO ACTUATE SMALL DC MOTOR (1 1/2 TO 6 VOLTS).


RY1 -
RADIO SHACK 275-005 OR SIMILAR.

POWER FET ACTUATOR (2)

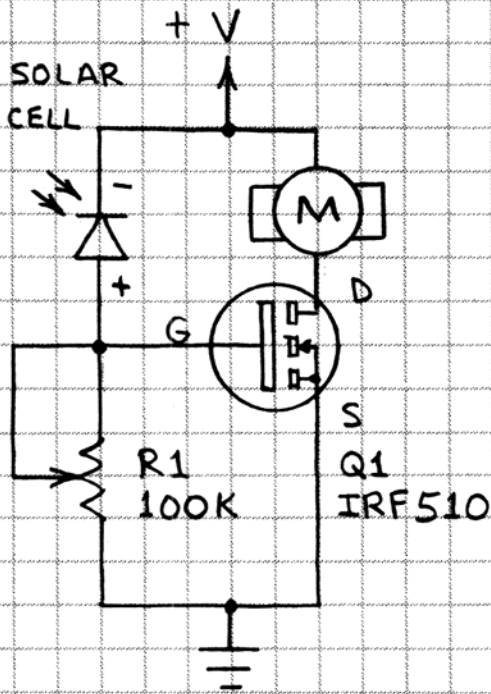

THIS CIRCUIT WILL DRIVE A SMALL DC MOTOR WHEN THE IRF510 POWER MOSFET IS SWITCHED ON BY THE VOLTAGE DIVIDER FORMED BY THE SOLAR CELL AND R1. ADJUST R1 TO CONTROL SENSITIVITY. THE IRF510 WILL DRIVE A MOTOR THAT CONSUMES UP TO 2 AMPERES. +V SHOULD NOT EXCEED THE MOTOR'S RATING. USE SUNLIGHT, FLASHLIGHT OR LASER POINTER.

OP AMP - POWER FET ACTUATOR

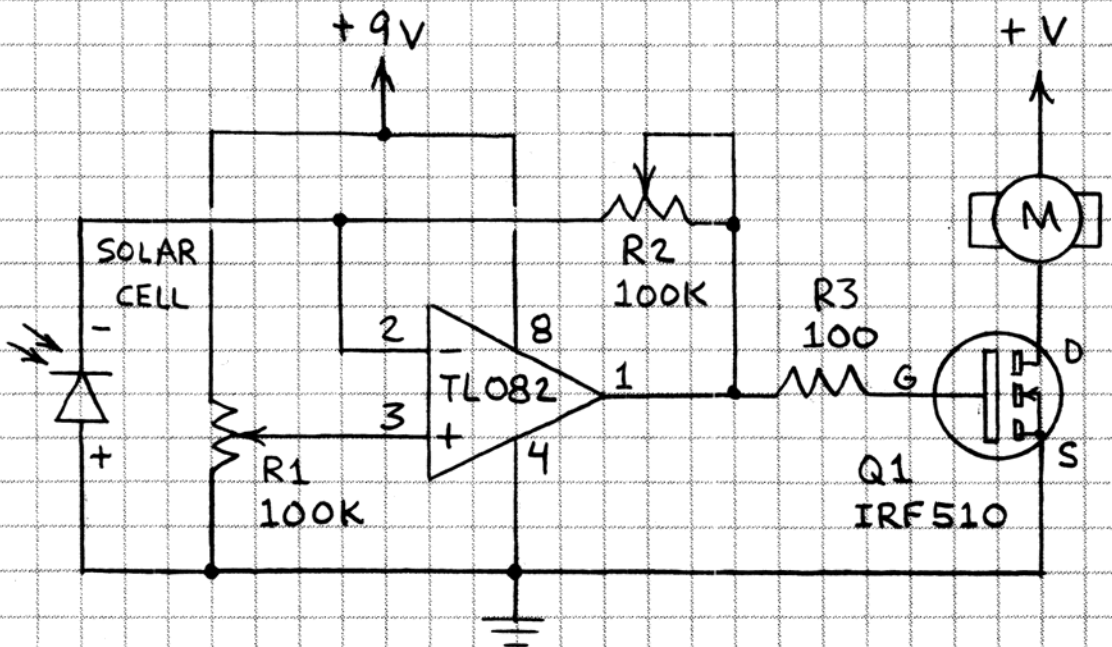


THIS CIRCUIT ALSO SWITCHES A SMALL DC MOTOR WITH AN IRF510 POWER MOSFET. ADDITIONAL FLEXIBILITY IS PROVIDED BY THE TL082 OP AMP. R1 CONTROLS THE SWITCHING THRESHOLD AND R2 CONTROLS THE GAIN. +V SHOULD NOT EXCEED THE MOTOR'S RATING.

SOLAR CELL LIGHT METERS


THE PHOTOCURRENT FROM A SILICON SOLAR CELL IS LINEAR WITH RESPECT TO LIGHT INTENSITY. THIS MEANS SOLAR CELLS MAKE EXCELLENT SENSORS FOR LIGHT METERS. THE APPLICATIONS SHOWN BELOW ARE FOR LIGHT METERS MADE FROM A SOLAR CELL AND A RADIOSHACK MULTITESTER.

LIGHT METER (VOLTAGE TYPE)

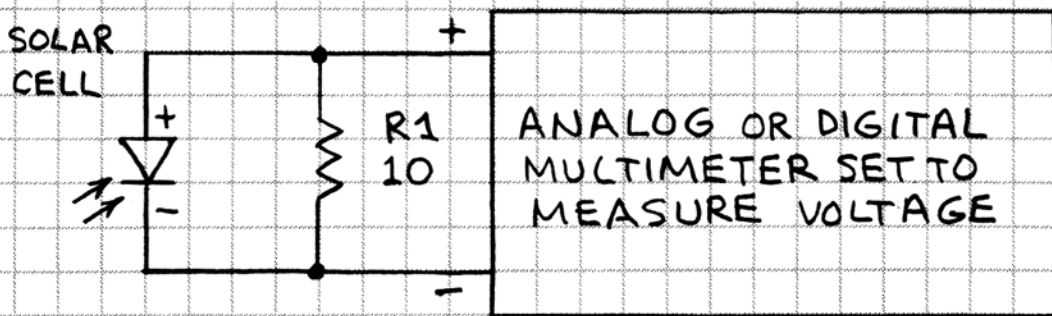


THE VOLTAGE PRODUCED BY A SOLAR CELL IS NOT LINEAR WITH RESPECT TO LIGHT INTENSITY. THIS ARRANGEMENT MEASURES THE PHOTOCURRENT (I_p) FROM A SOLAR CELL, WHICH IS LINEAR. FROM OHM'S LAW, THE CURRENT THROUGH A RESISTOR IS V/R . IF R_1 IS 10 OHMS AND THE VOLTAGE ACROSS R_1 IS 0.42 VOLT, THEN $I_p = 0.42 / 10$ OR 0.042 AMPERE (42 mA).

LIGHT METER (CURRENT TYPE)

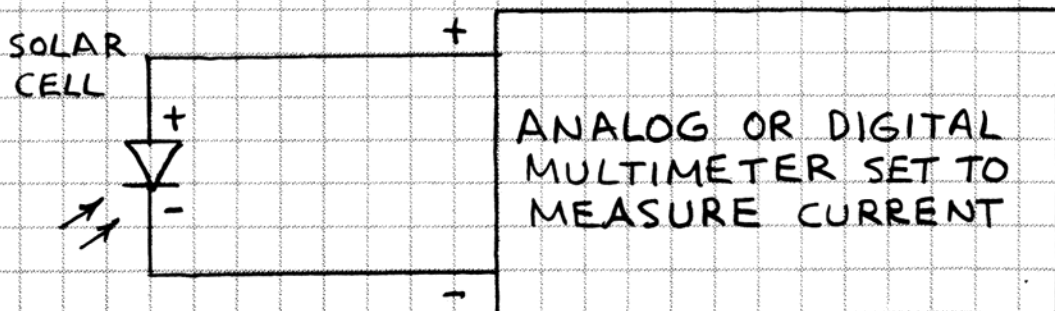

THIS ARRANGEMENT DIRECTLY MEASURES SOLAR CELL PHOTOCURRENT.

SOLAR CELL RADIOMETER

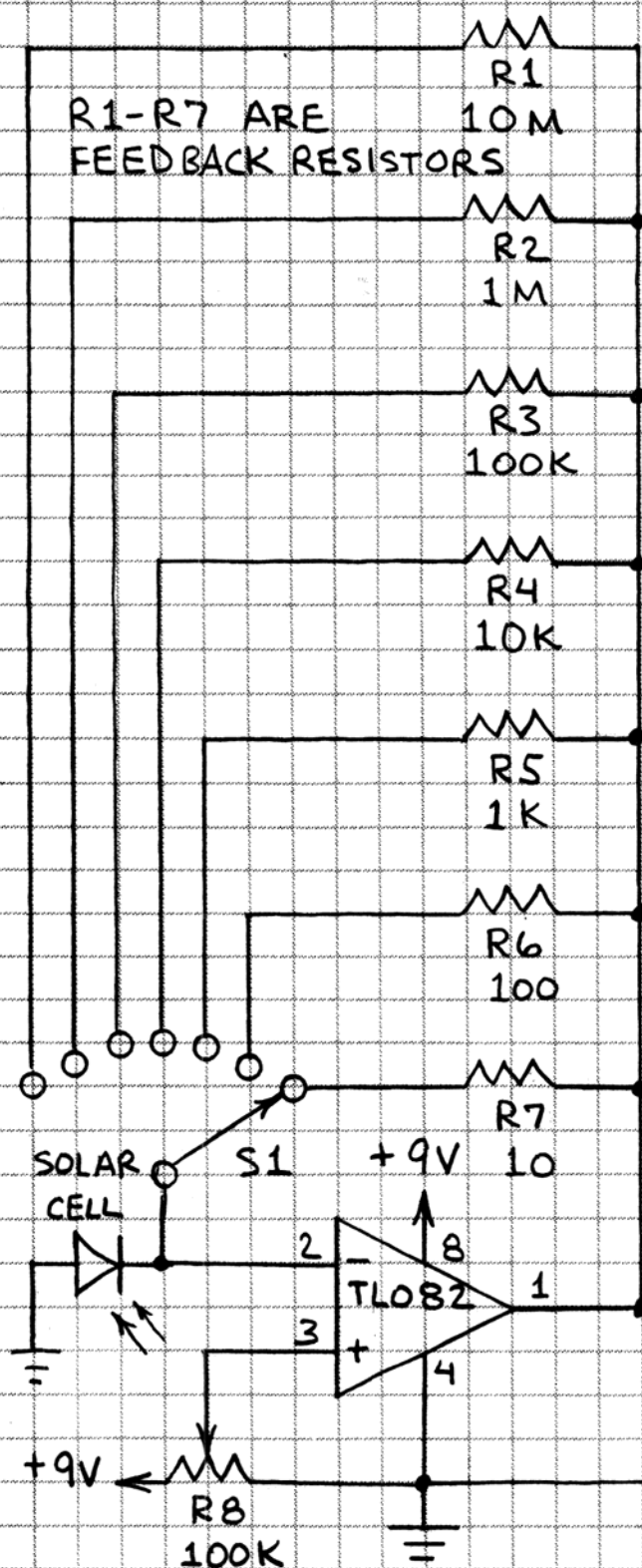


THIS RADIOMETER MEASURES A VERY WIDE RANGE OF LIGHT LEVELS. FOR BEST RESULTS, INSTALL CIRCUIT AND SOLAR CELL IN AN ENCLOSURE. KEEPS LEADS TO BATTERY AND R1-R7 SHORT TO AVOID OSCILLATION.

IN USE, SET S1 (MULTI-POSITION ROTARY SWITCH, RADIOSHACK 275-1385) TO LOWEST GAIN SETTING (10). WITH SOLAR CELL DARK, ADJUST R8 UNTIL METER INDICATES LOWEST VOLTAGE. ALLOW LIGHT TO ILLUMINATE SOLAR CELL AND ADJUST S1 TO THE MOST APPROPRIATE GAIN.

THE GAIN OF THE RADIOMETER EQUALS THE FEEDBACK RESISTANCE (R1-R7). THUS WHEN R4 IS SELECTED, THE RADIOMETER MULTIPLIES THE SOLAR CELL PHOTOCURRENT 10,000 TIMES.

SUNLIGHT ACTUATED RELAY

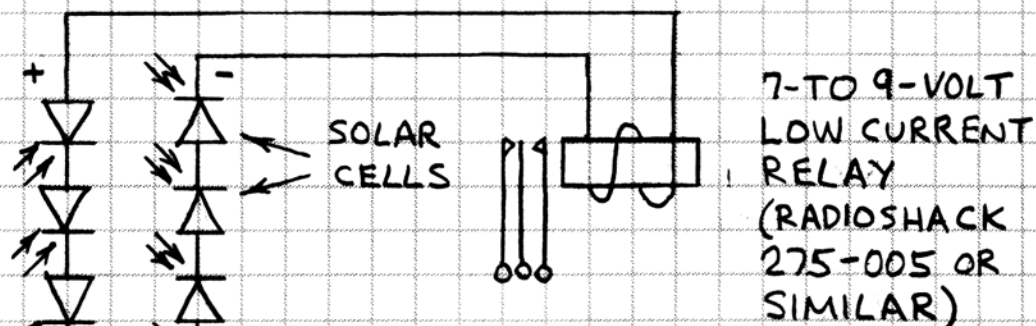A SERIES ARRANGEMENT OF SILICON SOLAR CELLS WILL ACTIVATE A RELAY. THE SOLAR CELL ARRAY MUST PROVIDE SUFFICIENT VOLTAGE AND CURRENT TO OPERATE THE RELAY. THE ARRAY SHOWN HERE WILL PULL IN A LOW CURRENT RELAY WITH A 7-TO 9-VOLT COIL.




EXAMPLE: A 7-TO 9-VOLT RELAY REQUIRES FROM 14 TO 18 CELLS. USE INDIVIDUAL CELLS OR CONNECT APPROPRIATE NUMBER OF SOLAR ARRAYS IN SERIES.

IN TESTS OF PROTOTYPE CIRCUIT, THE RELAY PULLED IN EVEN WHEN THE ARRAY WAS TILTED SOMEWHAT AWAY FROM SUN.

SENSITIVITY ADJUSTMENTS:




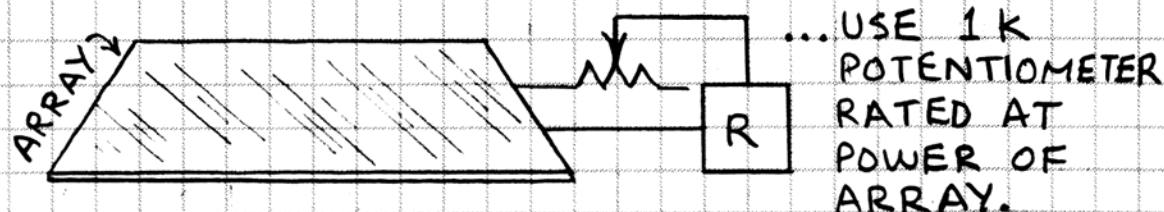BLOCK PART OF THE ARRAY WITH AN OPAQUE COVER TO REDUCE SENSITIVITY, OR...



LIGHT ACTUATED RELAY

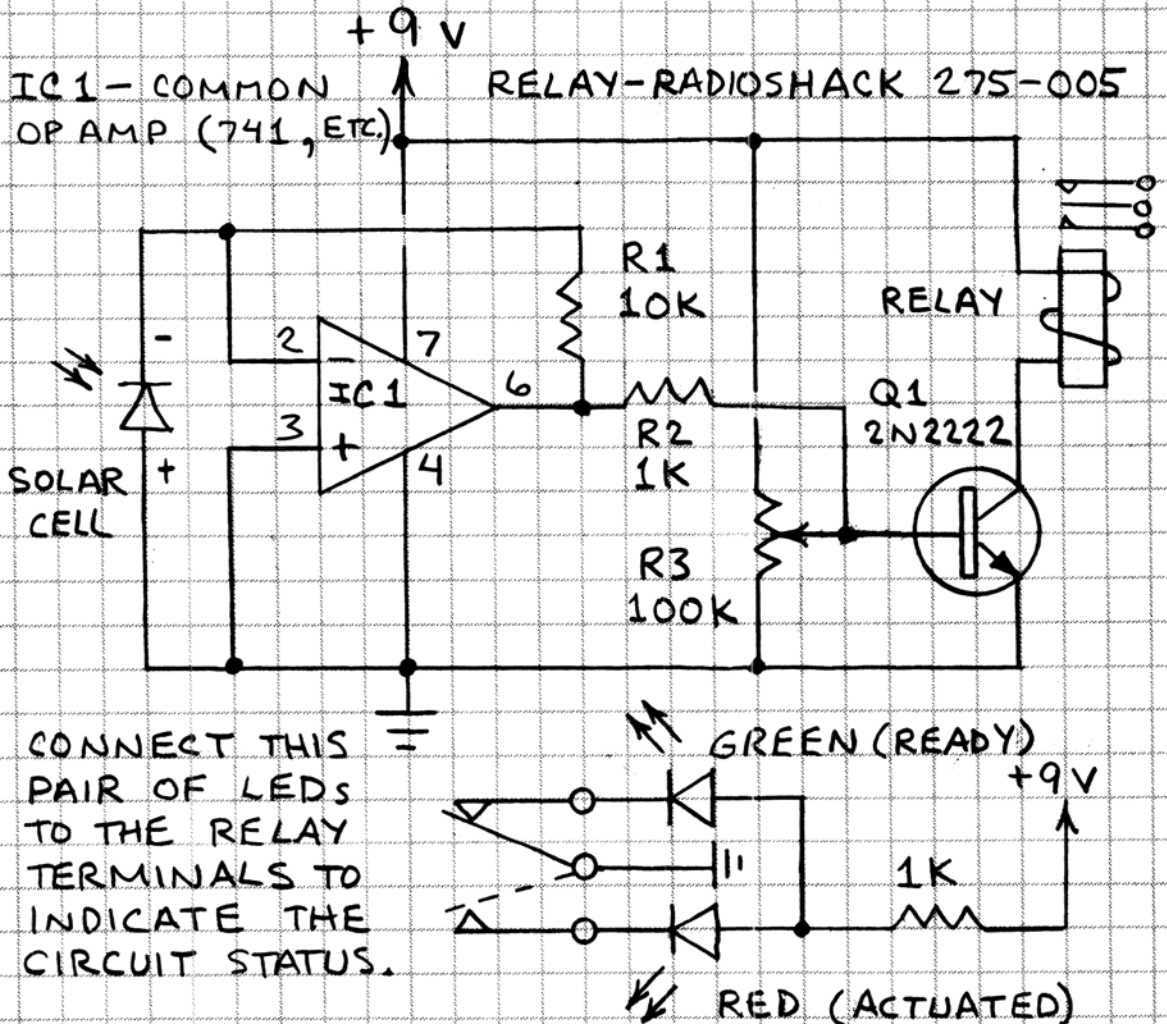A SOLAR CELL GENERATES A PHOTOCURRENT WHEN ILLUMINATED. THE CIRCUIT SHOWN HERE AMPLIFIES THE CURRENT FROM A SINGLE SOLAR CELL AND DRIVES A RELAY. THIS CIRCUIT WILL WORK WITH A VERY SMALL SOLAR CELL AND WILL RESPOND TO VERY LOW LEVELS OF LIGHT.




WITH ROOM LIGHTS SUBDUED, ADJUST R3 UNTIL THE RED LED JUST STOPS GLOWING AND THE GREEN LED GLOWS. LIGHT FROM A FLASHLIGHT WILL TRIGGER THE CIRCUIT AND THE RED LED WILL GLOW. THE CIRCUIT WILL RESPOND TO AN LED, MATCH, CANDLE, DAYLIGHT AND A LASER POINTER. SINCE THE CIRCUIT RESPONDS TO MANY LIGHT SOURCES, NEVER USE IT TO CONTROL HAZARDOUS THINGS (MACHINERY, ETC.).


BREAK-BEAM DETECTION SYSTEMS

BREAK-BEAM DETECTION SYSTEMS DETECT EVERYTHING FROM ITEMS ON A CONVEYOR BELT AND SMOKE TO CUSTOMERS IN STORES AND BURGLARS. WHEN A LIGHT BEAM IS INTERRUPTED, THE SYSTEM SWITCHES AN ALARM, COUNTER OR LIGHT. HERE ARE SOME COMMON BREAK-BEAM CONFIGURATIONS:


IN-LINE MODE

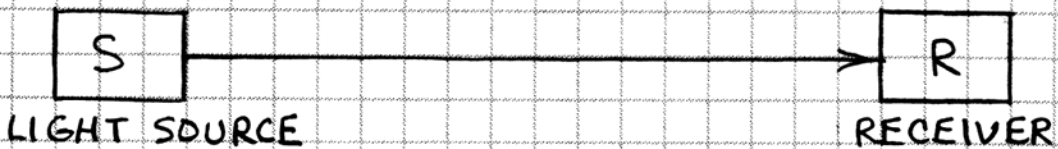

REFLECTION MODE

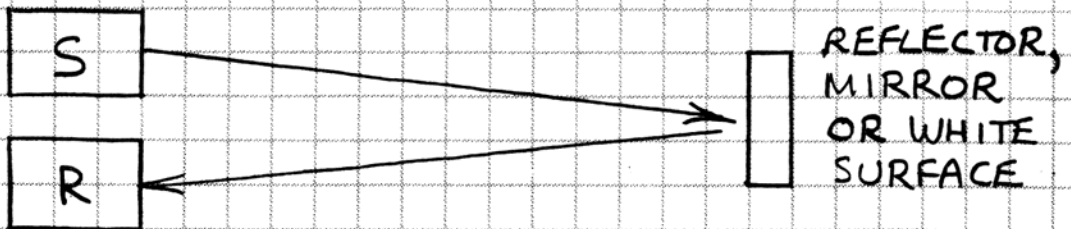

PROXIMITY MODE

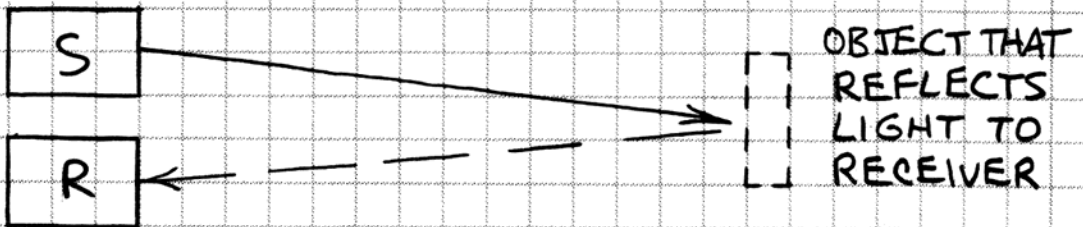


KINDS OF BREAK-BEAM SYSTEMS

STEADY STATE — THE LIGHT SOURCE IS A LAMP, LED OR SUNLIGHT. WHILE VERY SIMPLE, A STEADY-STATE SYSTEM CAN BE INTERFERED WITH BY AN OUTSIDE SOURCE.

PULSED — THE LIGHT IS A PULSED LED. A CAPACITOR BETWEEN THE SOLAR CELL AND THE RECEIVER BLOCKS INTERFERENCE FROM NON-PULSED OUTSIDE LIGHT SOURCES.

STEADY-STATE BREAK-BEAM SYSTEM

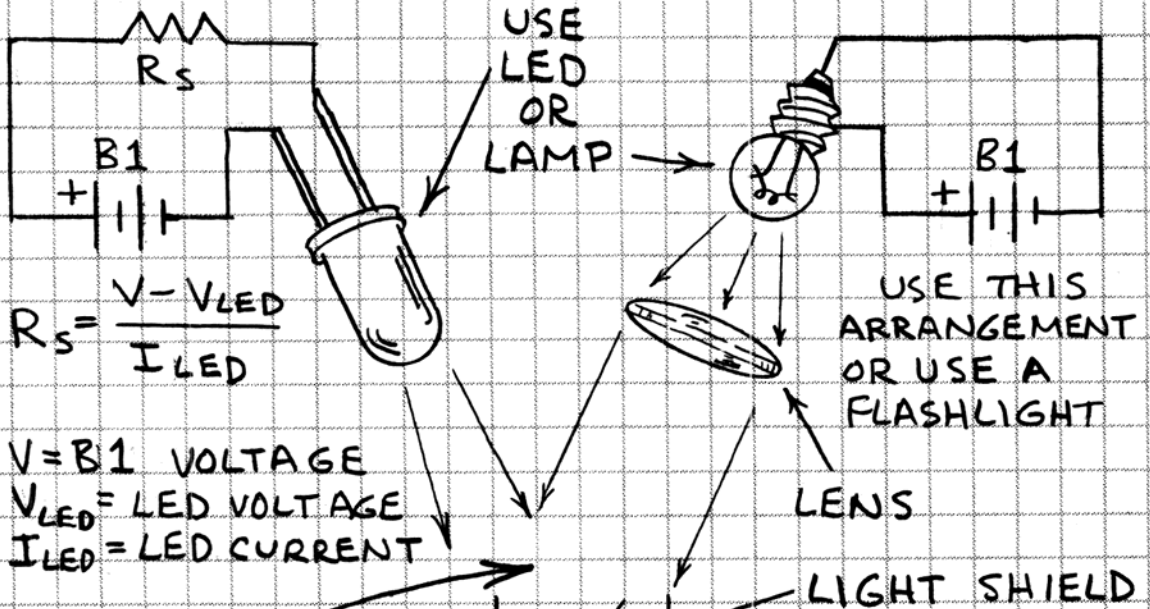
THIS SYSTEM PULLS IN A RELAY AND LIGHTS AN LED WHEN STEADY LIGHT ILLUMINATES THE SOLAR CELL.



WHEN THIS SPACE IS OPEN, THE CIRCUIT'S RELAY IS PULLED IN AND THE LED GLOWS. ADJUST R1 TO CONTROL SENSITIVITY.

THE RELAY CAN CONTROL A MOTOR, LAMP, ETC.

R2 CONTROLS OPAMP GAIN.

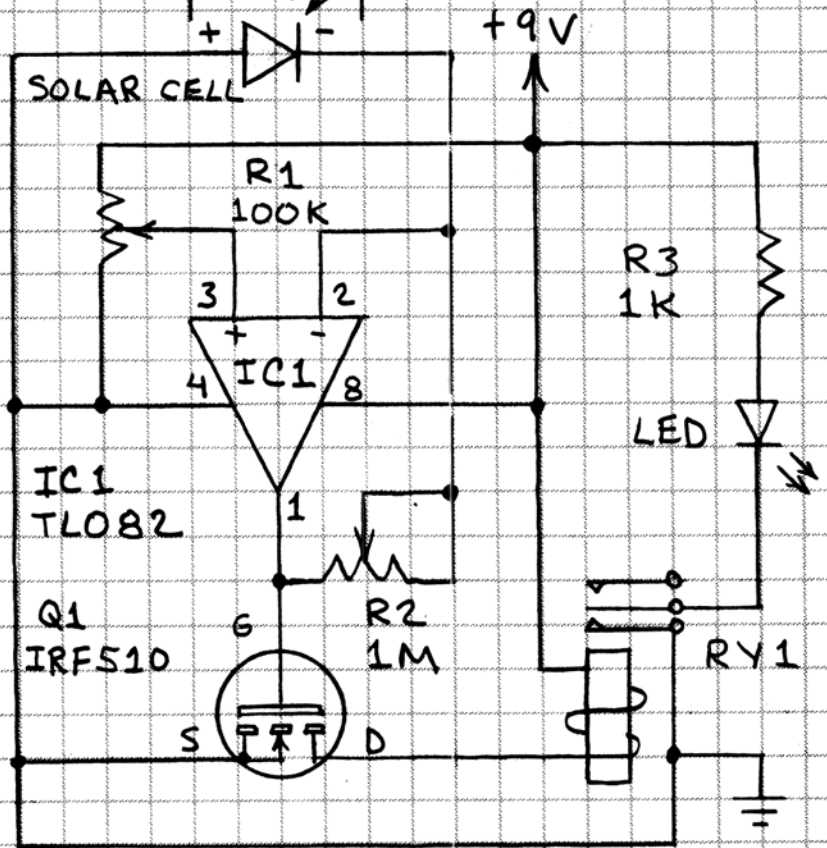


RY1 IS RADIOSHACK 275-005 OR SIMILAR LOW-CURRENT RELAY.

PULSED BREAK-BEAM SYSTEM

A PULSED BREAK-BEAM SYSTEM IS GENERALLY IMMUNE TO STEADY-STATE LIGHT SOURCES. THIS IS VERY IMPORTANT WHEN THE SYSTEM IS OPERATED IN THE PRESENCE OF ROOM LIGHTS OR WEAK SUNLIGHT. A SOLAR CELL RECEIVER FOR A PULSED BREAK-BEAM SYSTEM IS SHOWN ON THE FACING PAGE. SHOWN BELOW IS A 555 PULSED LED TRANSMITTER THAT WILL WORK WITH THIS RECEIVER.

PULSED BREAK-BEAM TRANSMITTER

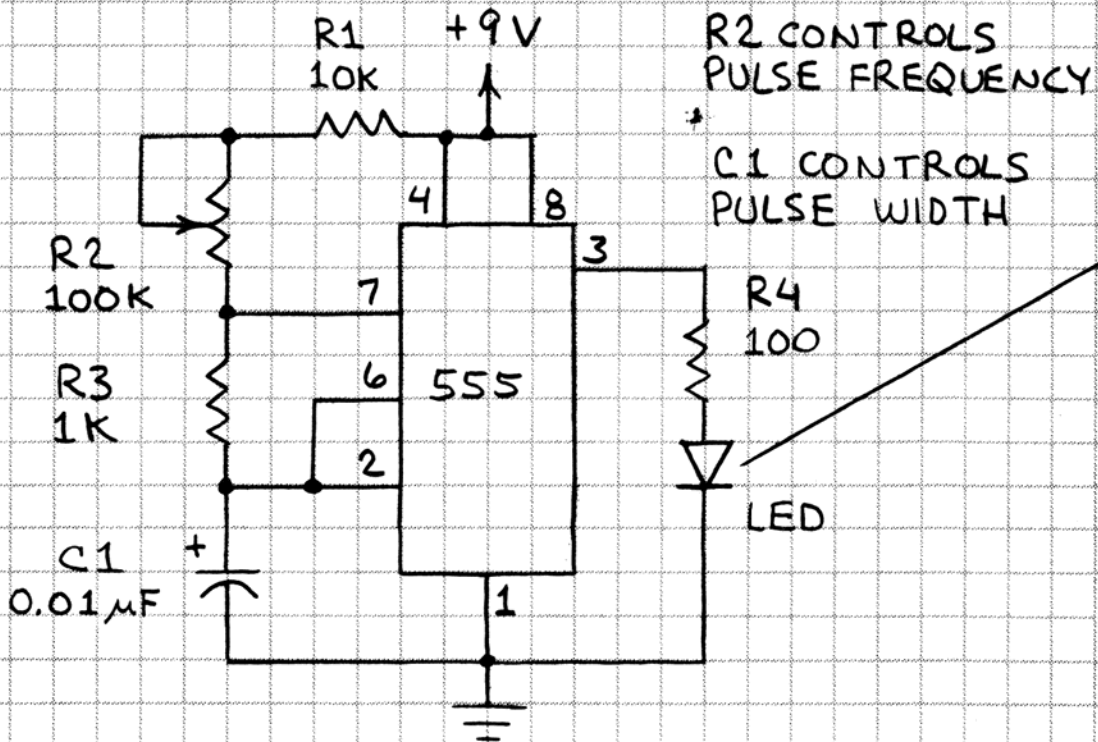

FOR BEST RESULTS:

1. USE AN INFRARED OR SUPER BRIGHT RED LED FOR MAXIMUM RANGE.
2. POWER THE TRANSMITTER AND RECEIVER FROM SEPARATE BATTERIES.
3. BE SURE THE BEAM FROM THE LED ILLUMINATES THE SOLAR CELL.

PULSED BREAK-BEAM RECEIVER


C1 BLOCKS THE SIGNAL FROM STEADY-STATE LIGHT SOURCES.

R1 CONTROLS THE GAIN OF OP AMP TL082. REDUCE R1 TO REDUCE THE GAIN.

SOLAR CELL

THE LED IS USED TO TEST CIRCUIT OPERATION.

S1 IS AN SPDT SWITCH.

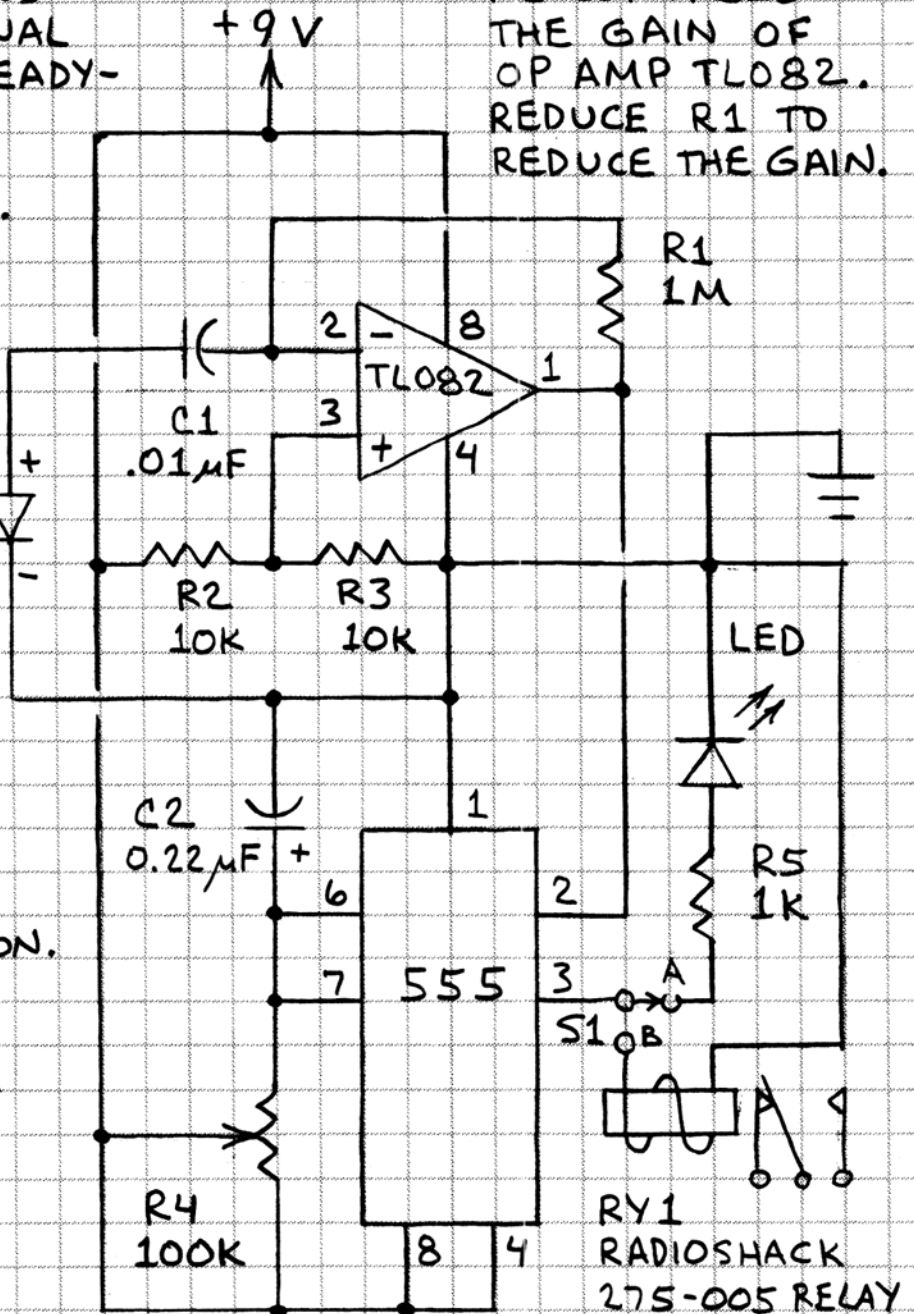


TO OPERATE, SWITCH S1 TO POSITION A. ADJUST R2 OF THE TRANSMITTER TO ITS MID-POINT. WHEN LIGHT FROM THE LED IS STRIKING THE SOLAR CELL, ADJUST R4 OF THE RECEIVER UNTIL THE RECEIVER'S LED SWITCHES ON. THE LED SHOULD SWITCH OFF WHEN THE TRANSMITTER LED IS POINTED AWAY FROM THE SOLAR CELL OR ITS LIGHT IS BLOCKED. SWITCH S1 TO B TO SELECT RELAY.

SUN POWERED TONE GENERATORS

THE CIRCUITS ON THIS AND THE FACING PAGE ARE POWERED SOLELY BY SUNLIGHT OR A BRIGHT LAMP. MOST PRODUCE A TONE OR BUZZ. ONE GENERATES A SOUND THAT SOUNDS MUCH LIKE A TICKING CLOCK.


SOLAR POWERED PIEZO BUZZER

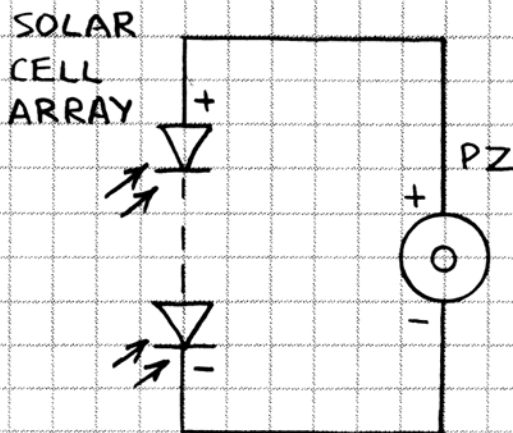

THE SOLAR ARRAY MUST PROVIDE SUFFICIENT VOLTAGE TO POWER THE PIEZO BUZZER. ANY PIEZO BUZZER CAN BE POWERED BY SUNLIGHT.


PZ IS A PIEZO BUZZER.

SOLAR POWERED DUAL-GATE OSCILLATOR

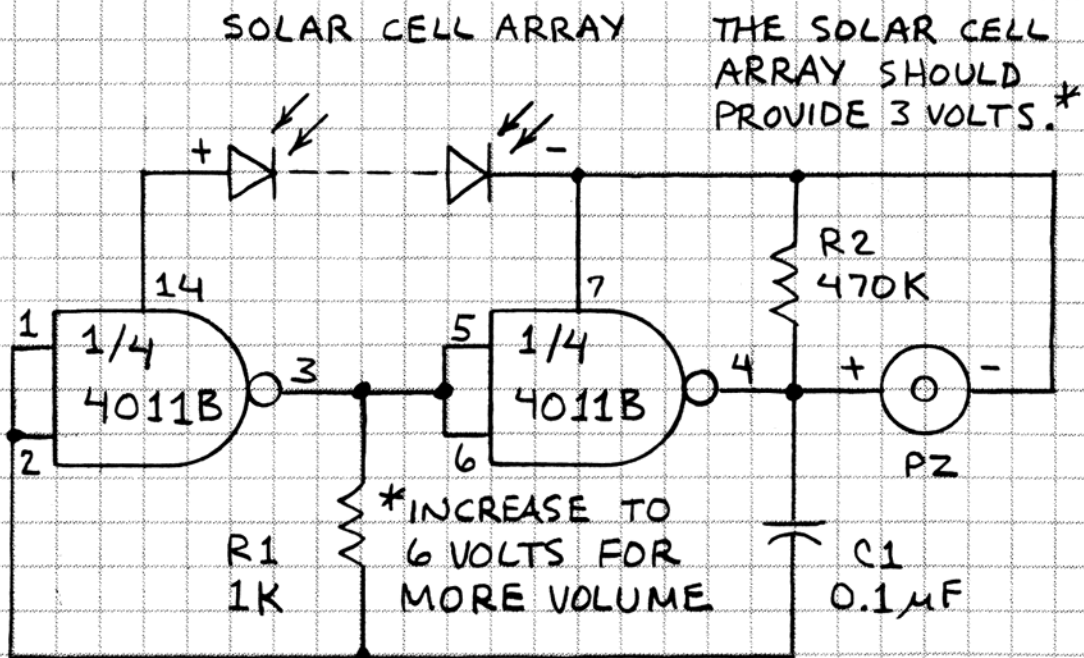


EXPERIMENT WITH VALUE OF C1 AND R1 TO CHANGE FREQUENCY.


SOLAR POWERED 555 OSCILLATOR

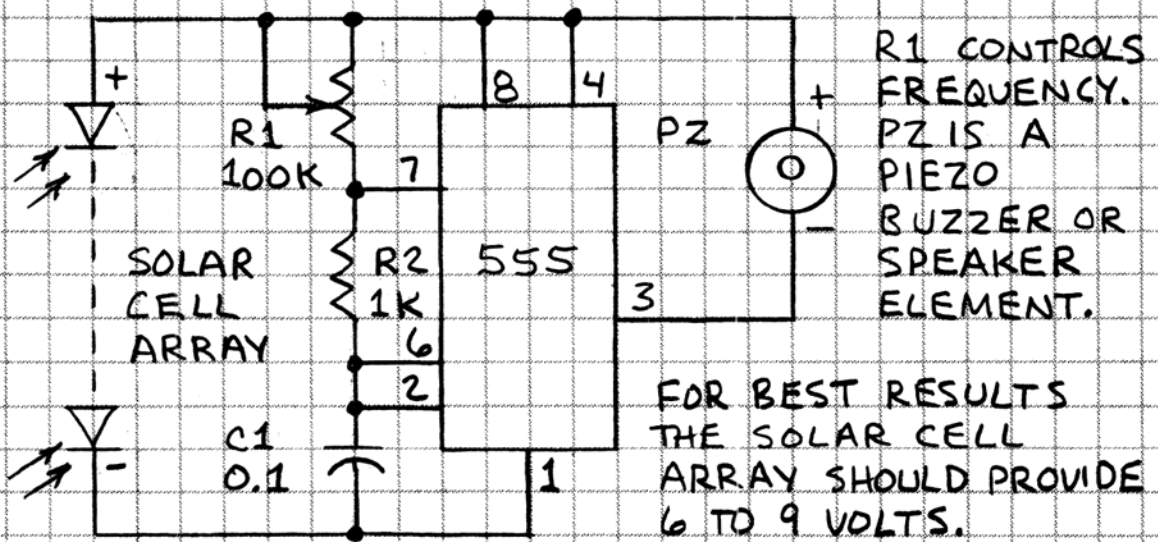

SOLAR POWERED CLICKER (1)

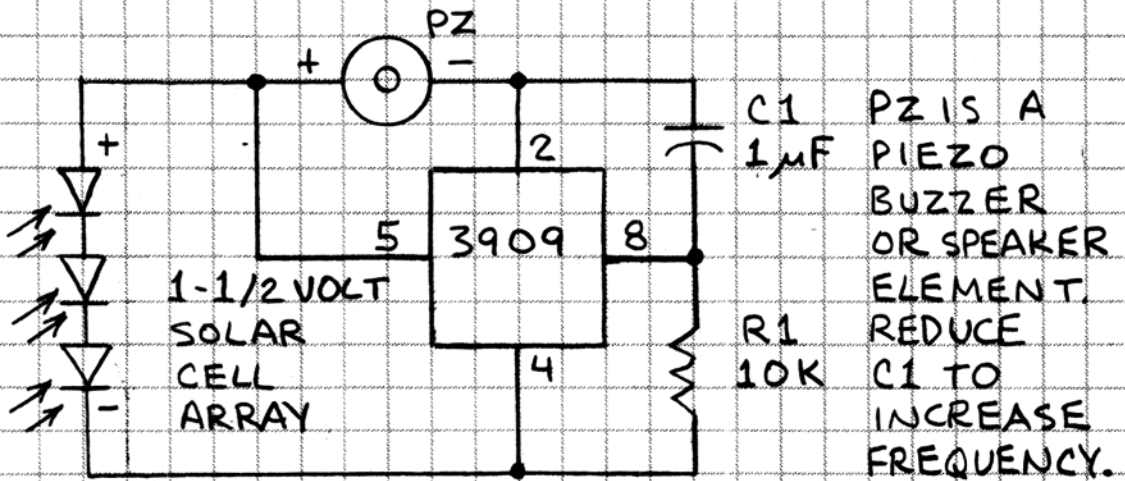

SOLAR POWERED CLICKER (2)

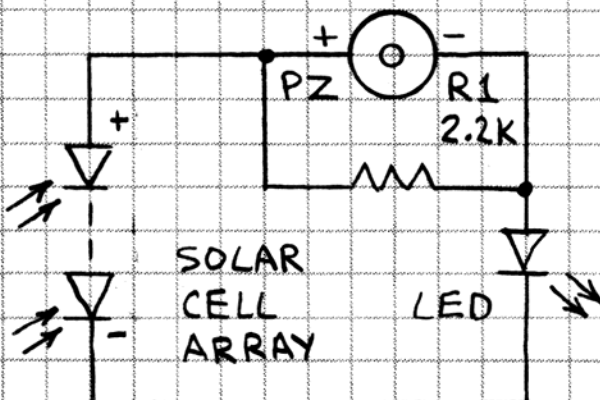


THIS CIRCUIT EMITS SOUND LIKE THAT OF A TICKING CLOCK. USE 3-VOLT SOLAR ARRAY. LED IS A BLINKING TYPE LED. OK TO REPLACE PZ WITH MAGNETIC SPEAKER.

LIGHT CONTROLLED TONE

SILICON SOLAR CELLS CAN BE USED IN MANY KINDS OF TONE GENERATORS THAT RESPOND TO DAYLIGHT OR ARTIFICIAL LIGHT.

LIGHT CONTROLLED 555 OSCILLATOR

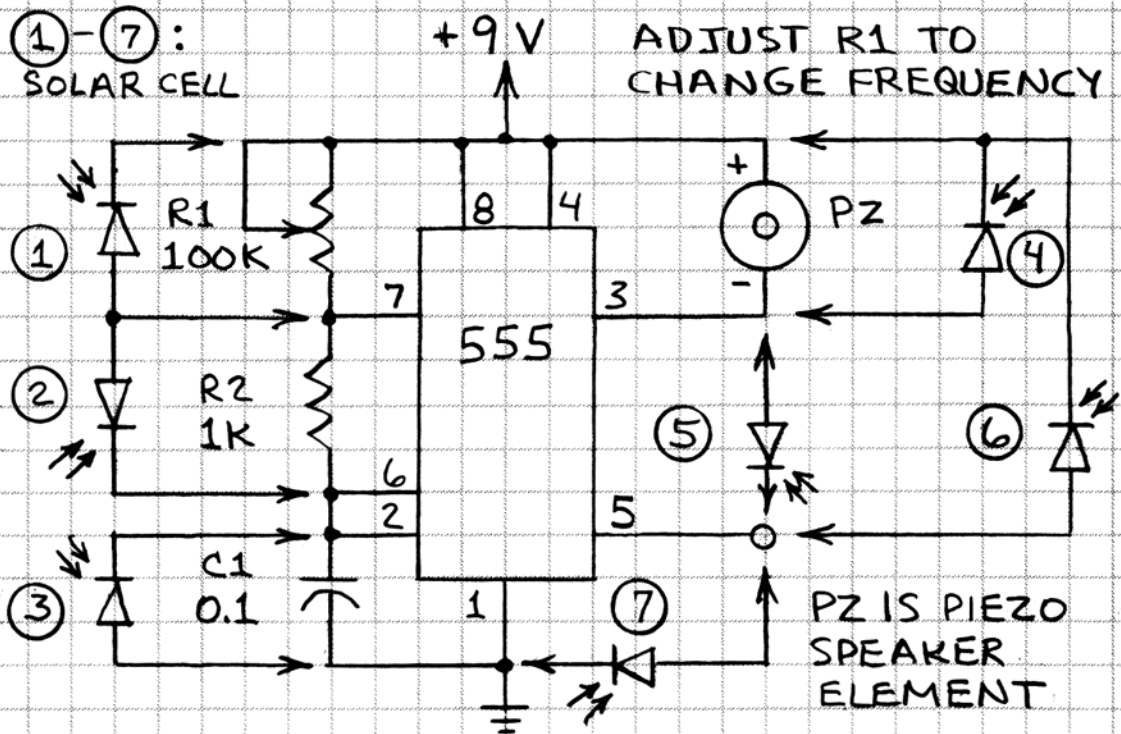THE FREQUENCY AND VOLUME OF SOUND PRODUCED BY A BASIC 555 OSCILLATOR CAN BE EASILY MODIFIED BY CONNECTING A SILICON SOLAR CELL AT VARIOUS POINTS.




- ① CONNECT SOLAR CELL HERE. INCREASING LIGHT WILL INCREASE TONE FREQUENCY.
- ② WITH CELL CONNECTED HERE, INCREASING LIGHT REDUCES VOLUME FROM PZ.
- ③ LIGHT FALLING ON CELL HERE REDUCES FREQUENCY OR CUTS OFF TONE ENTIRELY.
- ④ LIGHT STRIKING CELL HERE REDUCES VOLUME FROM PZ OR CUTS OFF TONE.
- ⑤ LIGHT FALLING ON CELL HERE CUTS OFF TONE OR CAUSES CHIRPS.
- ⑥ LIGHT STRIKING CELL HERE REDUCES THE TONE FREQUENCY.

⑦ WITH CELL HERE, INCREASING LIGHT INCREASES TONE FREQUENCY.

AN INTERESTING APPLICATION IS TO REPLACE C1 WITH A SOLAR CELL. SINCE A SOLAR CELL HAS CAPACITANCE, THE CIRCUIT WILL OSCILLATE. LIGHT AT THE CELL WILL CHANGE THE TONE FREQUENCY OR CUT IT OFF ENTIRELY. THE CELL SHOULD BE ORIENTED LIKE CELL ③.

HIGH GAIN LIGHT CONTROLLED TONE

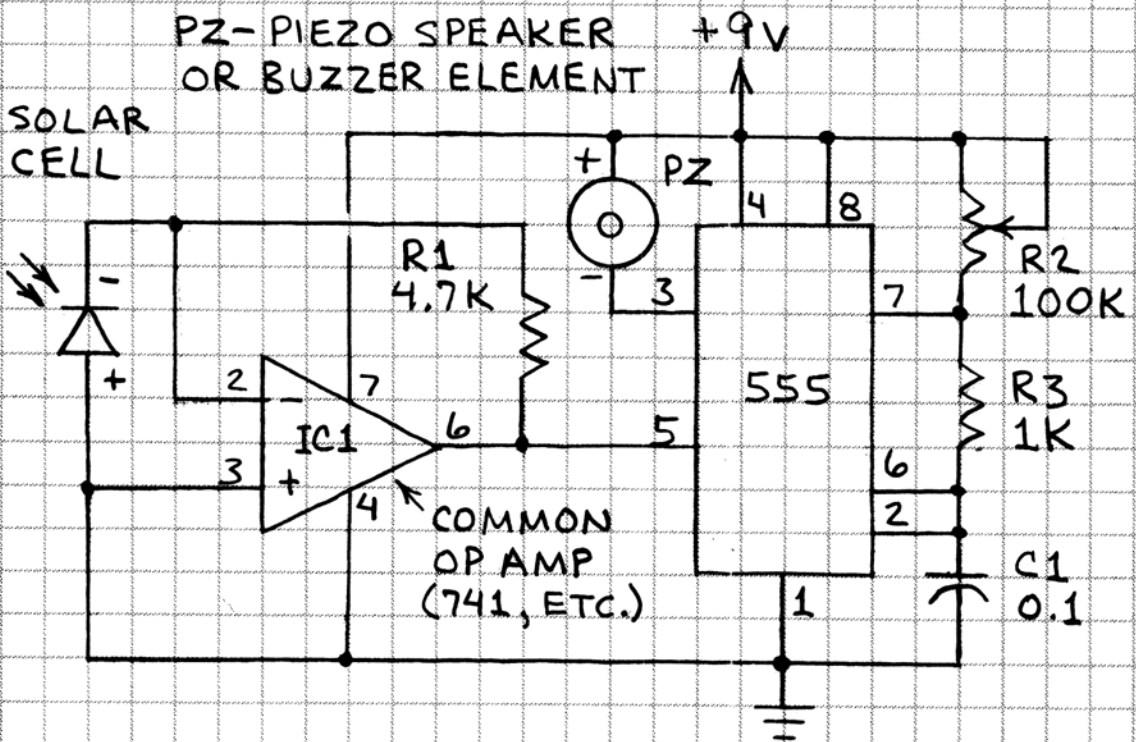


THE FREQUENCY OF THE TONE PRODUCED BY THIS CIRCUIT IS REDUCED AS THE INTENSITY OF LIGHT AT THE SOLAR CELL IS INCREASED. IN OPERATION, THE PHOTOCURRENT FROM THE SOLAR CELL IS AMPLIFIED AND CONVERTED TO A VOLTAGE BY OP AMP IC1. THIS VOLTAGE IS THEN APPLIED TO THE CONTROL INPUT OF A 555 IC CONNECTED AS AN OSCILLATOR. WHEN THE SOLAR CELL IS DARK, ADJUST R2 UNTIL THE DESIRED TONE IS PRODUCED. THEN ILLUMINATE THE SOLAR CELL. YOU CAN GET UNIQUE EFFECTS BY USING A FLASHING LIGHT.

IR REMOTE CONTROL TESTERS


NEAR-INFRARED EMITTING DIODES ARE USED IN REMOTE CONTROL TRANSMITTERS FOR TELEVISIONS, VIDEO RECORDERS AND OTHER SYSTEMS. THEY ARE ALSO USED TO TRANSMIT DATA FROM VARIOUS COMPUTERS. THE CIRCUITS SHOWN HERE VERIFY THAT NEAR-INFRARED TRANSMITTERS ARE OPERATING.

PIEZO ELEMENT TESTERS

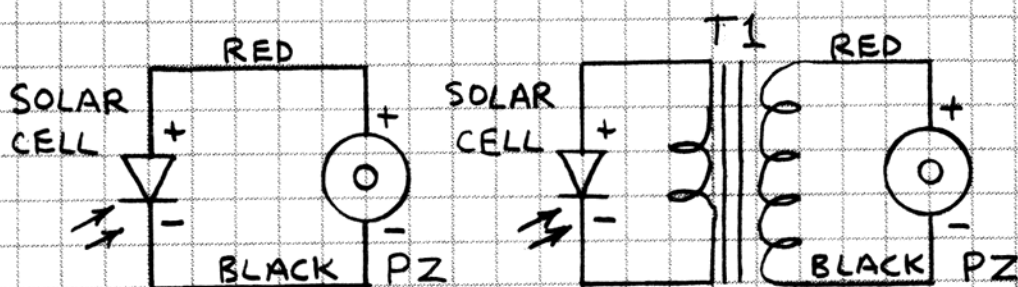

PZ IS ANY PIEZOELECTRIC SPEAKER ELEMENT OR EARPHONE. (DO NOT USE A PIEZOELECTRIC BUZZER.) T1 IN THE CIRCUIT ON THE RIGHT IS ANY MINIATURE AUDIO OUTPUT TRANSFORMER. THIS CIRCUIT PROVIDES A LOUDER SOUND THAN THE CIRCUIT ON THE LEFT. TEST THE IR REMOTE CONTROL TRANSMITTER BY POINTING IT AT THE SOLAR CELL. A TONE WILL BE HEARD IF THE UNIT IS WORKING.


MAGNETIC TRANSDUCER TESTERS

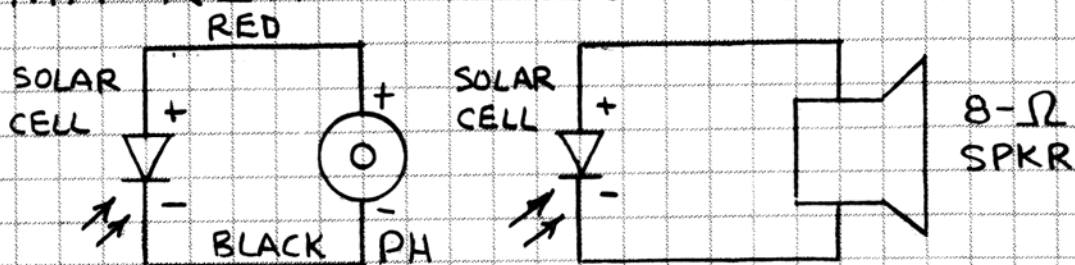

PH IS A MINIATURE MAGNETIC EAR PHONE. BOTH CIRCUITS EMIT A TONE WHEN A WORKING IR TRANSMITTER IS POINTED AT THE SOLAR CELL. USE A SOLAR ARRAY FOR MORE VOLUME.


TRANSISTOR REMOTE CONTROL TESTER

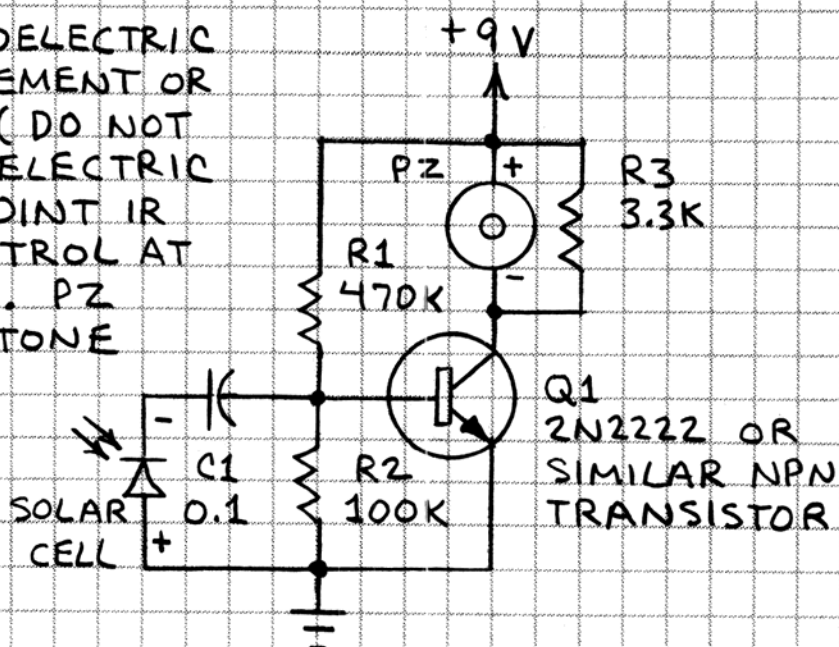PZ IS A PIEZOELECTRIC SPEAKER ELEMENT OR EARPHONE. (DO NOT USE A PIEZOELECTRIC BUZZER.) POINT IR REMOTE CONTROL AT SOLAR CELL. PZ WILL EMIT TONE IF UNIT IS WORKING.



OPAMP REMOTE CONTROL TESTER

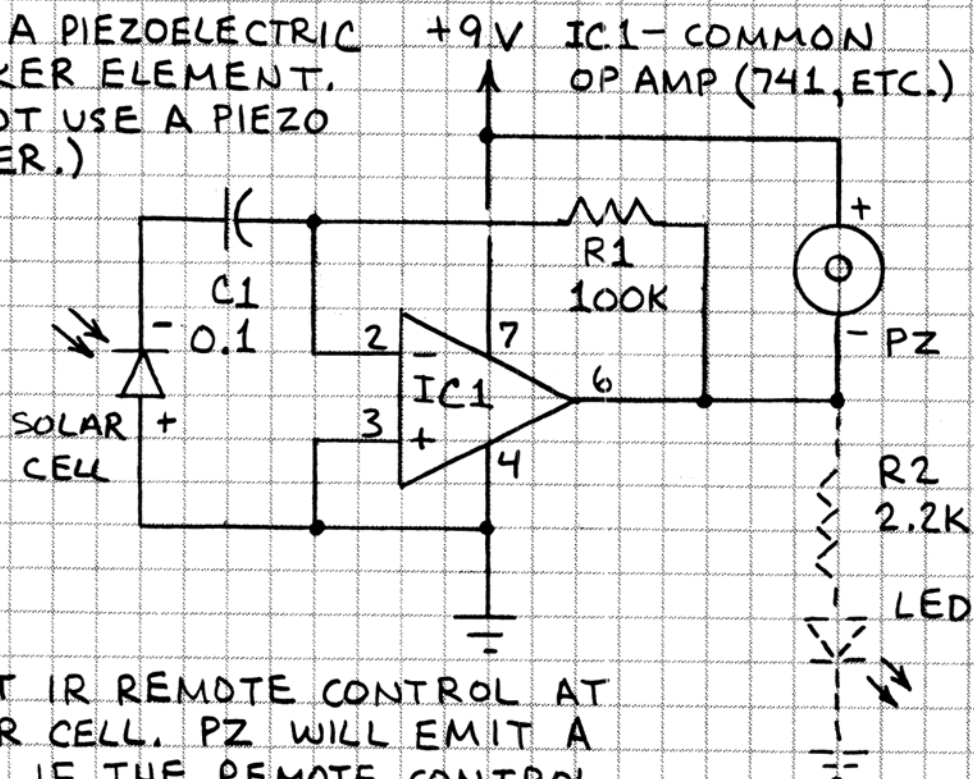PZ IS A PIEZOELECTRIC SPEAKER ELEMENT. (DO NOT USE A PIEZO BUZZER.)



POINT IR REMOTE CONTROL AT SOLAR CELL. PZ WILL EMIT A TONE IF THE REMOTE CONTROL TRANSMITTER IS WORKING.

ADD R2 AND LED TO PROVIDE A VISUAL OUTPUT. THE LED WILL FLASH WHEN THE REMOTE CONTROL IS POINTED AT SOLAR CELL.

SOLAR-POWERED NIGHT LIGHT

RADIOSHACK
SOLAR PANEL
OR PANELS
CONNECTED
TO PROVIDE
6-7 VOLTS.

OR MAKE
YOUR OWN
6-7 VOLT
SOLAR CELL
PANEL.

(12-14 CELLS) +

R1 CONTROLS
SENSITIVITY

R1
100K

SHIELD
PHOTOCELL
FROM LIGHT
EMITTED
BY THE LED

CdS
PHOTOCELL

D1
1N914

B1

B1-3 AA
NICKEL
CADMIUM
STORAGE
CELLS

R3
220Ω


R2
4.7K


Q1
2N2222


R3 LIMITS
CURRENT
THROUGH
THE LED


LED IS RED
OR GREEN
HIGH-
BRIGHTNESS
TYPE

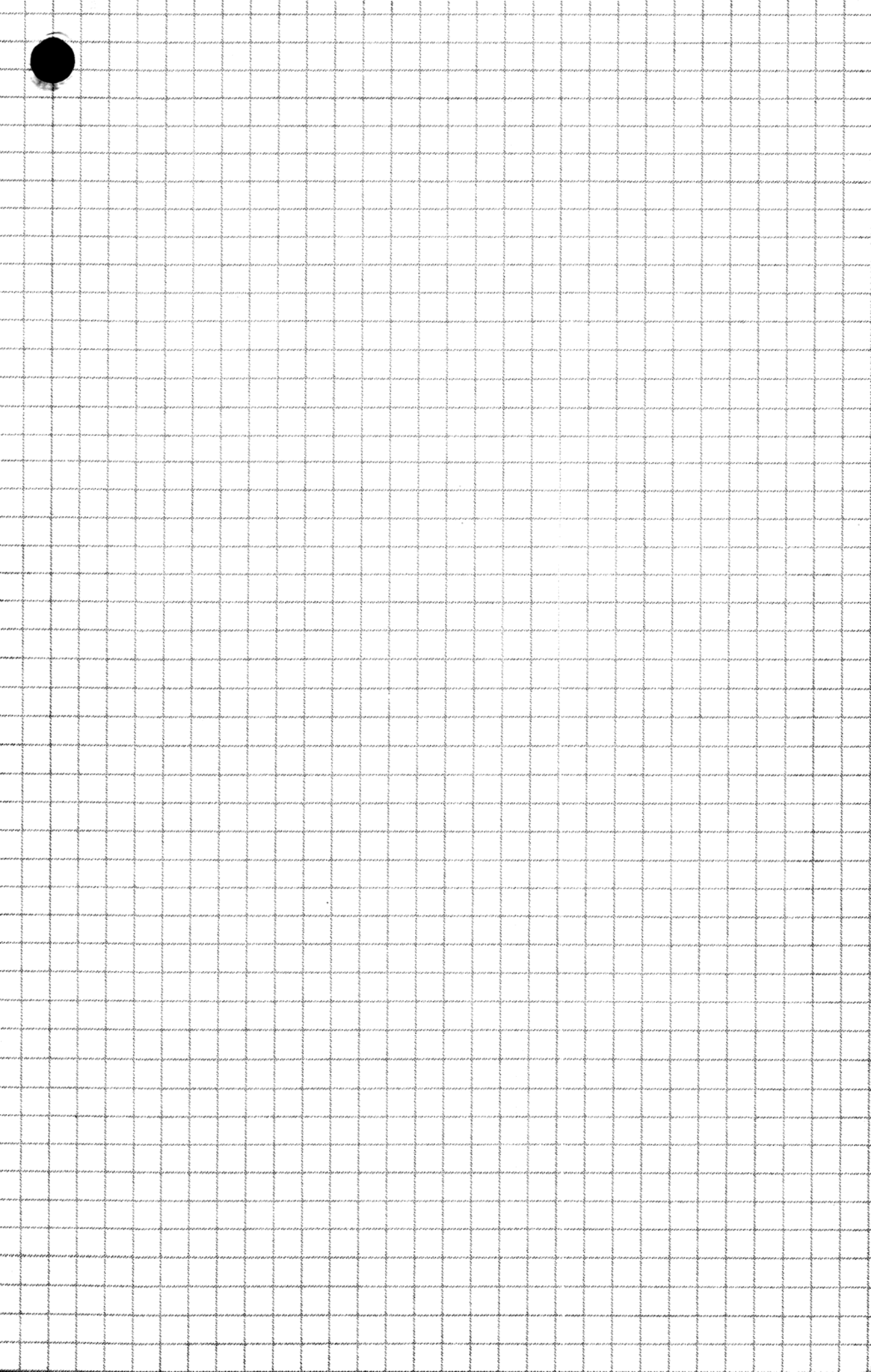DURING DAYLIGHT HOURS THE SOLAR PANEL
RECHARGES B1. AT NIGHT Q1 SWITCHES
ON AND APPLIES CURRENT TO THE LED.




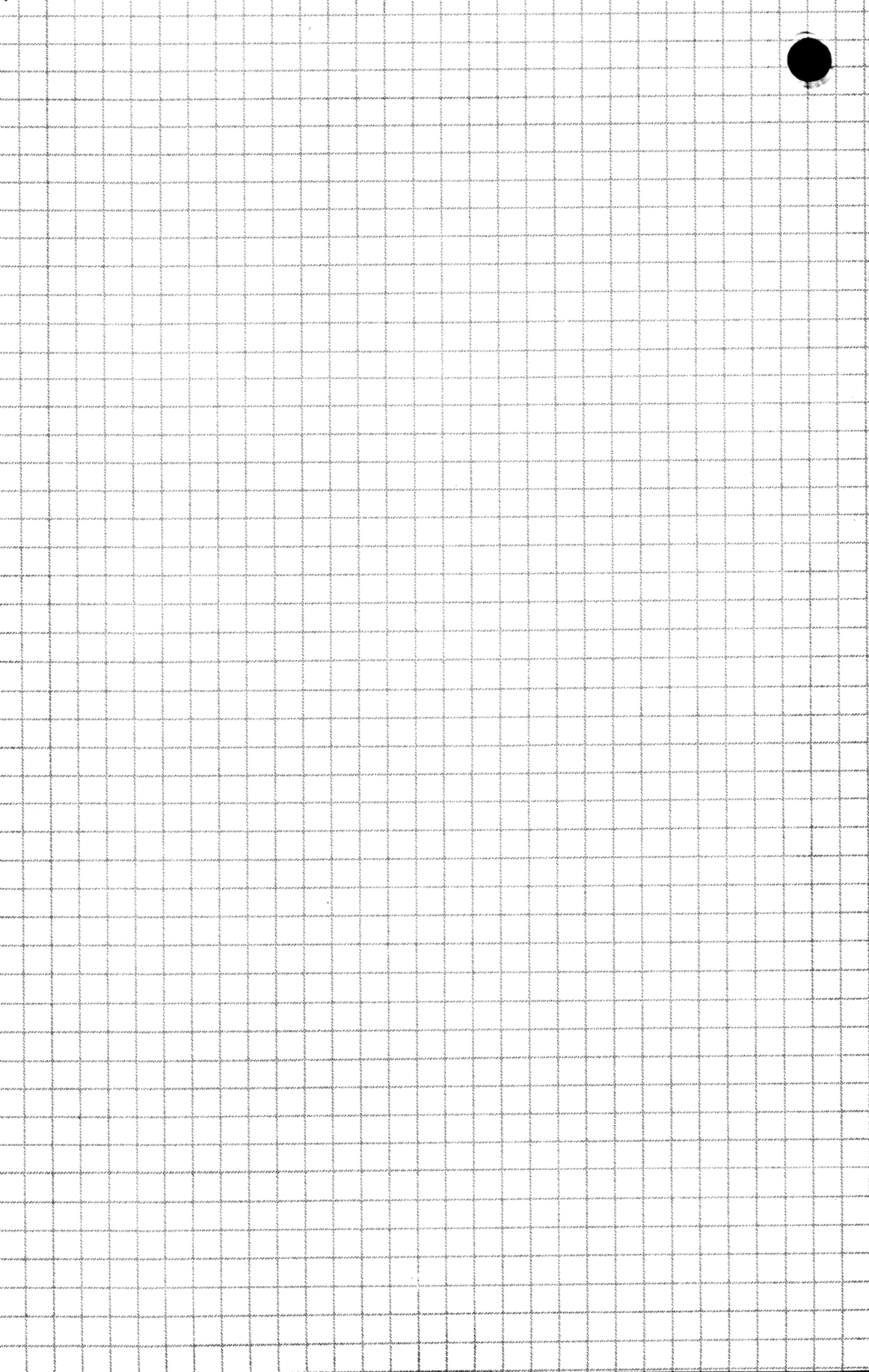

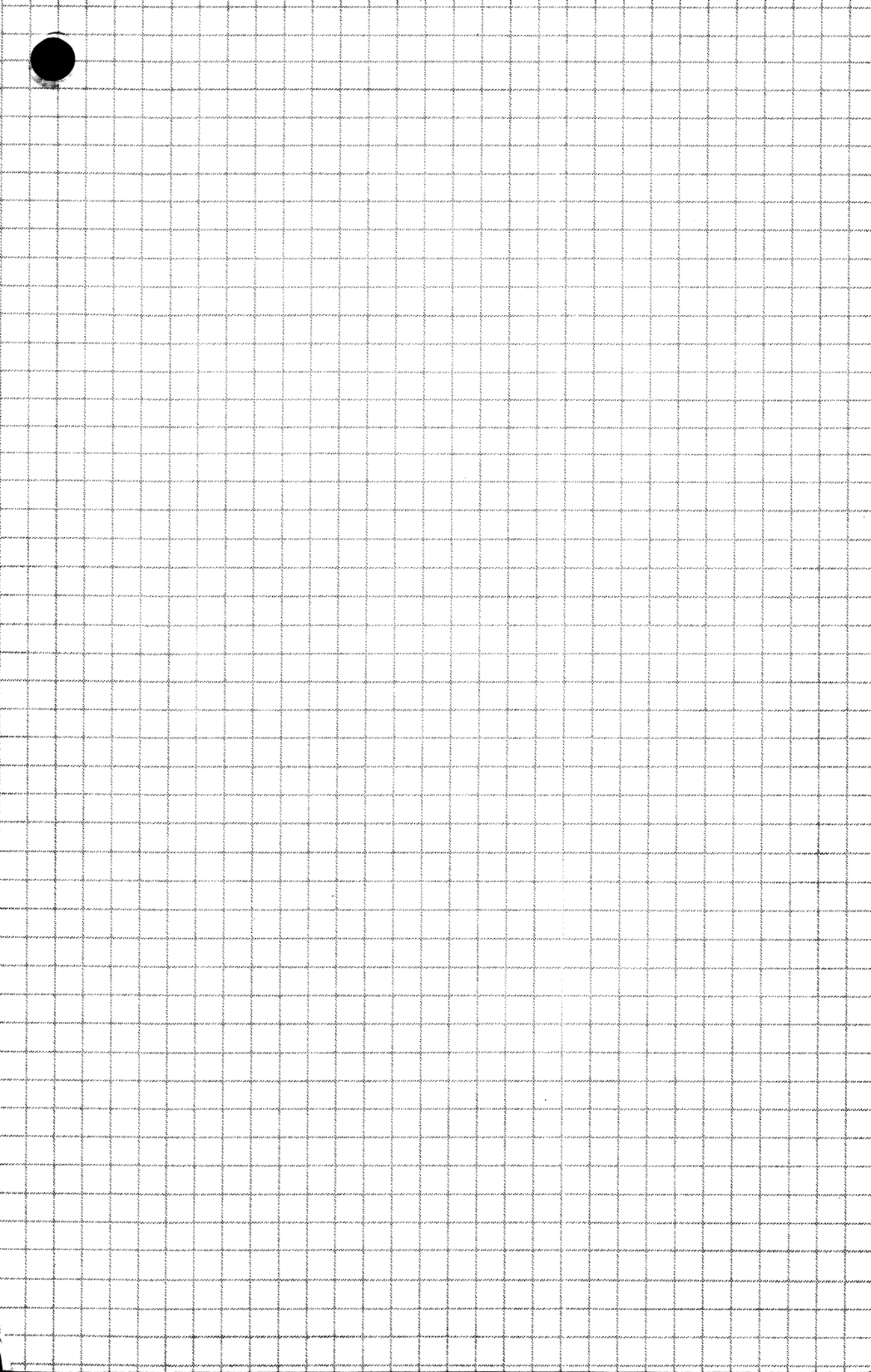

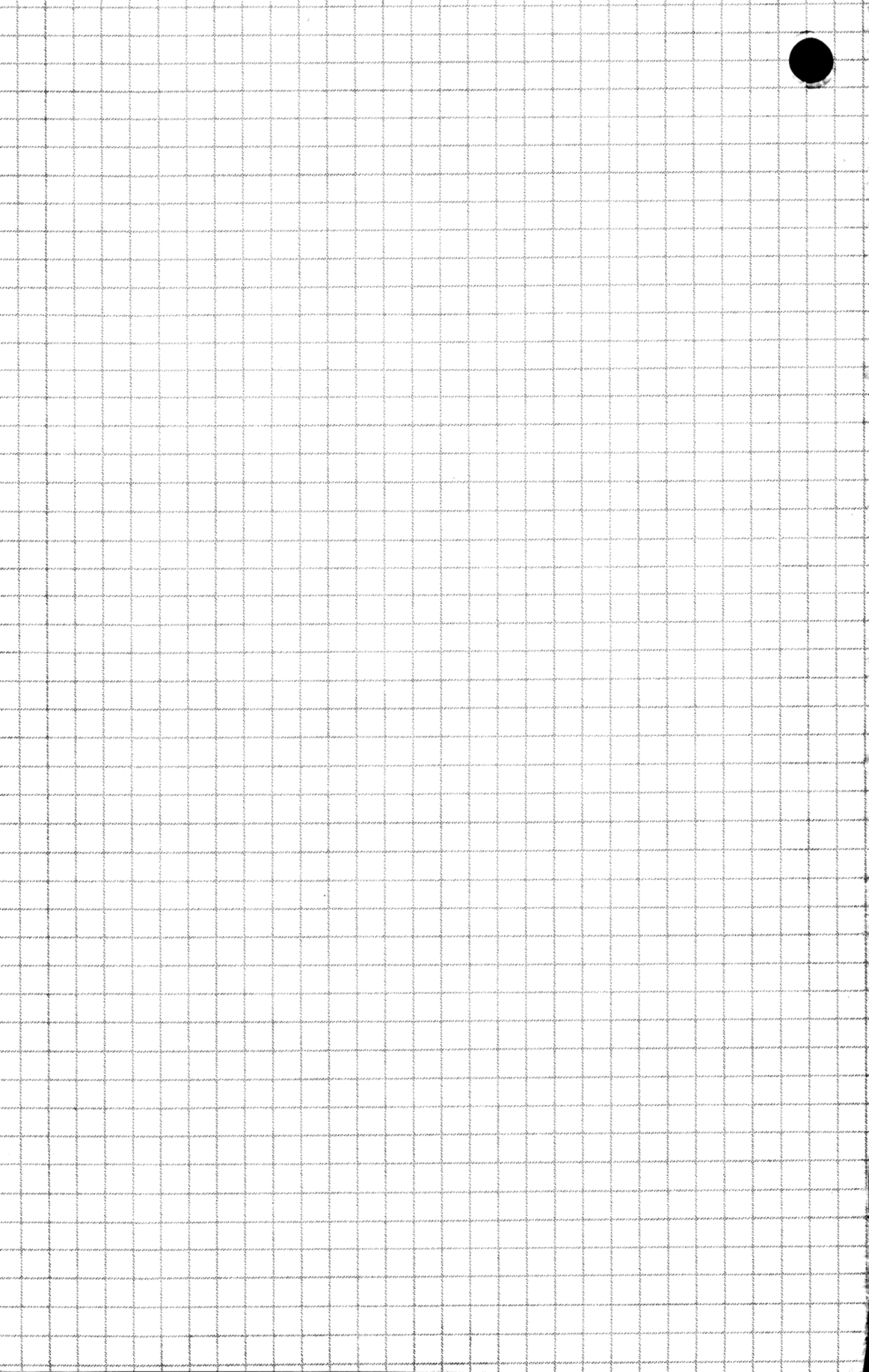

RESISTOR COLOR CODE

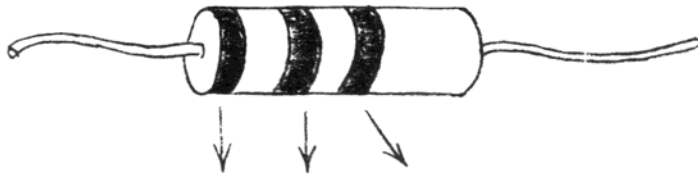

BLACK	0	0	$\times 1$
BROWN	1	1	$\times 10$
RED	2	2	$\times 100$
ORANGE	3	3	$\times 1,000$
YELLOW	4	4	$\times 10,000$
GREEN	5	5	$\times 100,000$
BLUE	6	6	$\times 1,000,000$
VIOLET	7	7	$\times 10,000,000$
GRAY	8	8	$\times 100,000,000$
WHITE	9	9	—

FOURTH BAND INDICATES TOLERANCE (ACCURACY):
 GOLD = $\pm 5\%$ SILVER = $\pm 10\%$ NONE = $\pm 20\%$

OHM'S LAW: $V = IR$ $R = V/I$
 $I = V/R$ $P = VI = I^2R$


ABBREVIATIONS

A = AMPERE	R = RESISTANCE
F = FARAD	V (OR E) = VOLT
I = CURRENT	W = WATT
P = POWER	Ω = OHM

M (MEG-)	= $\times 1,000,000$
K (KILO-)	= $\times 1,000$
m (MILLI-)	= .001
μ (MICRO-)	= .000 001
n (NANO-)	= .000 000 001
p (PICO-)	= .000 000 000 001

The original goal of the Mini-Notebooks included in this volume of the Engineer's Mini-Notebook Collection was to provide science project ideas for students and hobbyists. They succeeded admirably, for these little books have stimulated many science fair projects. They have also been popular with hobbyists of all ages. Even professional scientists have recommended them.

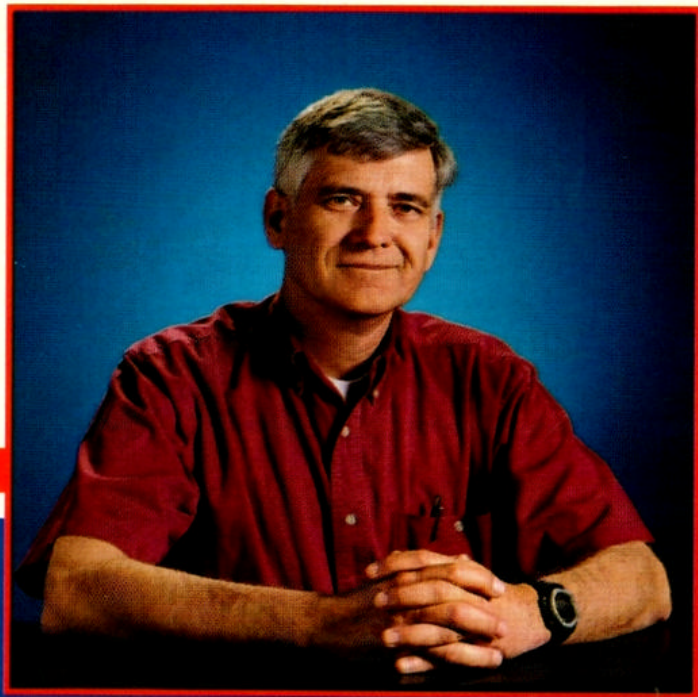The Mini-Notebooks in this volume are "Science Projects", "Environmental Projects" and "Communication Projects." Make a simple seismometer by hanging a magnet over a coil. Build a sun photometer to make accurate measurements of haze in the atmosphere. Study rain, lightning, clouds, sunlight, water, temperature and other topics. Build a wide variety of lightwave and radio communication circuits.



Forrest M. Mims III

Forrest M. Mims III has written dozens of books for RadioShack. He personally builds every circuit in his best-selling Engineer's Mini-Notebook series. He then uses a 0.7mm mechanical pencil to create pages for the finished book.

Building tiny instruments for model rockets, travel aids for the blind and high-power lasers is how Forrest got his start in electronics. When he's not writing RadioShack books, he writes magazine articles and teaches experimental science at the University of the Nations in Hawaii.

Forrest also does scientific studies of sunlight, the atmosphere, mosquitoes and bacteria using instruments he designs and makes. A simple instrument he developed to measure the ozone layer earned him a prestigious Rolex Award. NASA has sent Forrest and his instruments to several of the Western states and twice to Brazil to measure the effects of smoke from giant fires.

Forrest is a member of the Institute of Electrical and Electronics Engineers, the National Science Teachers Association and several scientific societies. He lives in Texas with his wife Minnie and their youngest daughter Sarah.

620-5033



0 40293 63773 6

Printed in USA